

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EPE EVERYDAY PRACTICAL ELECTRONICS

www.epemag.com

10-CHANNEL REMOTE CONTROL RECEIVER

Ideal for controlling motors, lights and relays
Uses any universal IR remote control
Infrared or UHF reception
Momentary or toggle operation

WIN ONE OF
TWO MICROCHIP
PICDEM 2 PLUS
BOARDS


LI'L PULSER MODEL TRAIN CONTROLLER

SMOOTH RUNNING WITH EXCELLENT
LOW-SPEED CONTROL



HUMAN COLOUR VISION

SIMPLE EXPERIMENTS TO TEST YOUR EYES!

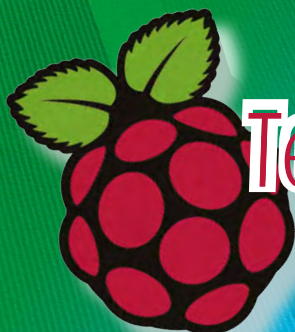

Teach-In 2014 Raspberry Pi - Part 10

EPE's comprehensive guide to Raspberry Pi

PLUS: PRACTICALLY SPEAKING, NET WORK, PIC N' MIX
CIRCUIT SURGERY AND TECHNO TALK

JULY 2014 £4.40



SPECIAL OFFERS
for full sales list
check our website

www.stewart-of-reading.co.uk

Check out our website, 1,000's of items in stock.

Used Equipment – **GUARANTEED**
All items supplied as tested in our Lab
Prices plus Carriage and VAT



FLUKE/PHILIPS PM3092
Oscilloscope
2+2 Channel 200MHZ
Delay TB, Autoset etc £295



FARNELL AP60/50 Power
Supply 0-60 Volt, 0-50 Amp
1KW Switch Mode £195



HP 54600B Oscilloscope
Analogue/Digital Dual
Trace 100MHZ £125



AGILENT E4402B Spectrum
Analyser
100HZ – 3GHZ with options £2950



HP 34401A Digital
Multimeter 6 1/2 Digit £325



MARCONI 2955B Radio
Communications Test Set £850



DRUCK DPI 515 Pressure
Controller/Calibrator £425



IFR 2025 Signal Generator
9KHZ – 2.51 GHZ Opt 04
High Stab, Opt 11
High Power £1250



HP SPECTRUM ANALYSERS –
Synthesised Check Options
8563A 9 KHZ – 22 GHZ £2750
8560A 50 HZ 2.9 GHZ £1950
8560E 30 HZ 2.9 GHZ £2400

STEWART OF READING

17A King Street, Mortimer, Near Reading, RG7 3RS
Telephone: 0118 933 1111 • Fax: 0118 933 2375

9am – 5pm, Monday – Friday

Please check availability before ordering or **CALLING IN**



UK designed,
UK made,
with pride.

Tel. 01298 70012
www.peakelec.co.uk
sales@peakelec.co.uk

Atlas House, 2 Kiln Lane
Harpur Hill Business Park
Buxton, Derbyshire
SK17 9JL, UK

Follow us on twitter
for tips, tricks and
news.
@peakatlas

For insured UK delivery:
Please add £3.00 inc VAT
to the whole order.
Check online or
give us a call for
overseas pricing.

PEAK[®]
electronic design ltd

LCR45 LCR and Impedance Meter with Auto and Manual modes

Brand new product!

Introducing a new powerful LCR meter that identifies your passive components (Inductors, Capacitors and Resistors) but also measures complex impedance, impedance with phase and admittance!

Auto and Manual test modes to allow you to specify the test frequency or component type.

- Continuous fluid measurements.
- Improved measurement resolution (<0.2µH, <0.2pF)




£99.95
£83.29+VAT

Component Summary
Inductor 23.6nH
L=123.4µH 0.200kH

Complex Impedance
Impedance 200kH
+25.6 +j155.1Ω

DCA75 The all new "A very capable analyser" DCA Pro

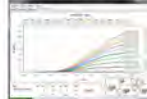Exciting new generation of semiconductor identifier and analyser. The **DCA Pro** features a new graphics display showing you detailed component schematics. Built-in USB offers amazing PC based features too such as curve tracing and detailed analysis in Excel. PC software supplied on a USB Flash Drive. Includes Alkaline AAA battery and comprehensive user guide.



Now Shipping
£115.95
£96.62+VAT

UTP05

- Identify and fault-find your network cabling.
- Comprehensive connection analysis.
- Detailed fault descriptions.
- Full colour wiring charts.
- Supplied with everything pictured here.

£77.95
£64.96+VAT



It's only possible to show summary specifications here. Please ask if you'd like detailed data. Further information is also available on our website. Product price refunded if you're not happy.

ISSN 0262 3617

• **PROJECTS • THEORY •**
• **NEWS • COMMENT •**
• **POPULAR FEATURES •**

VOL. 43. No 7

July 2014

EPE EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

www.epemag.com



Teach-In 2014
Raspberry Pi - Part 10



© Wimborne Publishing Ltd 2014. Copyright in all drawings, photographs and articles published in **EVERYDAY PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our August 2014 issue will be published on Thursday 3 July 2014, see page 72 for details.

Everyday Practical Electronics, July 2014

Projects and Circuits

VERSATILE 10-CHANNEL REMOTE CONTROL RECEIVER

10

by John Clarke

Superb 10-channel control system, couples with any universal IR remote control and even works with UHF!

LI'L PULSER MODEL TRAIN CONTROLLER

20

by John Clarke

Feature-loaded, high-current controller for the engine driver in all of us!

TWO DEMONSTRATION CIRCUITS FOR HUMAN COLOUR VISION

34

by James Goding

Simple, but fascinating experiments examine our perception of colour

Series and Features

TECHNO TALK by Mark Nelson

32

Fraudulent fridges and magic mushrooms

TEACH-IN 2014 by Mike and Richard Tooley

36

Part 10: Raspberry Pi: Real-time clock and improving user interfaces

MAX'S COOL BEANS by Max The Magnificent

48

From San Jose... ..to Hawaii

I didn't even know I wanted it... ..but I did!

PRACTICALLY SPEAKING by Robert Penfold

50

Project construction – the big picture

PIC N' MIX by Mike Hibbett

53

Revisiting the kitchen timer

AUDIO OUT by Jake Rothman

56

Working for yourself in electronics

CIRCUIT SURGERY by Ian Bell

58

Parallel batteries

NET WORK by Alan Winstanley

66

Feeling vulnerable

Not just browsers... Countdown to Zero

Intelligent lighting... Smart home

Regulars and Services

EPE BACK ISSUES – Did you miss these?

4

SUBSCRIBE TO EPE and save money

5

EDITORIAL

7

Support The National Museum of Computing

NEWS – Barry Fox highlights technology's leading edge

8

Plus everyday news from the world of electronics

MICROCHIP READER OFFER

33

EPE Exclusive – Win one of two Microchip PICDEM 2 Plus Boards

SUBSCRIBE TO EPE IN PDF VERSION and save money

IBC

RADIO BYGONES

61

CD-ROMS FOR ELECTRONICS

62

A wide range of CD-ROMs for hobbyists, students and engineers

DIRECT BOOK SERVICE

68

A wide range of technical books available by mail order, plus more CD-ROMs

EPE PCB SERVICE

70

PCBs for EPE projects

ADVERTISERS INDEX

71

NEXT MONTH! – Highlights of next month's EPE

72

Readers' Services • Editorial and Advertisement Departments

7

PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £9.95
18Vdc Power supply (661.121) £25.95
Leads: Parallel (LDC136) £3.95 / Serial (LDC441) £3.95 / USB (LDC644) £2.95

USB & Serial Port PIC Programmer



USB or Serial connection.
Header cable for ICSP.
Free Windows software.
See website for PICs supported.
ZIF Socket & USB lead extra. 16-18Vdc.

Kit Order Code: 3149EKT - £49.95

Assembled Order Code: AS3149E - £64.95

Assembled with ZIF socket Order Code: AS3149EZIF - £74.95

USB PIC Programmer and Tutor Board

This tutorial project board is all you need to take your first steps into Microchip PIC programming using a PIC16F882 (included). Later you can use it for more advanced programming. It programs all the devices a Microchip PICKIT2® can! You can use the free Microchip tools for the PICKIT2™ and the MPLAB® IDE environment.
Order Code: EDU10 - £55.96



ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. 16Vdc.



Kit Order Code: 3123KT - £28.95

Assembled Order Code: AS3123 - £39.95

Introduction to PIC Programming

Go from complete beginner to burning a PIC and writing code in no time! Includes 49 page step-by-step PDF Tutorial Manual + Programming Hardware (with LED test section) + Windows Software (Program, Read, Verify & Erase) + a rewritable PIC16F84A. 4 detailed examples provided for you to learn from. PC parallel port. 12Vdc.
Kit Order Code: 3081KT - £16.95
Assembled Order Code: AS3081 - £24.95



PIC Programmer Board

Low cost PIC programmer board supporting a wide range of Microchip® PIC™ microcontrollers. Serial port. Free Windows software.
Kit Order Code: K8076 - £29.94



PIC Programmer & Experimenter Board

PIC Programmer & Experimenter Board with test buttons and LED indicators to carry out educational experiments such as the supplied programming examples. Includes a 16F627 Flash Microcontroller that can be reprogrammed up to 1000 times. Software to compile and program your source code is included. Supply: 12-15Vdc.

Kit Order Code: K8048 - £23.94

Assembled Order Code: VM111 - £39.12



Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. 12Vdc PSU for all units: Order Code 660.446UK £11.52

USB Experiment Interface Board

5 digital input channels and 8 digital output channels plus two analogue inputs and two analogue outputs with 8 bit resolution.

Kit Order Code: K8055N - £25.19

Assembled Order Code: VM110N - £40.20



2-Channel High Current UHF RC Set

State-of-the-art high security. 2 channel. Momentary or latching relay output rated to switch up to 240Vac @ 10 Amps. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 3 indicator LEDs. Rx: PCB 88x60mm, supply 9-15Vdc.

Kit Order Code: 8157KT - £49.95

Assembled Order Code: AS8157 - £54.95



Computer Temperature Data Logger

Serial port 4-channel temperature logger. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor.

Kit Order Code: 3145KT - £19.95

Assembled Order Code: AS3145 - £26.95

Additional DS1820 Sensors - £4.95 each



Remote Control Via GSM Mobile Phone

Place next to a mobile phone (not included). Allows toggle or auto-timer control of 3A mains rated output relay from any location



4-Ch DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, **Rings** to Answer, Auto Hang-up and Lockout. Includes plastic case. 130 x 110 x 30mm. Power: 12Vdc.

Kit Order Code: 3140KT - £79.95

Assembled Order Code: AS3140 - £94.95



8-Ch Serial Port Isolated I/O Relay Module

Computer controlled 8 channel relay board. 5A mains rated relay outputs and 4 opto-isolated digital inputs (for monitoring switch states, etc). Useful in a variety of control and sensing applications. Programmed via serial port (use our new Windows interface, terminal emulator or batch files). Serial cable can be up to 35m long. Includes plastic case 130x100x30mm. Power: 12Vdc/500mA.

Kit Order Code: 3108KT - £74.95

Assembled Order Code: AS3108 - £89.95



Infrared RC 12-Channel Relay Board



Control 12 onboard relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112 x 122mm. Supply: 12Vdc/0.5A

Kit Order Code: 3142KT - £64.95

Assembled Order Code: AS3142 - £74.95

Audio DTMF Decoder and Display



Detect DTMF tones from tape recorders, receivers, two-way radios, etc using the built-in mic or direct from the phone line. Characters are displayed on a

16 character display as they are received and up to 32 numbers can be displayed by scrolling the display. All data written to the LCD is also sent to a serial output for connection to a computer. Supply: 9-12V DC (Order Code PSU375). Main PCB: 55x95mm.

Kit Order Code: 3153KT - £37.95

Assembled Order Code: AS3153 - £49.95

3x5Amp RGB LED Controller with RS232

3 independent high power channels. Preprogrammed or user-editable light sequences. Standalone option and 2-wire serial interface for microcontroller or PC communication with simple command set. Suitable for common anode RGB LED strips, LEDs and incandescent bulbs. 56 x 39 x 20mm. 12A total max. Supply: 12Vdc.

Kit Order Code: 8191KT - £29.95

Assembled Order Code: AS8191 - £39.95



Hot New Products!

Here are a few of the most recent products added to our range. See website or join our email Newsletter for all the latest news.

4-Channel Serial Port Temperature Monitor & Controller Relay Board

4 channel computer serial port temperature monitor and relay controller. Four inputs for Dallas DS18S20 or DS18B20 digital thermometer sensors (£3.95 each). Four 5A rated relay outputs are independent of sensor channels allowing flexibility to setup the linkage in any way you choose. Simple text string commands for reading temperature and relay control via RS232 using a comms program like Windows HyperTerminal or our free Windows application.

Kit Order Code: 3190KT - £84.95

Assembled Order Code: AS3190 - £99.95



40 Second Message Recorder

Feature packed non-volatile 40 second multi-message sound recorder module using a high quality Winbond sound recorder IC.

Standalone operation using just six onboard buttons or use onboard SPI interface. Record using built-in microphone or external line in. 8-24Vdc powered. Change a resistor for different recording duration/sound quality. Sampling frequency 4-12 kHz. (120 second version also available)

Kit Order Code: 3188KT - £29.95

Assembled Order Code: AS3188 - £37.95



Bipolar Stepper Motor Chopper Driver

Get better performance from your stepper motors with this dual full bridge motor driver based on SGS Thompson chips L297 & L298. Motor current for each phase set using on-board potentiometer. Rated to handle motor winding currents up to 2 Amps per phase. Operates on 9-36Vdc supply voltage. Provides all basic motor controls including full or half stepping of bipolar steppers and direction control. Allows multiple driver synchronisation. Perfect for desktop CNC applications.

Kit Order Code: 3187KT - £39.95

Assembled Order Code: AS3187 - £49.95



Video Signal Cleaner

Digitally cleans the video signal and removes unwanted distortion in video signal. In addition it stabilises picture quality and luminance fluctuations. You will also benefit from improved picture quality on LCD monitors or projectors.

Kit Order Code: K8036 - £24.70

Assembled Order Code: VM106 - £36.53



Motor Speed Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (100V/7.5A)

Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H.

Kit Order Code: 3067KT - £19.95

Assembled Order Code: AS3067 - £27.95



Bidirectional DC Motor Speed Controller

Control the speed of most common DC motors (rated up to 32Vdc/10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections.

Kit Order Code: 3166v2KT - £23.95

Assembled Order Code: AS3166v2 - £33.95



Computer Controlled / Standalone Unipolar Stepper Motor Driver

Drives any 5-35Vdc 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps. Provides speed and direction control. Operates in stand-alone or PC-controlled mode for CNC use. Connect up to six 3179 driver boards to a single parallel port. Board supply: 9Vdc. PCB: 80x50mm.

Kit Order Code: 3179KT - £17.95

Assembled Order Code: AS3179 - £24.95



Computer Controlled Bi-Polar Stepper Motor Driver

Drive any 5-50Vdc, 5 Amp bi-polar stepper motor using externally supplied 5V levels for STEP and DIRECTION control. Opto-isolated inputs make it ideal for CNC applications using a PC running suitable software. Board supply: 8-30Vdc. PCB: 75x85mm.

Kit Order Code: 3158KT - £24.95

Assembled Order Code: AS3158 - £34.95



AC Motor Speed Controller (600W)

Reliable and simple to install project that allows you to adjust the speed of an electric drill or 230V AC single phase induction motor rated up to 600 Watts. Simply turn the potentiometer to adjust the motors RPM. PCB: 48x65mm. Not suitable for use with brushless AC motors.

Kit Order Code: 1074KT - £15.95

Assembled Order Code: AS1074 - £23.95



See website for lots more DC, AC and stepper motor drivers!



QUASAR
electronics
The Electronic Kit Specialists Since 1993

Credit Card Sales
01279 467 799

Electronic Project Labs

Great introduction to the world of electronics. Ideal gift for budding electronics expert!

130-in-1 Electronic Project Lab

Get started on the road to a great hobby or career in electronics. Contains all the parts and instructions to assemble 130 educational and fun experiments and circuits. Build a radio, AM broadcast station, electronic organ, kitchen timer, logic circuits and more. Built-in speaker, 7-segment LED display, two integrated circuits and rotary controls. Manual has individual circuit explanations, schematic and connection diagrams. Requires 6 x AA batteries (not included). Suitable for age 14+.

Order Code EPL500 - £49.95

Also available: 30-in-1 £22.95, 50-in-1

£29.95, 75-in-1 £39.95

See website for full details.



Tools & Test Equipment

We stock an extensive range of soldering tools, test equipment, power supplies, inverters & much more - please visit website to see our full range of products.

Advanced Personal Scope 2 x 240MS/s

Features 2 input channels - high contrast LCD with white backlight - full auto set-up for volt/div and time/div - recorder roll mode, up to 170h per screen - trigger mode: run - normal - once - roll ... - adjustable trigger level and slope and much more.

Order Code: APS230 - £374.95 £274.96



Handheld Personal Scope with USB

Designed by electronics enthusiasts for electronics enthusiasts! Powerful, compact and USB connectivity, this sums up the features of this oscilloscope.

40 MHz sampling rate, 12 MHz analog bandwidth, 0.1 mV sensitivity, 5mV to 20V/div in 12 steps, 50ns to 1 hour/div time base in 34 steps, ultra fast full auto set up option, adjustable trigger level, X and Y position signal shift, DVM readout and more...

Order Code: HPS50 - £289.96 £204.00

See website for more super deals!



www.quasarelectronics.co.uk

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

We can supply back issues of *EPE* by post, most issues from the past five years are available. An *EPE* index for the last five years is also available at www.epemag.com. Where we are unable to provide a back issue a photocopy of any one article (or one part of a series) can be purchased for the same price. Issues from Jan. 99 are available on CD-ROM or DVD-ROM – and back issues from recent years are also available to download from www.epemag.com. Please make sure all components are still available before commencing any project from a back-dated issue.

DID YOU MISS THESE?



BACK ISSUES ONLY £5.00 (each inc. UK p&p.)

Overseas prices £5.80 each surface mail, £6.80 each airmail.

We can also supply issues from years: 2006 (except Jan., Feb., Mar., Apr., May, July), 2007 (except June, July, Aug), 2008 (except Aug, Nov, Dec) 2009 (except Jan, Mar, Apr), 2010 (except May, June, July, August, Oct, Nov, Dec) 2011 (except Jan) Jan 2014.

MAY '13

PROJECTS • Electronic Stethoscope • PIC/AVR Programming Adaptor Board – Part 1 • Cheap, High-Current Bench Supply • Ingenuity Unlimited
FEATURES • Jump Start – Signal Injector Probe • Techno Talk • Raspberry Pi • PIC N' Mix • Circuit Surgery • Practically Speaking • Max's Cool Beans • Net Work

JUNE '13

PROJECTS • Mix-It • PIC/AVR Programming Adaptor Board – Part 2 • A Handy USB Breakout Box • Converter For Neon Lamp Experiments • Ingenuity Unlimited
FEATURES • Jump Start – Simple Radio Receiver • Techno Talk • PIC N' Mix • Circuit Surgery • Interface • Max's Cool Beans • Net Work

JULY '13

PROJECTS • 6-Decade Capacitance Substitution Box • Soft Starter For Power Tools • High Power Brushless Motors From Old CD/DVD Drives • High-Current Adaptor For Scopes And DMMs
FEATURES • Jump Start – Temperature Alarm • Techno Talk • Circuit Surgery • Practically Speaking • Max's Cool Beans • Net Work

AUG '13

PROJECTS • Driveway Sentry • Milliohm Meter Adaptor For DMMs • Build A Vox • Superb Four-Channel Amplifier – On The Cheap
FEATURES • Techno Talk • Circuit Surgery • Interface • Max's Cool Beans • Net Work • Computer Error: Reliable Digital Processing – Part 1

SEPT '13

PROJECTS • Digital Sound Effects Module • USB Stereo Recording & Playback Interface • Vacuum Pump From Junk • Minireg 1.3-22V Adjustable Regulator • Ingenuity Unlimited
FEATURES • Techno Talk • Circuit Surgery • Practically Speaking • Max's Cool Beans • Net Work • Computer Error: Reliable Digital Processing – Part 2

OCT '13

PROJECTS • LED Musicolour – Part 1 • High-Temperature Thermometer/Thermostat • Ingenuity Unlimited
FEATURES • Teach-In 2014 – Part 1 • Techno Talk • Circuit Surgery • Interface • Max's Cool Beans • Net Work • Computer Error: Reliable Digital Processing – Part 3

NOV '13

PROJECTS • CLASSiC-D Amplifier – Part 1 • LED Musicolour – Part 2 • Mains Timer For Fans Or Lights • Ingenuity Unlimited
FEATURES • Teach-In 2014 – Part 2 • Techno Talk • Circuit Surgery • Practically Speaking • Max's Cool Beans • Net Work

DEC '13

PROJECTS • Six Test Instruments In One Tiny Box • Virtins Technology Multi-Instrument 3.2 • CLASSiC-D Amplifier – Part 2 •
FEATURES • Teach-In 2014 – Part 3 • Techno Talk • Circuit Surgery • Interface • Max's Cool Beans • Net Work

JAN '14

PROJECTS • 2.5GHz 12-Digit Frequency Counter With Add-on GPS Accuracy – Part 1 • The Champion Amplifier • Simple 1.5A Switching Regulator •
FEATURES • Teach-In 2014 – Part 4 • Techno Talk • Circuit Surgery • Practically Speaking • Max's Cool Beans • Net Work • PIC N' Mix • Net Work

FEB '14

PROJECTS • High-energy Electronic Ignition System – Part 1 • Mobile Phone Loud Ringer! • 2.5GHz 12-Digit Frequency Counter With Add-on GPS Accuracy – Part 2
FEATURES • Teach-In 2014 – Part 5 • Techno Talk • Circuit Surgery • Interface • Max's Cool Beans • Net Work • PIC N' Mix • Net Work

MAR '14

PROJECTS • Infrasonic Detector • Extremely Accurate GPS 1pps Timebase For A Frequency Counter • High-energy Electronic Ignition System – Part 2 • Automatic Points Controller For Your Model Railway Layout
FEATURES • Teach-In 2014 – Part 6 • Techno Talk • Circuit Surgery • Practically Speaking • Max's Cool Beans • Net Work • PIC N' Mix • Net Work

APR '14

PROJECTS • Jacobs Ladder • Deluxe GPS 1pps Timebase For Frequency Counters • Capacitor Discharge Unit For Twin-Coil Points Motors
FEATURES • Teach-In 2014 – Part 7 • Techno Talk • Circuit Surgery • Interface • Max's Cool Beans • Net Work • PIC N' Mix • Net Work • Beta-Layout's Re-Flow Oven Kit And Controller review

MAY '14

PROJECTS • Rugged Battery Charger • CLASSiC-D $\pm 35V$ DC-DC Converter • Digital Multimeter Auto Power-Down • Control Relays Over The Internet With Arduino
FEATURES • Teach-In 2014 – Part 8 • Techno Talk • Circuit Surgery • Practically Speaking • Max's Cool Beans • Net Work • PIC N' Mix • Net Work •

JUNE '14

PROJECTS • Cranial Electrical Stimulation Unit • Mini Audio Mixer • Adding Voltage And Current Meters To The Bits 'N' Pieces Battery Charger •
FEATURES • Teach-In 2014 – Part 9 • Techno Talk • Circuit Surgery • Interface • Max's Cool Beans • PIC N' Mix • Net Work •

Where we do not have an issue a photocopy of any one article or one part of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOCOPIES – INDEXES

☐ Send back issues dated.

☐ Send photocopies of (article title and issue date)

Name

Address

Tel:

☐ I enclose cheque/P.O./bank draft to the value of £

☐ Please charge my Visa/Mastercard/Maestro £

Card No. Maestro Issue No.

Valid From Card Expiry Date Card Security Code
(The last 3 digits on or just under the signature strip)

SEND TO: **Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU.**
Tel: 01202 880299. Fax: 01202 843233.
E-mail: orders@epemag.wimborne.co.uk On-line Shop: www.epemag.com

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally posted within seven days of receipt of order. Send a copy of this form, or order by letter if you do not wish to cut your issue. M07/14

UK readers you can **SAVE 81p** on every issue of **EPE**

How would you like to pay £3.59 instead of £4.40 for your copy of **EPE**?



Well you can – just take out a one year subscription and save **81p** an issue, or **£9.80** over the year. You can even save **£1.08** an issue if you subscribe for two years – a total saving of **£26.10**.

Overseas rates also represent exceptional value.

You also:

- Avoid any cover price increase for the duration of your subscription
- Get your magazine delivered to your door each month
- Ensure your copy, even if the newsagents sell out

Order by phone or fax with a credit card or by post with a cheque or postal order, or buy online from www.epemag.com (go to the Online Shop).

EPE EVERYDAY PRACTICAL ELECTRONICS

SUBSCRIPTION PRICES

Subscriptions for delivery direct to any address in the UK: 6 months £23.50, 12 months £43.00, two years £79.50; Europe Airmail: 6 months £27.00, 12 months £50.00, 24 months £95.00; Rest Of The World Airmail: 6 months £37.00, 12 months £70.00, 24 months £135.00.

Cheques or bank drafts (in **£ sterling only**) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Tel: 01202 880299. Fax: 01202 843233. Email: subs@wimborne.co.uk. Also via the Web at: www.epemag.com.

Subscriptions start with the next available issue. We accept MasterCard, Maestro or Visa. (For past issues see the Back Issues page.)

ONLINE SUBSCRIPTIONS

Online subscriptions, for reading the magazine via the Internet, £19.99 for one year, visit www.epemag.com for more details.

SUBSCRIPTION ORDER FORM

- ☐ 6 Months: UK £23.50, Europe £27.00 (Airmail), Rest Of The World £37.00 (Airmail)
☐ 1 Year: UK £43.00, Europe £50.00 (Airmail), Rest Of The World £70.00 (Airmail)
☐ 2 Years: UK £79.50, Europe £95.00 (Airmail), Rest Of The World £135.00 (Airmail)

To: Everyday Practical Electronics,
 Wimborne Publishing Ltd., 113 Lynwood Drive, Merley,
 Wimborne, Dorset BH21 1UU
 Tel: 01202 880299 Fax: 01202 843233
 E-mail: subs@epemag.wimborne.co.uk

I enclose payment of £ (cheque/PO in £ sterling only), payable to *Everyday Practical Electronics*

☐ Please charge my Visa/Mastercard/Maestro

My card number is:
 Please print clearly, and check that you have the number correct

Signature

Card Security Code Valid From Date.....
 (The last 3 digits on or just under the signature strip)

Card Ex. DateMaestro Issue No.

Name

Address

Post code Tel.

Subscriptions can only start with the next available issue.



Sales: 0845 251 4363 Online: www.esr.co.uk/epe

ANTEX



£127.76
Inc Delivery* & VAT

Antex 660TC Soldering Station

~~£174~~ RRP

Includes: Solder & HQ Desolder Pump
50W Temperature Controlled Soldering station, adjustable temp 65-425°C, Stand with sponge included Quote: EPE660

FREE DVM worth £19.96

FREE
with every order

3½ Digital Class III 600V DVM
AC / DC Voltage upto 600V
DC Current upto 10A
Resistance upto 20M
Audible Continuity
One per customer, while stocks last
offer valid until: end of July 2014



New Lower Price
£574.80
Inc Delivery* & VAT

FREE

2.4GHz Frequency Counter

0.01Hz to 2.4GHz
8 Digit LED Display
Gate Time: 100ms to 10s
2 Channel Operating mode
Power Supply: 110-220Vac 5W
Quote: EPE24G

valleman

£81.00
Inc Delivery* & VAT





3D Printer Kit K8200

Build your own 3D Printer.

FREE 1kg Roll of Filament# with every order worth over £27

Print objects upto 200 x 200 x 200mm via your PC or stand alone controller (VM8201 available separately) The High Quality self assembly kit is an advanced level kit, requiring mechanical & electronic constructional experience. # Colour may vary. Quote: EPE3D

Repetier
Uses **FREE** Software

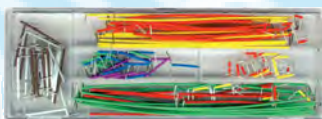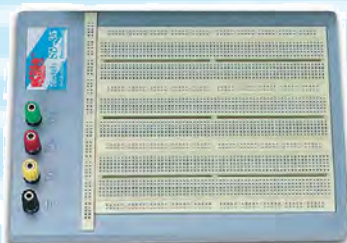

£77.62
Inc Delivery* & VAT

Breadboard & Components Starter Pack

A High Quality Large Breadboard with binding posts, a 140 piece Jump Wire Kit and 6 Component Packs with over 1100 components. Quote: EPEBCS



Over 1100 Components

30V 5A Programmable PSU

Dual LED (Voltage & Current) Displays
Course & Fine V / A Adjustment
5 Programmable Memories
PC Link via USB or RS232
Output: 0-30Vdc
0-5A

Quote: EPEPSU

£114.00
Inc Delivery* & VAT




Build your own Oscilloscope

A new self assembly kit, ideal for education and way to visualise signals. Features: Markers, Frequency, dB, True RMS readouts
Timebase range:
10µs-500ms/division (15 steps)
Input sensitivity:
100mV-5V/division (6 steps)
Max Input voltage: 30Vpp
Max Sample Rate:
1ms/s repetitive signal,
100ks/s real time signal
Dim: 80 x 115 x 40mm

Quote: EPESCOPE

£65.00
Inc Delivery* & VAT

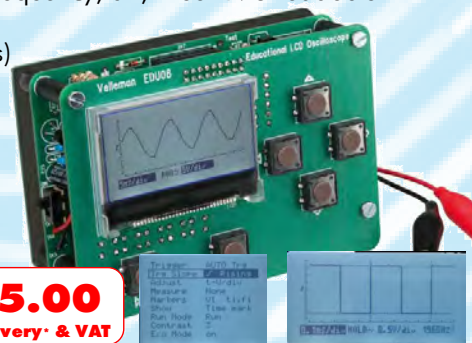

Tel: 0191 2514363
Fax: 0191 2522296
sales@esr.co.uk

Station Road
Cullercoats
Tyne & Wear
NE30 4PQ



Prices **INCLUDE** Delivery* & VAT.
*Delivery to any UK Mainland address, please call for delivery options for Highland & Island, Northern Ireland, Ireland, Isle of Man, Isle of Wight & Channel Islands

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS
 EDITORIAL Wimborne Publishing Ltd., 113 Lynwood
 Drive, Merley, Wimborne, Dorset, BH21 1UU
Phone: (01202) 880299. **Fax:** (01202) 843233.
Email: fay.kearn@wimborne.co.uk
Website: www.epemag.com

See notes on **Readers' Technical Enquiries** below
 – we regret technical enquiries cannot be answered
 over the telephone.

Advertisement Offices:

Everyday Practical Electronics Advertisements
 113 Lynwood Drive, Merley, Wimborne, Dorset,
 BH21 1UU
Phone: 01202 880299 **Fax:** 01202 843233
Email: stewart.kearn@wimborne.co.uk

Editor: MATT PULZER
Subscriptions: MARILYN GOLDBERG
General Manager: FAY KEARN
Graphic Design: RYAN HAWKINS
Editorial/Admin: 01202 880299
**Advertising and
 Business Manager:** STEWART KEARN
 01202 880299
On-line Editor: ALAN WINSTANLEY

Publisher: MIKE KENWARD

READERS' TECHNICAL ENQUIRIES

Email: fay.kearn@wimborne.co.uk

We are unable to offer any advice on the use, purchase,
 repair or modification of commercial equipment or the
 incorporation or modification of designs published
 in the magazine. We regret that we cannot provide
 data or answer queries on articles or projects that are
 more than five years' old. Letters requiring a personal
 reply must be accompanied by a stamped self-
 addressed envelope or a self-addressed envelope and
 international reply coupons. We are not able to answer
 technical queries on the phone.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that
 the advice and data given to readers is reliable. We
 cannot, however, guarantee it and we cannot accept
 legal responsibility for it.

A number of projects and circuits published in
 EPE employ voltages that can be lethal. You should
 not build, test, modify or renovate any item of mains-
 powered equipment unless you fully understand the
 safety aspects involved and you use an RCD adaptor.

COMPONENT SUPPLIES

We do not supply electronic components or kits for
 building the projects featured, these can be supplied
 by advertisers.

We advise readers to check that all parts are still
 available before commencing any project in a back-
 dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY
 PRACTICAL ELECTRONICS take reasonable
 precautions to protect the interests of readers by
 ensuring as far as practicable that advertisements are
 bona fide, the magazine and its publishers cannot give
 any undertakings in respect of statements or claims
 made by advertisers, whether these advertisements
 are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances
 will the magazine accept liability for non-receipt of
 goods ordered, or for late delivery, or for faults in
 manufacture.

**TRANSMITTERS/BUGS/TELEPHONE
EQUIPMENT**

We advise readers that certain items of radio
 transmitting and telephone equipment which may
 be advertised in our pages cannot be legally used in
 the UK. Readers should check the law before buying
 any transmitting or telephone equipment, as a fine,
 confiscation of equipment and/or imprisonment can
 result from illegal use or ownership. The laws vary from
 country to country; readers should check local laws.

EPE EVERYDAY PRACTICAL ELECTRONICS

Support The National Museum of Computing

Bletchley Park – the once top-secret British home of world-beating WWII
 German codebreaking that saved countless lives and helped end the war
 – looks like it's about to be turned into an iPod-Touch-powered tourist
 theme park sponsored by £5 million of Heritage Lottery funds.

It's great to see that the work of Bletchley Park is being made more
 attractive and accessible to today's more sophisticated visitors ensuring our
 proud history can be kept alive. In contrast, the on-camp home of Colossus,
 arguably the world's first electronic supercomputer, rebuilt and housed at
 The National Museum of Computing (TNMOC) in one of Bletchley Park's
 blocks (H) next door, claims it's being starved of through-visitors due to a
 turf war between them and Bletchley Park's theme park owners.

Thanks to TNMOC, it's possible to track the evolution of electronic
 computing from that top-secret era of WWII through to the mainframes
 of the 1950s, then to the dawn of personal computing in the 1980s and
 beyond. TNMOC is desperate for funding, and previous sponsors have
 included IBM, HP, Google UK and encryption specialists Pretty Good
 Privacy. Unbelievably, the Museum also has to pay Bletchley Park for rent
 and overheads.

In the West, we pretty much owe our freedom to the likes of both
 Bletchley Park and the world-class codebreakers who used British
 computing expertise to crack the 'unbreakable' codes of the German
 Enigma machine. Unsung heroes do much valuable work and it's a
 scandal that TNMOC should have to rely on handouts and industry
 funding to keep their charity alive.

Bletchley Park, funded by Heritage Lottery cash (ours) should be doing
 everything possible to support the fantastic work of TNMOC instead of
 fencing off Block H, and we understand that Arts Council England was
 hoping to mediate between the two interests. It is very much to be hoped
 that these two 'natural allies' find a better way to support each other so that
 the remarkable wartime story of the Colossus computer will live on in a
 spirit of mutual co-operation rather than one of bitter rivalry. Readers can
 help by 'Sponsoring a Valve' (vacuum tube) at: www.colossusonline.org


Kickstarter success

I hope readers will join me congratulating Mike Hibbett for his dramatic
 Kickstarter project success (see last month's *Editorial*). Mike's 'Low Power,
 Low Cost Microprocessor Development Board' was pitched modestly
 at £1100 to succeed. At the end of the funding period he achieved a
 remarkable £4225! More details at: <http://tinyurl.com/n7x2zv>

New columnist

Last, but not least, I'd like to introduce a new regular writer to EPE – Jake
 Rothman. Jake has produced projects for us before, and now has his own
 monthly slot. He'll mostly be writing about audio and analogue, but this
 month kicks off with a great article on working for yourself in electronics
 – welcome aboard Jake!

Alan Winstanley
 EPE On-line editor

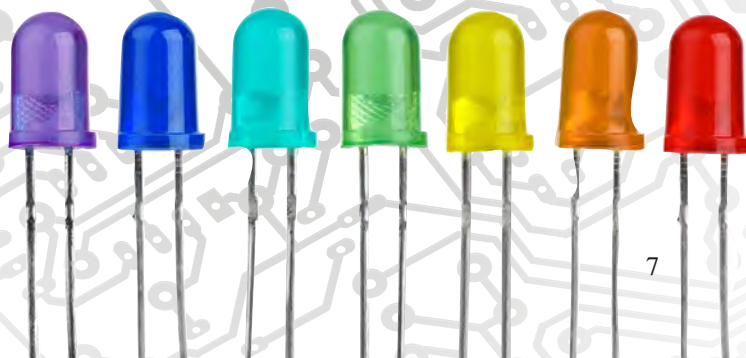

NEWS

A roundup of the latest Everyday News from the world of electronics



The push to Ultra HDTV – report by Barry Fox

Although 4k Ultra HDTV sets are already on sale, there is no standard for the system. Japanese broadcasters want to push on to 8k, with broadcasts to the home in time for the 2020 Tokyo Olympics.

4k or not 4k?

The SMPTE, Society of Motion Picture & Television Engineers, is trying to set the standards for both 4k and 8k, which are more accurately called UHDTV1 (3840 × 2160 pixels) and UHDTV2 (7680 × 4320), and build on today's (HDTV (1920 × 1080 pixels).

The popular consumer term '4k' is confusing, warns the SMPTE, because 4k actually defines images with 4096 × 2160 pixels, the professional Digital Cinema standard.

Gamut standards

UHDTV is not just about more pixels per picture. It also brings extended colour space to the table; essentially a wider (twice as wide) range or 'gamut' of colours than HDTV. But so far, the existing HDTV colour gamut has had to be used because of camera and display limitations. There are no TVs yet that can support the UHDTV colour gamut. So, conversion techniques to and from HD, SD and UHD will be needed.

This, warns the SMPTE bluntly, is 'NOT trivial'. Simplistic conversion may make UHD colour look worse than original HD material. Content with UHDTV gamut may look worse on HDTV than native HDTV.

Techniques used for HD conversion won't be good for UHD conversions. Colours will look over-saturated or muted. Manual grading, scene by scene, as used for Blu-ray releasing, may be needed.

Frame rate

The existing TV frame rates (50 and 60Hz) are accepted as not good enough for UHD action capture and panning; 100Hz and 120Hz are favoured as the best compromises, with 120Hz proposed as a possible world standard.

The frame rate for NTSC is not exactly 30Hz, it is 23.97Hz (set 50 years ago to avoid interference between analogue colour and sound signals). So, for legacy material, UHD will need to support a slightly-off-120Hz rate (120Hz divided by 1.001).

There will also be a need for time code that runs at speeds higher than 60Hz (to synchronise cameras and

UHD also opens the door to high dynamic range pictures, which are brighter, with a wider contrast range between black and pure white.

The latest TVs can now display over 500cdm⁻² (candela per square metre) – and up to 1000cdm⁻² – and there is far less noise or snow to degrade the picture. But the number of digital bits which video signals use to code the range of brightness (or grey scale) from black to white (usually 10 bits, maximum 12 bits) is set by industry standards. So there is a need for more efficient coding to make better use of the bits available and improve the 'electro-optical transfer function' (EOTF) or gamma encoding without the need to change the whole ecosystem.

Coding

Current coding systems date back to the days of CRTs and show visible steps in the grey scale – rather than a smooth transition between different shades of grey – even when 12 bits are used.

The SMPTE is looking at ways of making the EOTF more closely match the way the human eye detects brightness. A new PQ

'perceptual quantiser' curve lets 12 bits accurately describe a far wider brightness range – up to 1 million:1 contrast ratio. Often 11, 10 or even 9 bits are able to disguise the steps between shades of grey, with brightness up to 10,000cdm⁻².

PQ is based on the brightness levels actually seen on a screen rather than the levels captured by the camera. It relies on test patterns, which concentrate on the most sensitive part of the human eye/brain system, the region near white or grey.



When is 4k actually 4k – and will it be quickly superseded by 8k?

recorders), as well as a new standard for digital 'interfaces' to connect UHD equipment running at higher than 60Hz. But there may also be 'mezzanine' compression standards to let new UHD equipment use existing interfaces.

A standard is also needed for 'immersive audio' with up to 22.2 channels (22 main and 2 sub-woofer) for surround with height. And consideration must be given to the fact that most homes will not have 22.2 speaker systems.

Super-fast-charging batteries

An Israeli start-up called StoreDot has demonstrated a device made of biological structures, which when substituted for a Samsung S4 smartphone battery went from dead to fully charged in just 26s.

StoreDot uses a novel technology, based on its discovery of new generation, self-assembled 'nanodots'. These elementary biological building blocks are at the core of several patented innovations by StoreDot. The nanodots are nano-crystals, uniform in size, 2.1nm in diameter, and consist of bio-organic peptide molecules.


Thanks to their small size, nanodots improve electrode capacitance and electrolyte performance and the end result is batteries that can be fully charged in seconds rather than hours.

StoreDot have effectively developed a new kind of electrode. The electrolyte is modified with nanodots in order to make the multifunction electrode more effective. On one side it acts like a supercapacitor (with very fast charging), and on the other it is like a lithium electrode (with slow discharge).

StoreDot claim that unlike other nanodot and quantum-dot materials that are based on heavy metals – making them toxic – its nanodots are produced from a range of bio-organic materials that are cheap and environmentally-friendly.

StoreDot is currently working on smartphone-sized batteries, but sees no reason why its technology could not be scaled to car batteries, which would revolutionise that sector.

GPS tracking bracelet

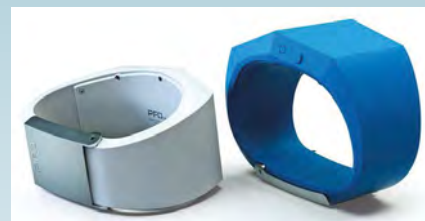

PFO Tech has launched a GPS tracking bracelet designed for reporters. Journalism can be one of the most dangerous professions today, and in places like Syria it is often called 'an impossible job.' Journalists risk attacks, imprisonment and even death for seeking to tell the truth. The bracelet was launched at the World Press Freedom Day at UNESCO Headquarters aimed in part to address the safety of journalists, adding to a Declaration that highlights the contribution of free expression to development.

PFO's solution includes a GPS bracelet with patented alarm mechanism, a secure monitoring system, a mobile application and hosting service. By triggering the alarm, a journalist can send their live position to pre-chosen recipients such as headquarters, alarm receiving centres, colleagues nearby, and even out on social media platforms to involve the whole world in the event of an attack.

Smartphone 'value'

New research from mobile network Three has found Brits value the content of their smartphone at £1,117 – six times the value of the phone itself (average value £199).


Nearly half (47%) of those polled would rather lose their passport than their smartphone and a third (38%) don't know how to back up their smartphone.

The research found that smartphone users place the most sentimental value on photographs, while their list of contacts came in second. These were followed by banking details, videos, work, music, films and then games.

Regarding photographs, the average Brit values their mobile snaps at £357. Photos and videos can hold a huge amount of sentimental value to owners, who on average store more than 100 of them on their device. Half of all parents (54 per cent) store photos of their children on their phone and do not back them up elsewhere. Ironical, given that one in ten parents have had their smartphones smashed, destroyed or otherwise put out of operation by their children.

The world's smallest movie

The ability to move single atoms, one of the smallest particles of any element in the universe, is crucial to research in the field of atomic-scale memory. In 2012, IBM scientists announced the creation of the world's smallest magnetic memory bit, made of just 12 atoms. This breakthrough could transform computing by providing the world with devices that have access to unprecedented levels of data storage. But even nanophysicists need to have a little fun. In that spirit, IBM researchers used a scanning tunneling microscope to move thousands of carbon monoxide molecules (two atoms stacked on top of each other), all in pursuit of making a movie so small it can be seen only when you magnify it 100

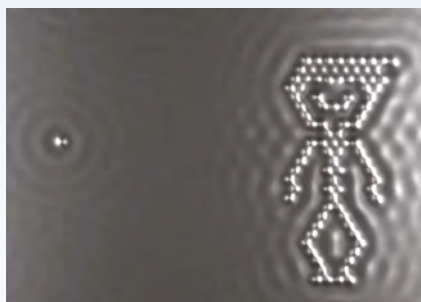

million times. The resulting atomic movie has been verified by Guinness World Records as the world's smallest stop-motion film. In other words, discrete atoms have been repositioned and then an image taken to create the stop-motion effect, a little like a cartoon. It can be viewed at: <http://youtu.be/oSCX78-8-q0>

USB connector upgrade

Thanks to low cost and speed upgrades, the USB cable/connector has become the ubiquitous digital interface. Not only for computer equipment and peripherals, but also cameras, MP3 players and a host of other digital devices. That said, one of its main irritants has been the polarised plug – it will only fit in one way. Now, the familiar USB Type-A and Type-B ports are to be upgraded to Type-C. The aim is to make USB similar in operation to Apple's successful Lightning connector, which can be plugged in 'up or down' – there is no wrong way. The target is to have the design finalised by mid-2014.

When all (or most) devices move to Type-C ports, the number and variety of cables users need should fall.

Although there are no definitive illustrations of the new connector yet, it will have to be different enough from existing designs to be incompatible. This is of course unfortunate; however, the new connector is designed to 'scale for future USB bus performance' improvements. So, as USB 3.1 is supplanted by newer and faster versions of the standard, the new Type-C connector shouldn't have to change.



Artist rendering courtesy of Foxconn, the final design is subject to change

Versatile 10-Channel Remote Control Receiver

Works with a universal IR remote, either directly or via a UHF radio link

This 10-channel control system can be used with any universal IR remote control and can even be controlled via a UHF link so you don't have to worry about range or high light levels affecting infrared operation. It can be used to switch relays (and other devices) on and off, making it ideal for controlling motors, lights, solenoids, door catches and even robots.

LET'S CLEAR UP some confusion right at the start. Most infrared remote controls are intended to control various functions on just one appliance. For example, your TV remote enables you to control all its functions: channel change, volume, mute, picture and so on. By contrast, this *10-Channel Remote Control Receiver* enables you to use a single infrared remote control to control up to 10 separate devices, turning them on or off. Or you could use it to control more functions on less devices but still using up to 10 buttons on your universal remote.

Each channel in the receiver unit has an open-collector output that can drive an external relay, drive one or more LEDs or even directly switch low-power 12V equipment. Each output is initially set as momentary, meaning that the output is only active while you press the relevant button on the remote control.

Alternatively, one or more of the outputs can be set to change state (toggle) when you press the relevant button on the remote (ie, each output can be set independently). That means that an output that was previously ON turns OFF (and stays OFF) when its channel button is pressed, while an output that was previously OFF turns ON when its button is pressed.

Each individual toggle output can also be set up to be either ON or OFF when power is applied to the unit. For example, you can set the unit to switch on with Channel 1 OFF, Channel 2 ON, Channel 3 ON and so on. By contrast, the momentary outputs are always all off at power up and their initial switch-on state cannot be altered.

An Acknowledge LED indicates whenever a valid remote control signal is received.

Presentation

The *10-Channel Remote Control Receiver* comprises a small box that includes 10 LEDs to indicate the state of each channel. These are labelled from 0-9, corresponding to the 0-9 buttons on the remote control. Each channel has an output that is capable of sinking up to 500mA, so it is suitable for driving a 12V relay or similar load, as indicated above.

Power for the unit comes from a 12V DC plugpack supply. The current requirements depend on what sort of load each channel drives. For 12V relays, you could need up to 75mA for each relay, but the overall current requirements depend on whether the outputs are set for momentary or toggle operation.



Most universal remote controls can be used with the unit.

If momentary operation for all outputs is selected, there will be only one relay on at one time, and so a minimum of 85mA is required for the supply, ie, 75mA for the relay and about 10mA for the circuitry. For toggle operation on all outputs, all relays could be switched on at the same time and up to 750mA or so would be needed from the 12V plugpack.

The infrared (IR) remote control needs to be a universal type that can be programmed to operate Philips brand or similar appliances. The *10-Channel*



By JOHN CLARKE

Remote Control Receiver can operate using the code for either a TV, a CD player or one or two satellite receivers. Alternative choices are given so that when using the remote to operate the 10-Channel Remote Control Receiver, it does not affect any other appliances you may have.

For example, you may find that when the 10-Channel Remote Control Receiver is set to operate using the TV code, your TV also responds. In that case, it's simply a matter of using one of the alternative codes (ie, for a CD player or satellite receiver).

UHF radio link

As well as making provision for IR reception, the 10-Channel Remote Control Receiver can alternatively use an IR to 433MHz UHF Transceiver module. This means that it can be controlled from an IR remote via a UHF radio link – necessary if you don't have line-of-sight for infrared signals.

For this reason, we're also publishing the circuit details for an 'IR To UHF Transceiver' (see the following article). Push a button on your IR remote and the coded IR signal is picked up by this transceiver, converted to a 433MHz radio signal and transmitted to the 10-Channel Remote Control Receiver. Provided you have line-

of-sight between the remote and the transceiver, you're in business – the UHF radio link does the rest.

How it works

Refer now to Fig.1 for the circuit of the 10-Channel Remote Control Receiver. It's based on either an infrared receiver (IRD1) or a 433MHz receiver module (RX1), a PIC16F88 microcon-

troller (IC1) and a couple of ULN2003 Darlington arrays (IC2 and IC3). The micro decodes the remote control signal codes and drives the channel outputs accordingly.

The IR receiver module (IRD1) comprises an IR detector, an amplifier and a demodulator. The demodulator removes the 38kHz infrared modulation of the transmitted signal and the output at pin 1 then comprises the on and off levels that constitute the IR encoding. With no signal, the output remains high at about 5V.

The alternative UHF receiver (RX1) receives the UHF signal from the IR to 433MHz UHF Transceiver and outputs the encoded signal at its Data terminal. This signal is inverted compared to IRD1's output and so the SET jumper at pin 8 of IC1 is provided to allow either receiver to be selected. When open, the SET input is pulled high (ie, to 5V) via a pull-up resistor inside IC1 and this selects IR signal decoding.

Alternatively, when the SET jumper is installed, pin 8 of IC1 is pulled low (0V) and this instructs IC1 to decode a UHF signal.

Note that for UHF reception, RX1 is installed but IRD1 must be left off the PCB. Alternatively, for IR reception, you would normally just have IRD1 installed. However, in the latter case, you can actually also mount the UHF receiver on the PCB. That's because RX1's output is a high impedance and so would have negligible effect on IRD1's output.

Features and Specifications

Main Features


- Uses a commercial infrared hand-held transmitter
- 10 independent channels
- Momentary or toggle operation
- Selectable output state on power up for toggle selection
- 500mA open-collector sinking outputs for each channel
- Outputs suitable to directly drive 12V relays
- Infrared or UHF (433MHz) reception
- Acknowledge LED flashes while receiving transmission

Specifications

Power supply requirements.....12V at up to 50mA plus current drawn by each output; up to 760mA required for 10 relays if all powered at once

Infrared range 10m line-of-sight

UHF range30m in open space

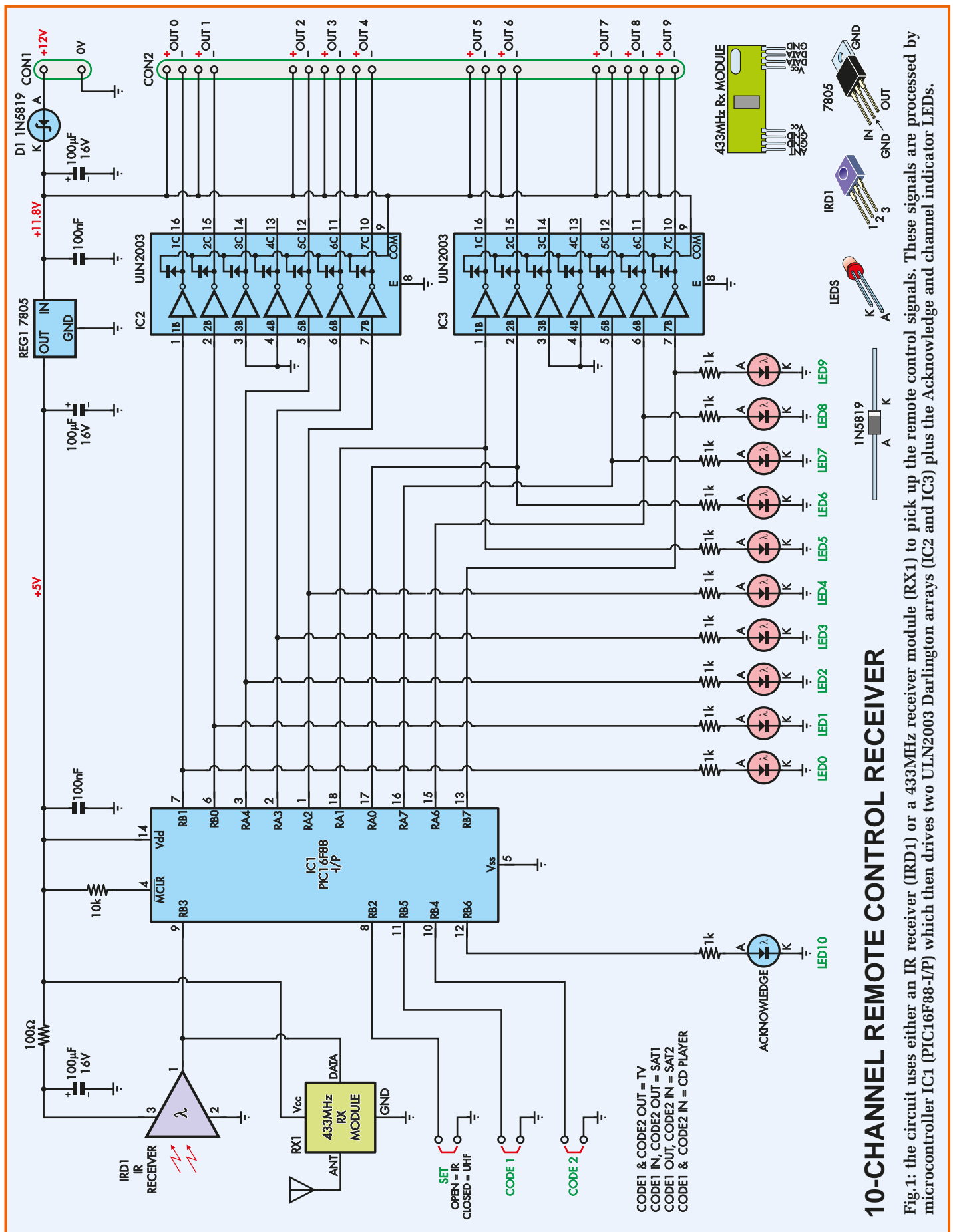

Parts List

- 1 PCB, available from the *EPE PCB Service*, code 15106131, 123 × 61mm
- 1 UB3 box, 130 × 68 × 44mm
- 1 panel label, 102 × 61mm
- 11 2-way PCB-mount screw terminals, 5.04mm pitch
- 1 DIP18 IC socket
- 1 M3 × 10mm screw
- 1 M3 nut
- 3 2-way pin headers with 2.54mm pin spacing
- 3 pin header jumper shunts
- 1 170mm length of hook-up wire (UHF version only)
- 1 2.1mm bulkhead-mount DC socket

Semiconductors

- 1 PIC16F88-I/P microcontroller programmed with 1510613A. hex (IC1)
- 2 ULN2003 Darlington arrays (IC2, IC3)
- 1 infrared receiver (TOSOP4136 or similar) (IRD1) or 1 433MHz receiver (Jaycar ZW-3102, Altronics Z 6905A) (RX1)
- 1 7805 5V regulator (REG1)
- 1 1N5819 1A Schottky diode (D1)
- 10 3mm red high-brightness LEDs (LED0-LED9)
- 1 3mm blue high-brightness LED (LED10)

Capacitors

- 3 100µF 16V PC electrolytic
- 2 100nF MKT polyester

Resistors (0.25W, 1%)

- 1 10kΩ
- 1 100Ω
- 11 1kΩ

Miscellaneous

- Cable glands, hook-up wire

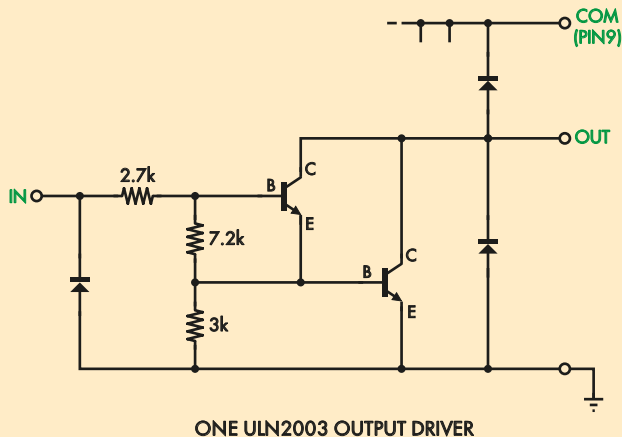


Fig.2: the internal Darlington transistor arrangement for the ULN2003 ICs. There are seven such output driver stages inside each device.

Code links

The Code 1 and Code 2 jumpers, on pins 10 and 11 of IC1 respectively, select the encoding mode; ie, either TV, satellite (SAT1 or SAT2) or CD player. Both the circuit and Table 3 towards the end of the article show the jumper linking options to select each code (eg, leave both jumpers out to select TV encoding).

IC1's RB6 output at pin 12 drives the Acknowledge LED (LED 10). This lights whenever a valid remote control signal, either IR or UHF, is being received.

IC1 decodes the remote control signals and provides the 10 channel output signals to drive the Darlington arrays (IC2 and IC3). For example, the channel 0 signal is at RB1 (pin 7) and this drives pin 1 of IC2. Similarly, the channel 1 signal appears at the RB0 output and this drives pin 2 of IC3, and so on for the remaining eight outputs. Note that output channels 0-4 drive IC2, while outputs 5-9 drive IC3.

IC2 and IC3 each include seven separate Darlington transistors, with five Darlings used in each package to make up the 10 channels. Fig.2 shows the internal Darlington transistor arrangement for each driver.

As can be seen, the first NPN transistor is driven via a 2.7kΩ resistor, while its emitter drives the second NPN transistor's base. The collectors are commoned to provide an output that can sink up to 500mA when the input is driven by 5V (ie, a Darlington arrangement).

In addition, a diode clamp is connected between each output and the common pin of the IC. This ensures that the transistors are protected from over-voltage when driving an inductive load.

The common pin for the diodes connects to the 11.8V supply. This 11.8V supply is also connected to each of the channel outputs on CON2 (a 20-way screw-terminal block), to provide the positive output terminals. The collector outputs from the Darlington arrays connect to the negative terminals, so that they sink the load current when active.

That way, a relay coil can be directly connected to each pair of output terminals; ie, between the +11.8V supply and the individual collector outputs.

5V regulator

Power for the circuit is derived from an external 12V supply (eg, a plugpack), with Schottky diode D1 providing reverse polarity protection. The resulting 11.8V rail is then filtered using 100µF and 100nF capacitors and fed to 3-terminal regulator REG1. REG1 then provides a 5V supply rail for IC1, IRD1 and RX1 (the 433MHz receiver module).

Note that the supply rail for IRD1 is decoupled via a 100Ω resistor and 100µF capacitor. This minimises supply variations and glitches from being decoded as control signals.

In addition, the 11.8V rail at the output of D1 is fed to the positive terminals of CON2, as described above.

RC5 codes

The Philips RC5 code for infrared transmission is used by many manufacturers, including Philips, Marantz, Mission, Grundig and Loewe. The code comprises two start bits and one toggle bit that alternates between high and low on successive same key presses. A five-bit address is then sent, followed by six command bits.

The bits are sent using bi-phase encoding, whereby a high-to-low transition represents a low bit and a

low-to-high transition a high bit. The data is transmitted at a 1.778ms rate, with the whole code taking 24.889ms to send. The next code starts after 113.778ms.

As stated above, the RC5 remote control signal, either from IRD1 or RX1, is decoded by IC1.

Building it

Take a look now at Fig.3 for the assembly details of the 10-Channel Remote Control Receiver. It's built on a PCB available from the *EPE PCB Service*, coded 15106131 (123 × 61mm) and this clips neatly into a plastic utility case measuring 130 × 68 × 44mm.


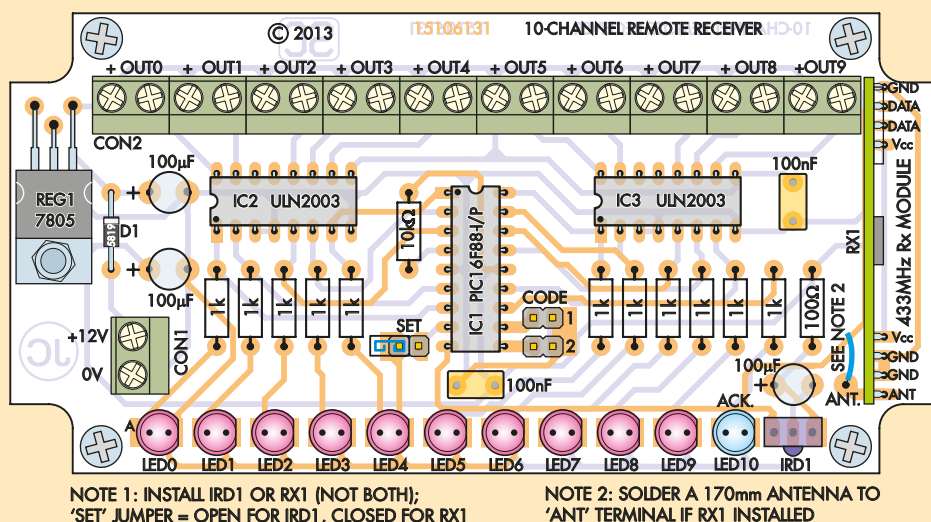


Fig.3: follow this layout diagram to install the parts on the PCB. Note that either IRD1 or RX1 is installed – but not both (see text). You will need to solder a 170mm-long antenna to the ‘ANT’ terminal if RX1 (the UHF module) is used.

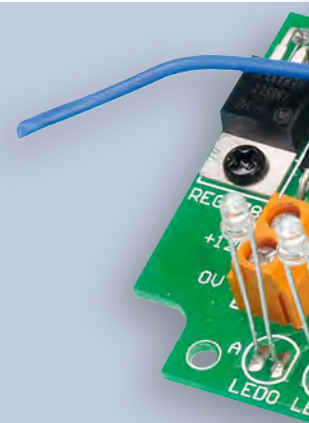

Right: the prototype PCB, ready for installation in the case. Note how the LEDs are all stood off the board (on 25mm lead lengths) so that they later protrude through the holes in the case lid.

Install the resistors and diode D1 first. Table 1 shows the resistor colour codes, but you should also check each one using a digital multimeter before soldering it into place. Make sure the diode is installed with the correct polarity, with the banded end oriented as shown on the layout diagram.

Once these parts are in, REG1 can be fitted. It's mounted horizontally on the PCB, with its leads bent down through 90° so that they go through their respective holes. Secure its metal tab to the PCB using an M3 × 10mm machine screw and nut before soldering its leads (note: don't solder the leads first, otherwise the PCB tracks could fracture as the nut is tightened).

Follow with the three 2-way pin headers for the SET, Code 1 and Code 2 jumpers, then install an 18-pin IC socket for IC1 (be sure to position the notched end as shown). You can also install sockets for IC2 and IC3 if you wish, but these are optional. If you don't wish to use sockets, these two devices can now be directly soldered to the PCB, with their notched ends facing towards REG1.

Do not insert IC1 into its socket yet – that step comes later, after you've checked the 5V supply rail.

The capacitors are next on the list. The two 100nF capacitors can go in either way round, but be sure to install the three 100μF electrolytics with the correct polarity.

The 20-way screw terminal block (CON2) can now be installed. It's made up by dovetailing together 10 2-way blocks, and must be fitted with the wire entry holes facing outwards. Push it all the way down so that it sits flush against the PCB before soldering the terminals. Once it's in, the 2-way terminal block (CON1) can be fitted at lower left.

Installing the LEDs

Now for the LEDs. These must be installed so that the top of each LED is exactly 30mm above the PCB surface, which means mounting them with 25mm lead lengths.

The easiest way to do this is to use a 25mm-wide strip of cardboard as a spacer. It's just a matter of pushing each LED down onto this strip (ie, leads on either side) before soldering it to the PCB. Be sure to orient each LED correctly, with the longer anode leads to the left.

Our prototype used red LEDs for LEDs0-9 and a blue LED for LED10

(Acknowledge) but any colour can be used.

IR/UHF receiver module

The PCB assembly can now be completed by installing either the infrared receiver (IRD1) or the UHF receiver (RX1) and configuring the SET jumper.


Install IRD1 and leave the SET jumper out if you want to use infrared signals to control the 10-channel receiver. It goes in with its lens facing the adjacent edge of the PCB and is installed with its leads left at full length so it can later be pushed into position to align with its case hole.

Alternatively, install RX1 and fit the SET jumper if you want to control the receiver using a 433MHz UHF radio link. RX1 must be oriented with its component side to the right. **In addition, a 170mm-length of hook-up wire must be soldered to the antenna (ANT) terminal to pick up the 433MHz signal.**

Don't also install IRD1 if you intend using the 433MHz transceiver (RX1), as this would upset the latter's operation. Conversely, you can fit both IRD1 and RX1 if you intend using IRD1 to

Table 1: Resistor Colour Codes

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
□	1	10kΩ	brown black orange brown	brown black black red brown
□	11	1kΩ	brown black red brown	brown black black brown brown
□	1	100Ω	brown black brown brown	brown black black black brown

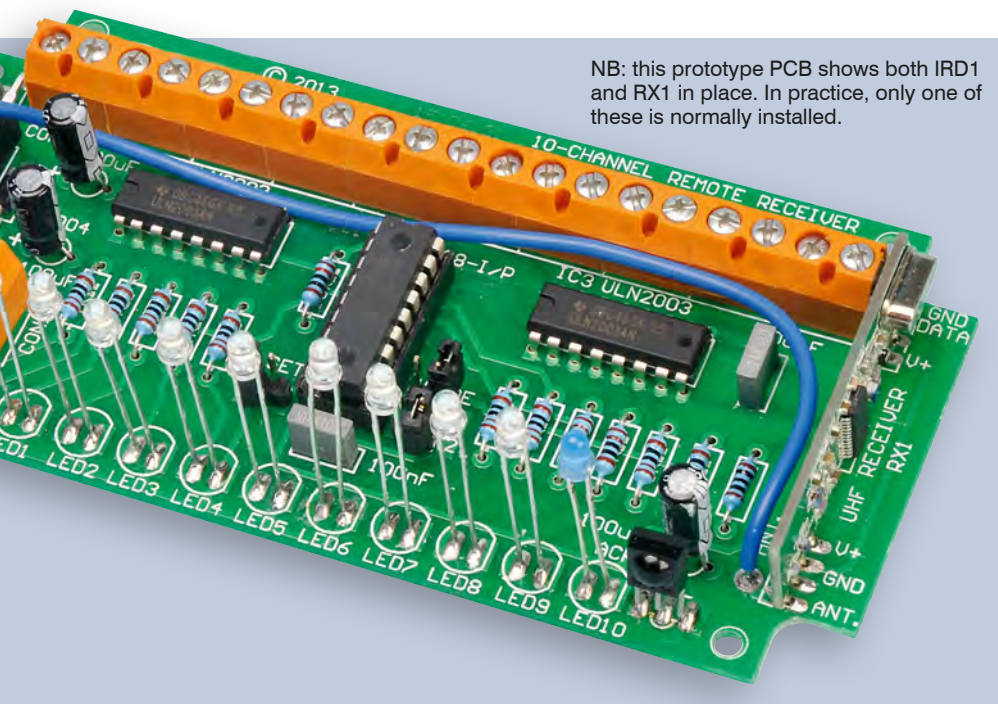

pick up the remote control codes, as explained previously. You might want to do that if you intend swapping over and using RX1 at some later date (in which case you would then have to remove IRD1).

Final assembly

Before installing the PCB in the case, you will need to drill holes in the rear of the base for the DC power socket, plus holes to accept two cable glands. The cable glands route and secure the

various leads from the output terminals on CON2.

The DC socket hole should be drilled in one end of the case, ie, near CON1 on the PCB. It should be centred horizontally and positioned about 12mm down from the top of the base. Use a small pilot drill to drill this hole first, then carefully enlarge it to size with a tapered reamer until the socket is a neat fit.

The two cable gland hole centres are exactly 14mm down from the top of

the base and must be centred between the two sets of vertical rib pairs. Drill these holes using a pilot drill initially, then enlarge them to 12mm using a tapered reamer.

In addition, a 4mm hole must be drilled in the front of the base in-line with IRD1's lens. This hole is positioned 22mm in from the adjacent side (as measured at the top of the base) and 11mm down.

A row of 11 3mm holes is also required along one edge of the lid to accept the LEDs. These holes can be drilled using the front panel artwork as a template. This artwork can be downloaded from the *EPE* website and temporarily attached to the lid using tape.

After drilling, clean up the holes using an oversize drill, then print out another copy of the artwork onto photo paper and attach it to the lid using silicone sealant (or some other suitable adhesive). Once the silicone has cured, the holes for the LEDs can either be punched out or cut out using a sharp hobby knife.

The assembly can now be completed by clipping the PCB into place, fitting the cable glands and the DC socket and running the positive and negative supply leads between the DC socket and CON1. **It's also necessary to bend IRD1's leads so that its lens is aligned with its hole in the side of the case.**



The PCB clips into the integral slots in the sides of the UB3 case. You need to drill holes in the rear edge for two cable glands, a hole in the front edge for the IR receiver (if used) and a hole in the lefthand end for the DC socket. Eleven holes are also required in the lid for the LEDs.

Constructional Project


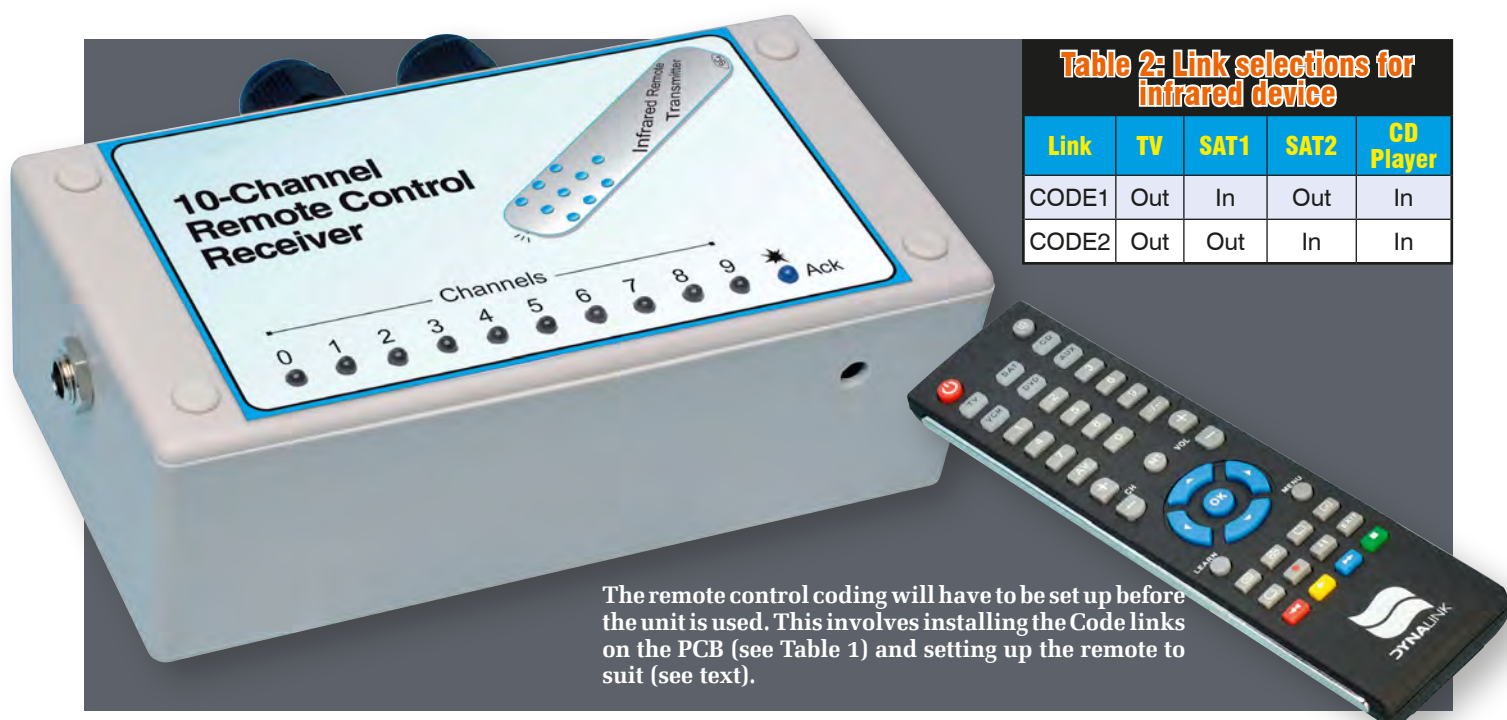


Table 2: Link selections for infrared device

Link	TV	SAT1	SAT2	CD Player
CODE1	Out	In	Out	In
CODE2	Out	Out	In	In

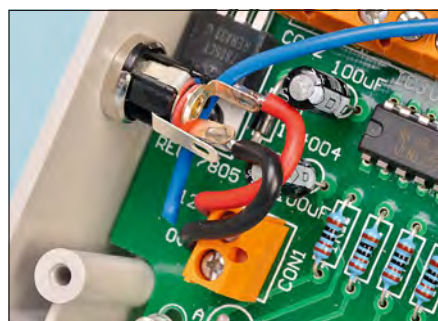The remote control coding will have to be set up before the unit is used. This involves installing the Code links on the PCB (see Table 1) and setting up the remote to suit (see text).



This close-up shows how the DC socket is wired to screw-terminal block CON1

Initial checks

Now for the smoke test. Check the assembly carefully, then connect a 12V DC plugpack, switch on and measure the voltage between pins 5 and 14 of IC1's socket. You should get a reading of between 4.85V and 5.15V. If this is incorrect, switch off immediately and check the supply polarity, the orientation of diode D1 and the 7805 regulator.

If the reading is correct, switch off and install IC1 in its socket. Make sure that this device is oriented correctly and that all its pins go into the socket. IC2 and IC3 should also now be installed if you are also using sockets for these devices.

Remote control coding

Before testing, you will need to set up the remote control coding. The first step is to decide whether you will be using a TV, satellite or CD player code on the remote, then configuring the jumpers on the 10-Channel Remote Control Receiver accordingly – see Table 1.

Omitting both the CODE1 and CODE2 jumpers selects the TV code; installing the CODE1 jumper only selects SAT1; installing the CODE2 jumper only selects SAT2; and installing both jumpers selects the CD player code.

That done, the correct code must now be programmed into the remote.

This involves selecting TV, SAT1, SAT2 or CD on the remote (to agree with the 10-Channel Receiver) and then programming in a 3-digit or 4-digit number for a Philips device.

Most universal remote controls can be used.

In the case of other universal remotes, it's just a matter of testing the various codes until you find one that works. There are usually no more than 15 codes (and usually a lot less) listed for each Philips device, so it shouldn't take long to find the correct one.

Note that some remotes may only work in one mode (eg, TV but not SAT). For example, if you have a Digitor 4-in-1 remote, you can use 5005 for TV1 but there's no suitable code for SAT. Similarly, if you have an AIFA RA7, you can use 026 for TV1, but again, there's no suitable code for SAT.

If you are using infrared reception (ie, IRD1 installed), the receiver

Darlington saturation voltage In the ULN2003 devices

According to the ULN2003 data sheet, the output saturation voltage of each Darlington output stage is typically 1.3V @ 350mA (but can be as high as 1.6V). And it's typically 1.1V @ 200mA and 0.9V @ 100mA.

This means that with a supply of exactly 12V and a load drawing 350mA, the load will typically see just 12V – 1.3V – 0.2V (the Schottky diode voltage) =

10.5V. And it could be less than that depending on how much current other channels are drawing, the temperature and so on.

As a result, the Darlington configuration results in a voltage across the load that's substantially below the 12V supply voltage, and while most 12V relays will happily run off 10.5V, other loads such as 12V LEDs may not. In fact, 12V LED

lamps and 12V LED strips would probably be quite dim if switched using this unit because of the Darlington saturation voltage.

This can be slightly improved if the positive power supply terminal of each load is connected directly to the 12V supply, ie, bypassing D1. And, in fact, this will be necessary if the load total exceeds 1A, as D1 is only rated as 1A DC.

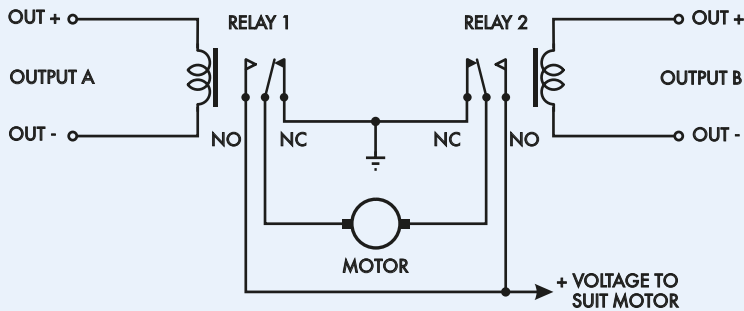


Fig.4(a): using two outputs to drive a motor in forward and reverse:
 (1) Both outputs set for momentary operation. In this case, pressing (and holding) the button for Output 'A' activates Relay 1 and causes the motor to rotate one way, while pressing the button for output 'B' activates Relay 2 and causes the motor to rotate the other way.
 (2) Both outputs set for toggle operation. If both outputs are off at power-up, the motor will be stopped until one of the outputs is toggled (its direction will depend on which output is turned on). Alternatively, if one output is high and the other low at power-up, then the motor will run as soon as power is applied. The motor can be stopped and reversed by toggling the outputs.
 (3) One output momentary and the other toggle. If the toggle output is high at power-up, the motor will immediately run. It can be stopped temporarily by pressing the button for the momentary output, or stopped permanently by pressing the button for the toggle output.

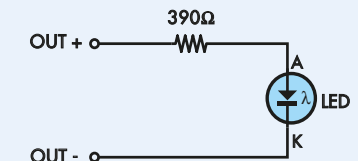


Fig.4(b): driving an LED output

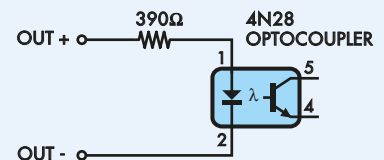


Fig.4(c): driving an optocoupler

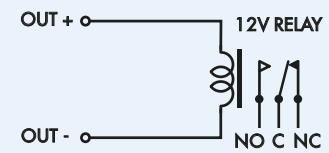


Fig.4(d): driving a 12V relay

If toggle operation (1) is selected, then you need to enter an additional number – either '0' or '1' – to select the state of the output at power up. A '0' sets the output to off at power up, while '1' will set the output to on. Once you have entered this number, the Acknowledge LED will extinguish and the settings will be stored.

This procedure must then be repeated for any additional channels that require changing. Note that the Channel Down (CH-) button can be pressed before all the numbers are entered to exit the channel programming. There will be no change to the setting if this is done. In addition, the numbers for each setting must be entered within 12 seconds, otherwise the program in the PIC micro will exit without making any changes.

Finally, Figs.4(a)-4(d) show how to use the outputs to drive various devices, including a 12V DC motor in forward or reverse. Note that while Fig.4(b) shows how to drive a single LED, it's also possible to drive series or parallel LEDs – just adjust the value of the current-limiting resistor accordingly.

Reproduced by arrangement
with SILICON CHIP
magazine 2014.
www.siliconchip.com.au

Table 3: Setting the outputs for momentary or toggle operation

Step 1	Step 2	Step 3 (toggle operation only)
Press Channel Up, then press channel number to set	Press '0' for momentary operation or '1' for toggle	Press '0' for output off at power up, '1' for output on

should now respond to the channel number buttons on the remote. When you press a button, the Acknowledge (ACK) LED should flash (to indicate that code is being received) and the indicator LED for that channel should light.

As mentioned, the 10-Channel Remote Control Receiver is initially set so that its outputs are momentary in operation. That means that a channel indicator LED should only light while its corresponding button on the remote is held down and should go out as soon as the button is released.

If it doesn't operate, check that IRD's lens is aligned with its hole in the case. Check also that the code programmed into the universal remote is correct and check that the SET input is open, ie, no jumper installed.

Note that the jumpers on the SET, CODE1 and CODE2 headers are only checked by the microcontroller at power up. So changing these jumpers with the power on will have no effect on the operation until the power is switched off and then on again.

Momentary or toggle

You can easily change one or more outputs to toggle operation to suit your particular application. In this operation mode, an output changes state when its remote button is pressed and remains in that state until the button is pressed again.

The output configuration is done using the hand-held remote. First, press the Channel Up (CH+) button and check that the Acknowledge LED on the receiver stays lit. Then press the number for the channel you wish to program. After that, pressing '1' will select toggle operation for that channel, while pressing '0' will select momentary. If momentary operation is selected, the Acknowledge LED will extinguish and the setting will immediately be stored.

Extending the range of the remote control


Want to extend the remote control range or want it to operate without line of sight? You can with the IR To 433MHz UHF Transceiver described on the following pages.



IR to 433MHz UHF Transceiver

Mates With 10-Channel Remote Control Receiver

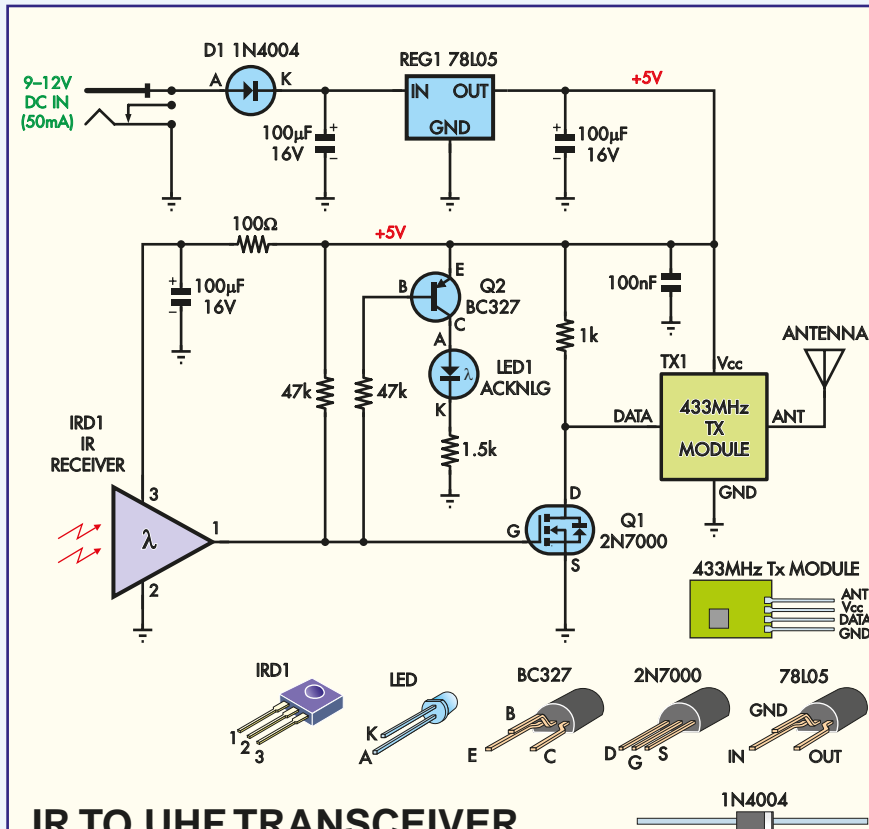Don't have line-of-sight between your infrared remote and the *10-Channel Remote Control Receiver*? Or do you simply want more range or want it to work outdoors? This *IR To 433MHz UHF Transceiver* will solve the problem.



IR TO UHF TRANSCEIVER

Fig.5: the circuit of the IR To UHF Transceiver. IRD1 picks up the infrared signal and its output drives the Data input of TX1 (the 433MHz transmitter module) via FET Q1. Transistor Q2 drives the Acknowledge LED (LED1).

THE WAY IN which this device works is straightforward: it picks up the coded signal from your IR remote and converts it to a 433MHz UHF radio signal. This is then picked up by the 433MHz receiver in the *10-Channel Remote Control Receiver*, which decodes the signal

and switches its outputs accordingly. In effect, all it does is convert the remote's infrared signals into a radio link, resulting in longer range and no line-of-sight problems. If you want to control the *10-Channel Remote Control Receiver* from another room or outdoors, this is the way to do it.

Specifications

Power supply: 9-12V DC, 50mA
Infrared range: 10m line-of-sight
UHF range: 30m in open space

The transceiver is quite compact and operates from a 9-12V DC supply. In operation, it must be located within range of the infrared remote so that its IR receiver can pick up the remote's signals.

An acknowledge LED on the front panel lights when a valid infrared signal is being received and re-transmitted as a UHF signal.

How it works

Fig.5 shows the circuit details of the *IR To 433MHz UHF Transceiver*. It's based on an infrared receiver (IRD1) and a 433MHz transmitter module (TX1) and not much else.

IRD1's pin 1 output is normally at 5V when no infrared signal is being received. This 5V 'high' is inverted by Q1, an N-channel enhancement-mode FET. It turns on when its gate is high and so the Data input of the UHF transmitter is normally low (ie, at 0V). This low voltage keeps the UHF transmitter off.

When an infrared signal is received from the remote, pin 1 of IRD1 pulses Q1 on and off. Each time FET Q1 turns off, a 1kΩ pull-up resistor at its drain pulls the Data input of TX1 to 5V and the UHF transmitter sends a signal.

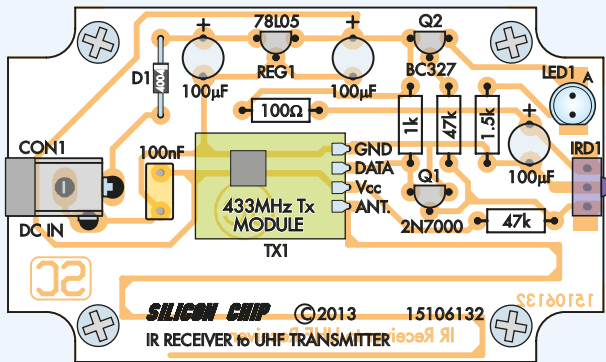


Fig.6: install the parts on the PCB as shown on this layout diagram. LED1 must be mounted with 12mm lead lengths, while the infrared receiver (IRD1) goes in with 4mm lead lengths.

At the same time, each time pin 1 of IRD1 goes low, transistor Q2 turns on and drives the Acknowledge LED (LED1) via a 1.5kΩ current-limiting resistor. So this LED flickers upon receipt of infrared transmission.

Power for the circuit is derived from a 12V DC 100mA plugpack supply, with diode D1 providing reverse-polarity protection. The nominal 11.4V supply at D1's cathode is then fed to 3-terminal regulator REG1, which provides a 5V supply for IRD1 and TX1 (the 433MHz transmitter).

Assembly

The *IR To 433MHz UHF Transceiver* is assembled on a PCB coded 15106132 and measuring 79 × 47mm. This is housed in a UB5 plastic utility box (83 × 54 × 31mm).

Fig.6 shows the parts layout on the PCB. Install the resistors and diode D1 first, taking care to ensure that the latter is correctly oriented. REG1, Q1 and Q2 can then be mounted, but be careful not to get these mixed up.

Once these parts are in, install the capacitors but watch the polarity of the 100µF electrolytics. In addition, the tops of the electrolytics must be no more than 15mm above the PCB (so that they will later clear the case lid).

LED1 is mounted with the top of its lens 17mm above the PCB surface. That's done by pushing it down on a 12mm cardboard spacer inserted between its leads before soldering it to the PCB. Make sure the LED is oriented correctly, with its anode (longer) lead going to the pad marked 'A'.

The infrared receiver (RX1) can go in next. It's mounted on 4mm

lead lengths so that its top is 10mm above the PCB.

The PCB assembly can now be completed by installing the UHF transmitter (TX1). This module is mounted horizontally and so its four mounting pins will need to be bent down at right angles for insertion into its PCB pads. The antenna for this transmitter is a part of the track pattern on the PCB, so there's no need to fit a separate antenna wire.


Final assembly

The PCB simply clips into the integral ribs of the UB5 case. **Before doing this, you have to drill a hole at each end to give access to the IR receiver and the DC socket.** These holes are both 6mm in diameter and should be centred 7mm down from the top of the base (and centred horizontally).

A 3mm hole must also be drilled in the box lid for the Acknowledge LED. The front panel label can be used as a template to determine the position of this hole. You can download this panel (in PDF format) from the *EPE* website.

Once you have this file, print it out, attach it to the case lid and drill the LED hole to 3mm. A second copy of the artwork can then be printed onto photo paper and affixed to the lid using silicone or some other suitable adhesive. The hole for the LED can either be cut out or punched out with the back end of a 3mm drill bit.

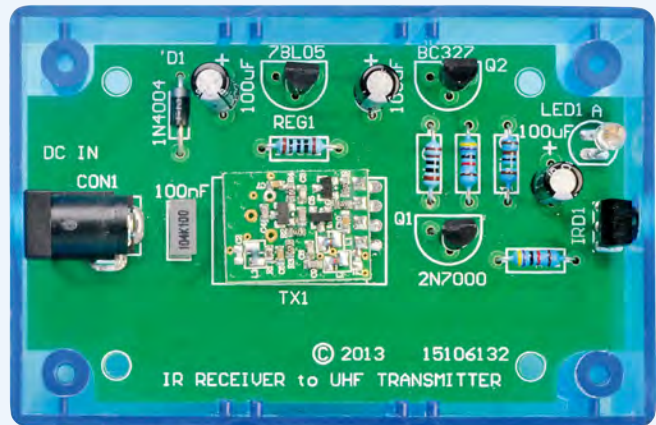In use, the *IR To 433MHz UHF Transceiver* should be placed no closer than 1m to the *10-Channel Remote Control Receiver* to prevent possible signal overload. In practice



The PCB clips neatly into the UB5 plastic case. Drill holes at each end for the DC socket and IRD1.

Parts List

- 1 PCB, available from the *EPE PCB Service*, code 15106132, 79 × 47mm
- 1 front panel label, 78 × 49mm
- 1 433MHz transmitter (TX1), (Jaycar ZW-3100, Altronics Z 6900)
- 1 UB5 utility case, 83 × 54 × 31mm
- 1 PCB-mount DC socket

Semiconductors

- 1 infrared receiver, TOSOP4136 or similar (RX1)
- 1 2N7000 N-channel enhancement-mode FET (Q1)
- 1 BC327 PNP transistor (Q2)
- 1 78L05 regulator (REG1)
- 1 1N4004 1A diode (D1)
- 1 3mm blue high-brightness LED (LED1)

Capacitors

- 3 100µF 16V PC electrolytic
- 1 100nF MKT polyester

Resistors (0.25W, 1%)

- 2 47kΩ 1 1kΩ
- 1 1.5kΩ 1 100Ω

of course, the two are likely to be much further away than that and you should get reliable operation at distances up to 30 metres in open space.

What's coming

Finally, we plan to publish a version of this *IR To 433MHz UHF Transceiver* that fits inside an IR remote control. We also plan to publish a companion *UHF To IR Receiver* unit so that the two can be used as an IR range extender with any equipment.

Into model railways?
Then you'll want to build the . . .



Li'l Pulser Model Train Controller

By JOHN CLARKE

This project started out as a simple revision to earlier train controllers. But this new controller has a lot of extra features and it can deliver considerably more current.

UNLESS YOU ARE already using a previously published model train controller, this little feature-packed controller is likely to be better than any controller you have used. This is particularly true if you are using a commercially-made low-cost rheostat or series transistor train controller.

Simple train controllers have plenty of shortcomings. To get the loco started, you have to wind the speed control way past the setting at which you would want it to run. Then the loco suddenly takes off like a startled

rabbit. Once running, with reduced throttle setting, the loco then slows down whenever there is the slightest incline.

So what makes *Li'l Pulser* so much better? Well, firstly, it will control the loco at the speed you want, with smooth starts and not too much speed reduction on hills. In model railway jargon, 'pulse power' is what makes this little train controller such a good performer.

Don't let the small case fool you. This little train controller has just

about all the operational features of the best designs (such as the *Railpower IV* from *EPE* October and November 2010). And there is no heavy mains transformer or mains wiring involved because you can use an original train controller supply, a 12V lead-acid battery charger or any 15-19V switch-mode laptop PC power supply rated at up to 8A.

Pulse power

As noted earlier, our *Li'l Pulser* applies pulse power to the railway track. This



The completed unit, shown here actual size, is quite compact but has lots of features and can deliver output currents up to 8A. Power comes from an external 15-19V DC supply rated up to 8A (eg, a laptop PC power supply).

involves applying 17V voltage pulses (typically) to the track, even at low throttle settings. These voltage pulses are much more effective at starting and running a loco, particularly at low settings.

The pulses overcome track resistance and motor and gearbox stiction, thus providing a smooth-running loco motor. At low speeds, the 17V pulses are very short, so that the average voltage is low and the motor runs at a slow speed. For faster operation, the pulses are wider, thus applying a higher average voltage to the motor.

But pulse power is not the only feature of this latest *Li'l Pulser* model train controller. It also includes monitoring of the motor back-EMF to provide very good speed regulation. Without this back-EMF control, the model locos would slow down unrealistically with any slight incline.

Naturally, *Li'l Pulser* has reverse polarity and overload protection (essential features for all but the simplest model train controller), together with an audible alarm which beeps briefly for momentary track shorts, but which sounds for longer for more severe overloads.

New features

Previous designs had useful but basic features: a speed control potentiometer, LEDs to indicate power on, reverse and track voltage, and a switch for forward/reverse operation.

By contrast, *Li'l Pulser* has several added features that vastly improve the realism of operation, including inertia (sometimes called 'momentum'), braking and reverse lockout, plus minimum and maximum speed settings.

The most useful added feature is reverse lockout. This makes it impossible

Main Features

- Pulse power for smooth running
- Excellent low-speed control
- Speed regulation
- Speed control pot
- Inertia and braking simulation
- Minimum and maximum speed adjustments
- Adjustable inertia and braking rates
- Inertia on and off selection
- Power on indication
- Track voltage LED indication
- Reverse indicator
- Over-current/short-circuit alarm
- Compact size
- Maximum current: 8A
- Power supply: 15-19V DC

Li'l Pulser Parts List

1 double-sided PCB, available from the <i>EPE PCB Service</i> , code 09107134, 129.5 × 100.5mm	7 PC stakes
1 front panel PCB, available from the <i>EPE PCB Service</i> , code 09107132, 132 × 30mm	1 200mm length of 8A hook-up wire
1 rear panel PCB, available from the <i>EPE PCB Service</i> , code 09107133, 132 × 30mm OR	
1 aluminium rear panel, 134 × 30 × 1mm (see text)	Semiconductors
1 plastic instrument case, 140 × 110 × 35mm	1 LM358 dual op amp (IC1)
1 piezo buzzer	1 LM324 quad op amp (IC2)
1 16mm 10kΩ linear PCB-mount potentiometer (VR1)	1 LM393 dual comparator (IC3)
1 1MΩ miniature horizontal-mount trimpot (VR4)	1 4013 dual D-flipflop (IC4)
1 250kΩ miniature horizontal-mount trimpot (VR5)	2 IRF1405 55V 169A MOSFETs (Q1,Q2)
3 10kΩ miniature horizontal-mount trimpots (VR2,VR3,VR6)	3 BC337 NPN transistors (Q3,Q5,Q6)
1 1kΩ miniature horizontal-mount trimpot (VR7)	1 BC327 PNP transistor (Q4)
2 nuts and washer for VR1	1 7812 3-terminal regulator (REG1)
1 19mm knob to suit potentiometer	1 15V 1W Zener diode (ZD1)
1 8A DPDT PCB mount relay (RELAY1)	1 8.2V 1W Zener diode (ZD2)
4 SPDT PCB mount toggle switches (S1-S4)	1 FR607 6A diode (D6)
1 2.5mm PC mount DC socket	2 1N4004 1A diodes (D1,D5)
1 black binding post	4 1N4148 diodes (D2-D4, D7)
1 red binding post	1 3mm 2-lead bi-colour LED (LED1)
2 white binding posts	1 3mm red LED (LED2)
4 6.3mm 45° chassis-mount spade terminals	1 3mm green LED (LED3)
1 8A M205 fuse (F1)	Capacitors
2 M205 fuse clips	3 2200μF 25V low-ESR electrolytic (22mm high or less; eg, element14 1800659)
2 TO-220 insulating bushes	4 100μF 16V PC electrolytic
2 TO-220 silicone insulating washers	1 47μF 16V low-leakage PC electrolytic or tantalum
4 M3 × 5mm screws	2 1μF 16V PC electrolytic
2 M3 × 10mm screws	1 1μF monolithic ceramic (MMC)
2 M3 nuts	1 220nF MKT polyester
	2 100nF MKT polyester
	1 22nF MKT polyester
	2 10nF MKT polyester
	Resistors (1%, 0.25W)
	1 1MΩ
	1 470kΩ
	2 220kΩ
	6 100kΩ
	2 47kΩ
	9 10kΩ
	5 4.7kΩ
	3 2.2kΩ
	2 1kΩ
	2 470Ω
	1 100Ω
	1 10Ω
	2 0.1Ω 5W 5%

a front panel switch to disable inertia when you don't need it.

Locos don't buzz when stopped

In case you are wondering, the *Li'l Pulser* does not cause locos to buzz when they are stopped. All model locomotives require a few volts DC before they will start moving and before that, pulse power will cause them to buzz. However, the minimum speed setting in the *Li'l Pulser* can be set to switch off the pulses whenever the loco is stopped.

The *Li'l Pulser* can deliver up to 8A DC. This means that it can easily handle trains with double-headed locos, even if they have smoke generators, sound and lighting. This is mainly due to vastly better MOSFETs than those used in earlier designs.

Despite these features, the controller is mounted in a compact plastic case, measuring just 140mm wide, 35mm high and 110mm deep. We have packed all the circuit features onto a double-sided PCB with plated-through holes.

On the front panel, there are toggle switches for power, inertia, braking and forward/reverse switching. There is one knob for the throttle control and the three LEDs. The track LED is bi-coloured: green for forward and red for reverse. The reverse LED is red, to give an indication when a train is set to go backwards.

There are four binding post terminals on the rear panel, two for the input power and two for the leads to the track. A DC socket is also included for power, but be aware that these DC sockets are not rated for much above about 4A. So use the binding posts for higher current operation.

Pulse-width modulation

Before having a look at the full circuit of the *Li'l Pulser*, we should describe how the circuit generates the varying width pulses which drive the loco motor. To do that, we have taken the core of the circuit, as shown in Fig.1. It basically consists of a ramp (triangle) wave generator based on IC1a and a comparator based on IC3b. The IC numbers correspond to the same parts on the main circuit shown in Fig.3.

IC1a is one half of an LM358 dual op amp and is configured to work as an oscillator running at about 160Hz. It works by charging and discharging a 22nF capacitor at its inverting input. The result is a triangle (ramp) waveform

to throw the loco into reverse while it is moving in the forward direction. This is highly desirable for two reasons. First, it is more realistic and second it prevents derailments. Reverse lockout means that even if you inadvertently switch to change the direction of the train while it is moving, the controller won't do anything until the train has come almost to a full stop.

Inertia and braking add realism to loco operation. While you can simulate the slow increase in speed during starting and the slow decrease in speed

during braking by careful adjustment of the speed control, the inertia and braking functions do it automatically and consistently.

It means that the throttle can be pre-set and the starting and stopping done entirely using the inertia and braking functions. The brake typically slows down the loco at a faster rate than the start-up inertia rate. There are trimpots on the PCB to set these rates.

But while simulated inertia is good most of the time, it can be a problem for shunting operations. So we've added

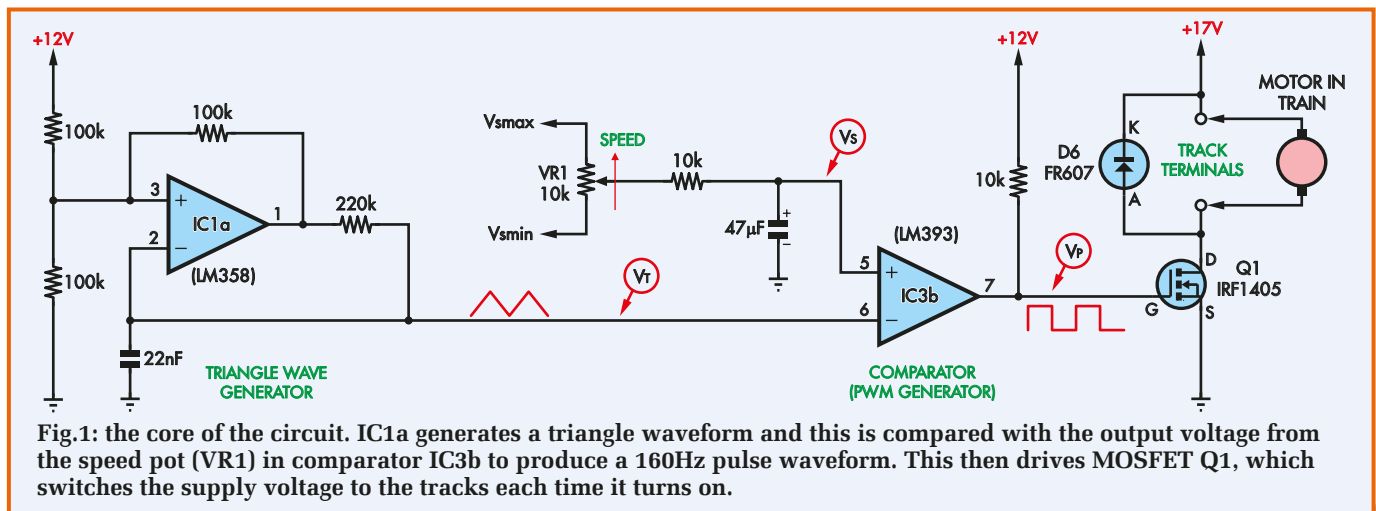


Fig.1: the core of the circuit. IC1a generates a triangle waveform and this is compared with the output voltage from the speed pot (VR1) in comparator IC3b to produce a 160Hz pulse waveform. This then drives MOSFET Q1, which switches the supply voltage to the tracks each time it turns on.

at pin 2 and a square wave at its output, pin 1. The triangle waveform is fed to the inverting input (pin 6) of IC1b, one half of an LM393 dual comparator.

The comparator compares the triangle wave at pin 6 with the DC voltage from VR1, the speed control potentiometer. This is depicted in the waveforms shown in Fig.2, with the DC voltage from VR1 shown as the horizontal line V_S . Whenever the triangle voltage V_T is below V_S , the output V_P at IC3b's pin 7 will go high. Similarly, when V_T is above V_S , V_P will go low.

The result is a 160Hz pulse waveform which drives the gate of MOSFET Q1, turning it on each time V_P is high. Fig.2(a) shows the result when the speed pot VR1 is set for a high speed, while Fig.2(b) shows the result for a low-speed setting.

These waveforms are confirmed by the scope shots accompanying this article.

Circuit description

Now let's have a look at the full circuit shown in Fig.3. It uses four low-cost ICs, two power MOSFETs and a relay for forward/reverse switching. IC1a is on the lefthand side of the diagram, while IC3b and MOSFET Q1 are on the righthand side. Most of the rest of the circuitry is there to add the various operating features such as braking, inertia and overload protection.

So let's start at the top lefthand corner of the circuit, which shows the DC input and MOSFET Q2 which has a rather odd configuration. It is actually in series with the negative return lead and we are using it for polarity protection instead of a silicon diode.

It works in two ways. Initially, at switch-on, the MOSFET is off, but its

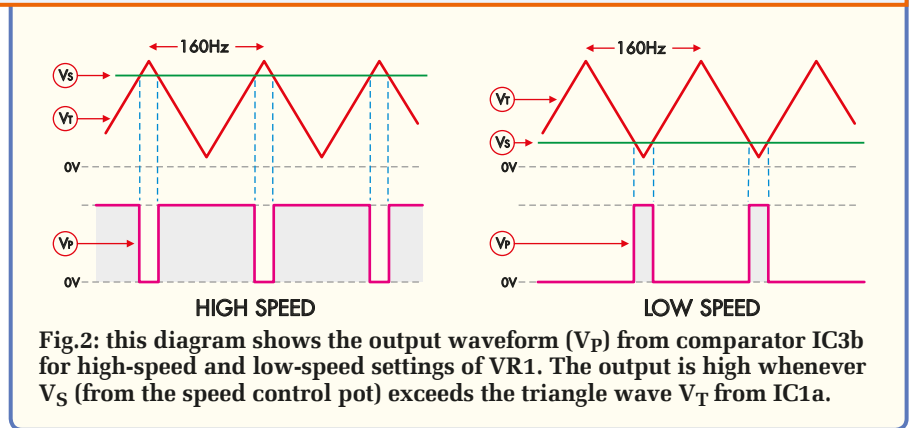


Fig.2: this diagram shows the output waveform (V_P) from comparator IC3b for high-speed and low-speed settings of VR1. The output is high whenever V_S (from the speed control pot) exceeds the triangle wave V_T from IC1a.

substrate diode (between drain and source) conducts to let current flow. Then, once the supply voltage across the three 2200 μ F input capacitors builds up, the MOSFET's gate is biased on and so the MOSFET turns hard on and conducts with a very low forward voltage of only a few tens of millivolts; much lower than even a Schottky diode, since its drain source resistance is only 5.3 milliohms!

Note that the MOSFET conducts even though its drain is negative with respect to its source electrode. If this seems a little puzzling, consider that a MOSFET will conduct in either direction, as long it has the correct gate voltage polarity; in this case, positive. If the supply polarity is reversed, there will be slightly negative gate bias (by virtue of reverse-biased Zener diode, ZD1) and neither the MOSFET nor its substrate diode will conduct.

Because the forward voltage loss across MOSFET Q2 is so low, the amount of power it dissipates at any current up to our rated circuit maximum is very low. In fact, at the rated circuit current of 8A, the power dissipated in Q2 is only around 340mW, which means

that, strictly speaking, it doesn't need any heatsinking at all.

The same general comment goes for Q1, which is also an IRF1405 automotive MOSFET. And minimum heat means that we can have a high-power circuit sitting in a small plastic case.


Relay rating

Given that the IRF1405 MOSFET is a high-power device, what actually sets our rated circuit current of 8A maximum? The answer is the reversing relay. Its contacts are rated to switch 8A DC. The other determinants of the maximum current are the two 0.1 Ω 5W wirewound resistors at Q1's source, as described later in this article.

Going back to the DC input, which can typically be 17V or more, after being fed in via the power switch S4, it then feeds 3-terminal regulator REG1, which provides 12V to all of the circuit except for Q1, which switches the 17V DC rail directly to the tracks.

Speed control

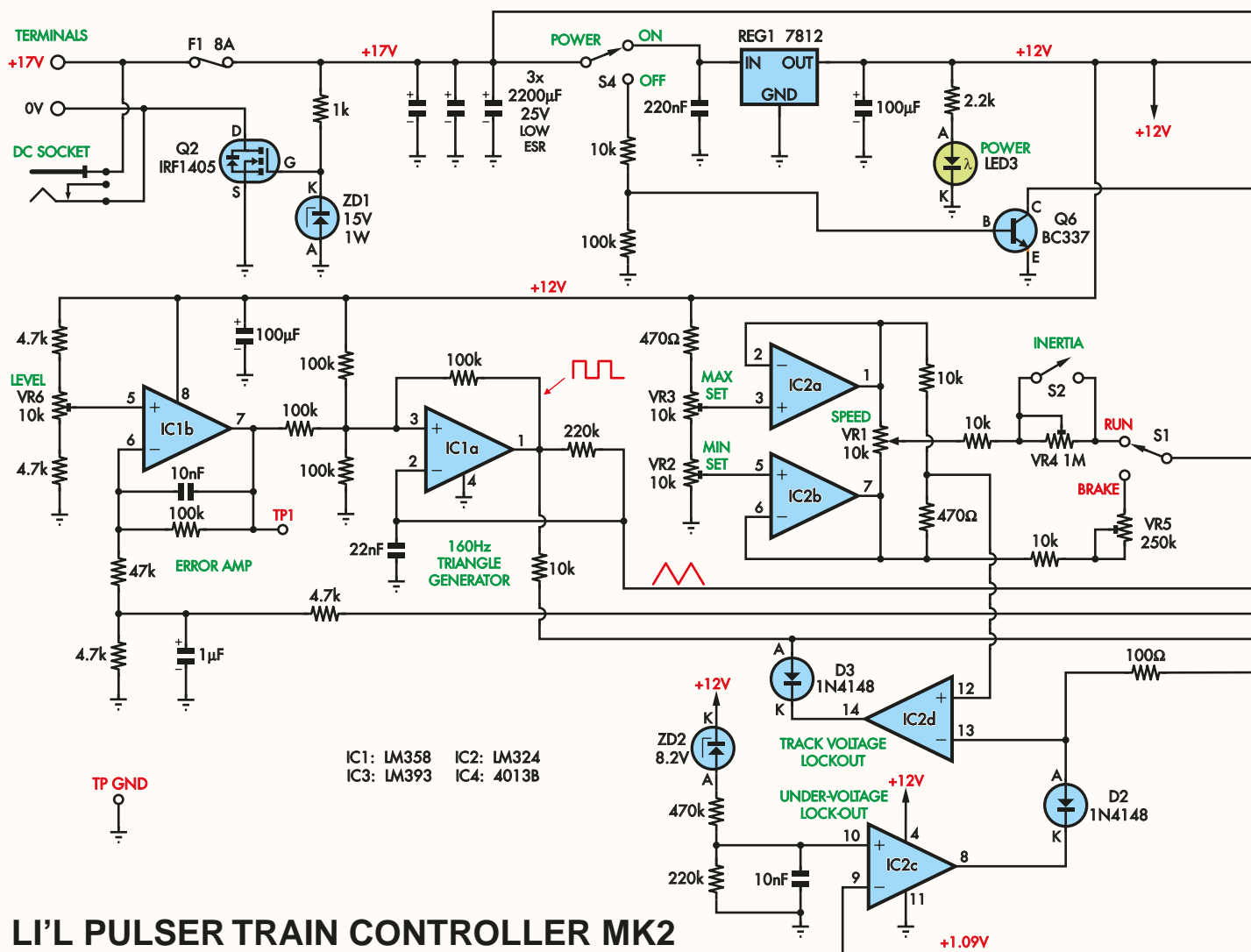Let's now look at how the basic circuit of Fig.1 has been refined. First, speed control potentiometer VR1 is fed via



LI'L PULSER TRAIN CONTROLLER MK2

Fig.3: the complete circuit for the *Li'l Pulser* includes back-EMF monitoring based on error amplifier IC1b, to ensure good speed regulation. Also included are a relay (RELAY1) to provide forward and reverse direction, simulated inertia, overload protection (IC3a) and a lock-out feature to prevent a change of direction until the loco has been brought to a stop (IC2d).

two op amps, IC2a and IC2b. These are connected as voltage followers, fed by trimpots VR2 and VR3. So VR2 provides the minimum speed setting (minimising the 'dead spot' at the low setting of speed potentiometer VR1) and VR3 provides the maximum speed setting, so that you cannot apply more than the maximum rated voltage for the locos you are using. Typically, HO-scale locos run with a maximum of 12V DC and N-scale locos typically run with a maximum of 9V.

The voltage from the wiper of speed control pot VR1 is fed via trimpot VR4 and switch S1 to the 47 μ F capacitor at pin 5 of IC3b. This provides the 'inertia'. What happens is that when you wind up the speed control pot, the actual change in voltage appearing at pin 5 of IC3b is slowed down by the time-constant of

VR4 and the 47 μ F capacitor. Higher settings of VR4 give more inertia, simulating the effect of a heavier train.

For shunting operations, we don't want inertia, so it can BE switched off by S2 which shorts out VR4.

Braking

While inertia is for simulating heavy trains, in the scale world of models, we normally want to stop or slow down trains much more quickly than would be possible (or safe) in the full-scale world. So braking switch S1 is included. It is set to RUN when the loco is being driven normally and then to BRAKE when you need to bring it to a quick stop.


In operation, setting S1 to BRAKE connects VR5 to the 47 μ F inertia capacitor and this has the effect of


discharging the capacitor to the output of IC2b, the minimum speed op amp. This means that the 47 μ F capacitor is only discharged to the point where Q1 is just turned off; any more and there would be more than the necessary delay when the brake was removed.

MOSFET switching

In our simplified circuit of Fig.1, we show the output pulses from IC3b directly driving the gate of MOSFET Q1. However, that is not the most effective way to drive the MOSFET if we want to minimise its power dissipation.

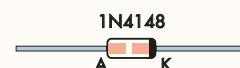The problem is that Q1 has quite a high gate capacitance, and if we just turn it on via IC3b's 10k Ω load resistor (this is an 'open-collector' output), Q1 would turn on relatively slowly for each



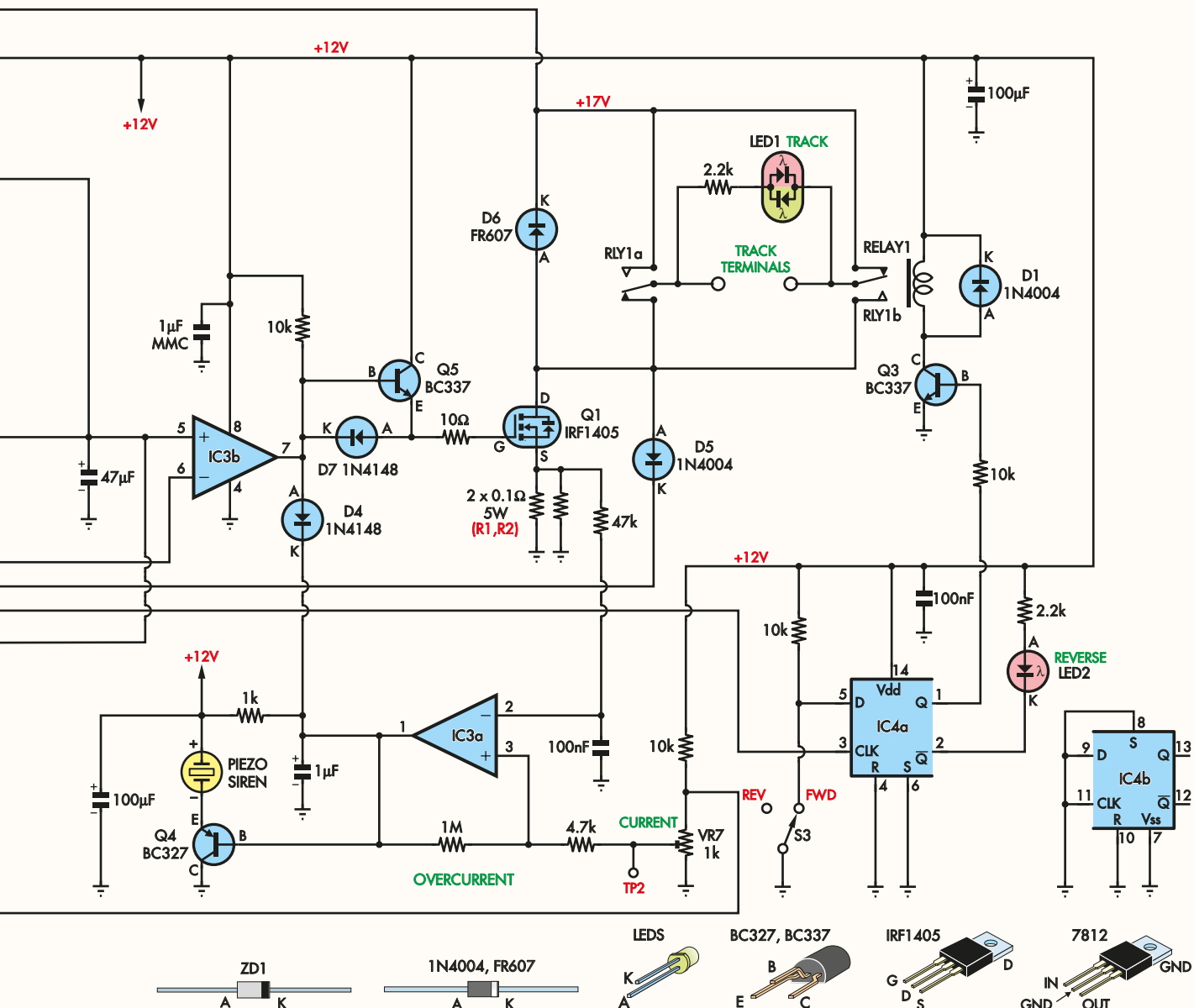

positive gate pulse. As a result, its dissipation would be higher than we want, as it would spend more time in partial conduction.

For that reason, the gate drive is via transistor Q5 which is connected as an emitter follower. This pulls up Q1's gate much faster, to minimise switch-on time. Conversely, when IC3b's output goes low, Q1's gate is quickly pulled low via diode D7.

Overload protection

Comparator IC3a provides the overload current protection. Two 0.1Ω 5W resistors connected in parallel monitor the load current (ie, through Q1) and the resulting voltage is fed to IC3a's pin 2 via a 47kΩ resistor. The associated 100nF capacitor provides filtering.

The non-inverting input at pin 3 is connected to trimpot VR7, the current setting control. If the voltage at pin 2 exceeds that at pin 3, IC3a's pin 1 output pulls pin 7 of IC3b low via diode D4. This removes gate drive from Q1.

You then get a 'hunt' condition whereby the removal of gate drive to Q1 stops the overload current, so IC3a's output goes high and the MOSFET switches on again. This switching on and off is slowed down using a 1μF capacitor connected to IC3a's output.

IC3a also drives a piezo alarm via transistor Q4 to indicate when an overload is occurring.

Speed regulation

The loco's motor generates a back-EMF that is directly proportional to

its speed. In other words, during the period that the motor is not driven by the pulses, it acts as a generator, supplying voltage at its output terminals. We use this back-EMF as a feedback signal to make sure that the controller maintains a relatively constant motor speed for a given throttle setting, regardless of variations in load.

In operation, the motor's back-EMF is monitored by D5, which conducts when MOSFET Q1 is off. Note that D5 monitors the negative terminal of the motor and any back-EMF will be negative with respect to the +17V rail. At low motor speeds, the back-EMF is close to the 17V supply. As the motor speeds up, it will generate more back-EMF and so the voltage we measure will be lower (with respect to +17V).

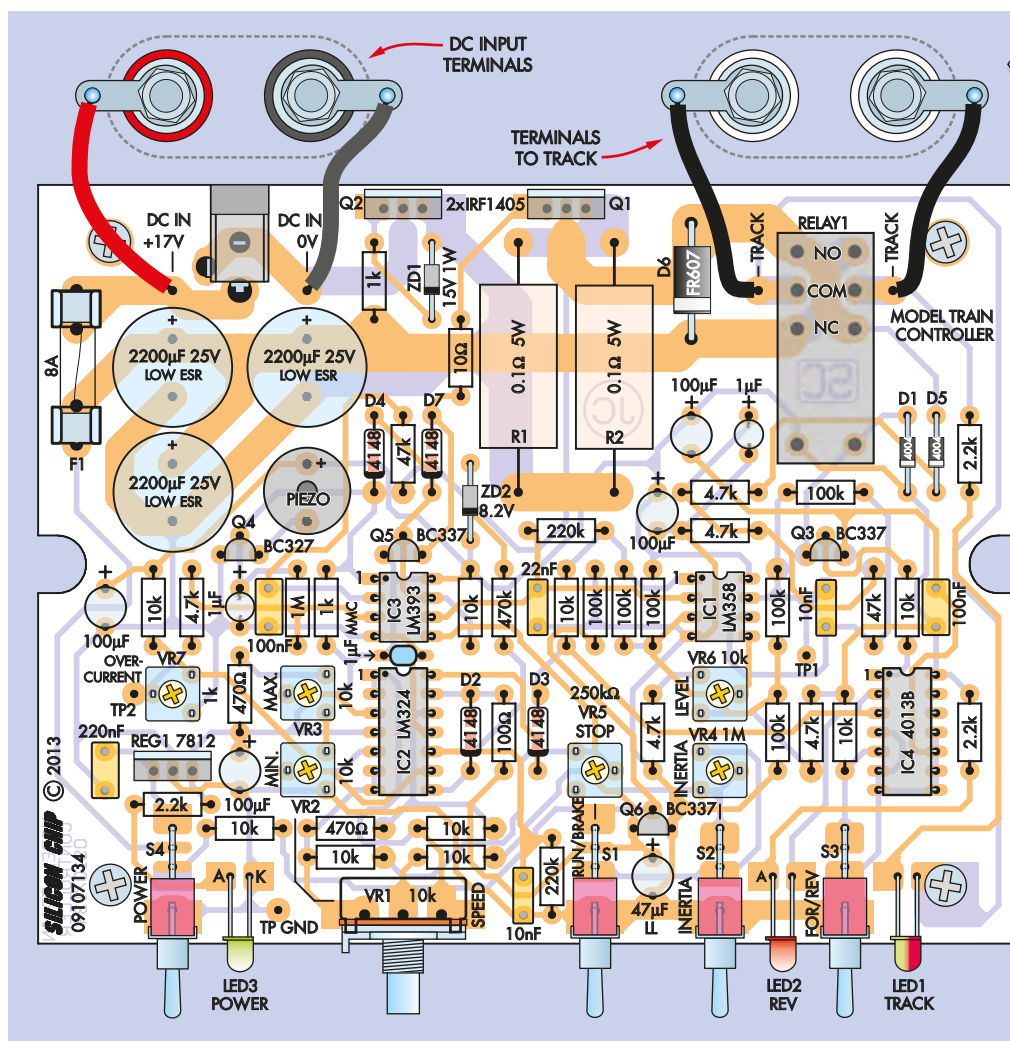


Fig.4: install the parts on the PCB as shown on this layout diagram. Be sure to orient the ICs, MOSFETs, diodes zener diodes and electrolytic capacitors correctly.



Right: the prototype used the plastic front panel supplied with the case, plus a paper label. PCB front panels with pre-drilled holes and screened lettering are available from the *EPE* online shop.

D5 feeds a $1\mu\text{F}$ capacitor via a voltage divider consisting of two $4.7\text{k}\Omega$ resistors and the resulting filtered voltage is fed to the pin 6 inverting input of op amp IC1b (the error amplifier). It amplifies the voltage by a factor of about two and its output is used to control the pin 3 threshold voltage of triangle generator IC1b via a $100\text{k}\Omega$ resistor.

So, as the motor speed drops, the back-EMF decreases, and the DC level from pin 7 of IC1b drops. This causes the triangle waveform generated by IC1a to drop with respect to the DC voltage from speed-control potentiometer VR1. This then results in wider positive gate pulses to MOSFET Q1 and more power fed to the motor to maintain the given speed setting.

Trimpot VR6, at pin 5 of IC1b, is included to give some compensation for different motor characteristics; some motors generate more back-EMF than others. VR6 is set so that pin 7 of IC1b is at about mid-supply voltage (ie, 6V) when a motor is con-

ected (more on that in the setting up procedure).

Reverse lockout

Forward and reverse switching is done by RELAY1. This turns on and reverses the loco when the Q output (pin 1) of D-type flipflop IC4a goes high and turns on transistor Q3. IC4a provides the forward/reverse lockout feature whereby the train's direction cannot be changed unless the track voltage is reduced to zero.

This works as follows: IC4a has its data input (pin 5) connected to either +12V via a 10kΩ resistor when the forward/reverse switch (S3) is open, or to 0V when S3 is closed. The Q output at pin 1 changes to the level set at pin 5 when a positive clock pulse is fed to pin 3. So if the setting of the forward/reverse switch is changed, the Q output of IC4a will not change until pin 3 gets a positive clock pulse.

In practice, we prevent a clock pulse from arriving until the gate pulses to

MOSFET Q1 are stopped. We do this by monitoring the voltage across the $47\mu\text{F}$ capacitor at pin 5 of IC3b (ie, the speed-setting voltage) using op amp IC2d, ie, via the 100Ω resistor to its pin 13 input.

IC2d's pin 12 is connected to a voltage divider between pin 1 of IC2a and pin 7 of IC2b. Hence, pin 12 will be very close to the minimum speed voltage from IC2b. So until the voltage across the 47 μ F capacitor drops below this minimum voltage (when the brake is applied, for example), IC2d's output will be low and this will short out any clock pulse to IC4a (ie, from IC1a) by forward biasing D3.

The 160Hz clock pulses are derived from the output of IC1a, the same op amp that provides the triangle waveform. As soon as the voltage across the 47 μ F capacitor drops below pin 12 of IC2d, the clock pulses will get through to IC4a. It will then change state and so will the relay.

IC2c is included to ensure that the 160Hz clock signal is applied to IC4a

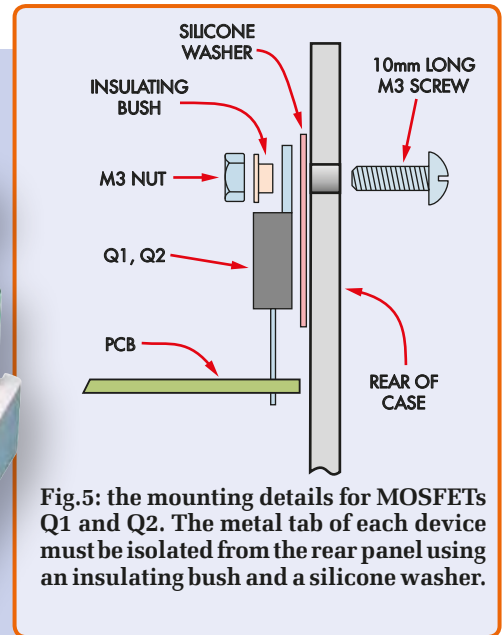


Fig.5: the mounting details for MOSFETs Q1 and Q2. The metal tab of each device must be isolated from the rear panel using an insulating bush and a silicone washer.

to give the correct setting of forward or reverse at switch-on, as set by the forward/reverse switch (S3). When power is first applied, the 10nF capacitor at pin 10 of IC2c is discharged and since this is lower than pin 9 which is biased to 1.09V, IC2c's output is low. As a result, diode D2 pulls pin 13 of IC2d low, so pin 14 of IC2d is high and the clock signal cannot be shunted to 0V by D3.

Zener diode ZD2 plus the voltage divider formed by the 470kΩ and 220kΩ resistors ensure that the supply rail has to rise above about 11V before IC2c's output goes high. When that happens, D2 is reverse biased and the forward/reverse lockout facility based on IC2d operates normally.

IC2c also provides an under-voltage lock-out facility. When the power is switched off, the supply rail quickly drops below 11V and pin 8 of IC2c goes low. As a result, the 47μF filter capacitor at pin 5 of IC3b quickly discharges via the 100Ω resistor in series with D2, and IC3b's output goes low.

This forces Q1 to stay off while the supply voltage decays to zero, so that no further output pulses are applied to the track.

As a belt and braces measure, transistor Q6 turns on when S4 is switched to the off position and rapidly discharges the 47μF filter capacitor. This ensures that there's no possibility of an output pulse, regardless of how quickly the under-voltage lock-out circuit kicks in.

Construction

Building the *Li'l Pulser* is easy, with all the parts assembled onto a PCB available from the *EPE PCB Service*, coded 09107134 and measuring 129.5 × 100.5mm. This is housed in a small instrument case measuring 140 × 35 × 110mm (W × H × D).

Our prototype used an adhesive label attached to the plastic panel supplied with the case for the front panel. However, we're making available from the *EPE PCB Service*, a PCB

front panel (code 09107132) with blue solder masking, screened lettering and all the holes pre-drilled for a really professional finish. This PCB panel is simply substituted for the supplied plastic panel.

We've also designed a rear-panel PCB (code 09107133) which is also available from the *EPE PCB Service*. This has solder-masked copper on both sides to provide heatsinking for the two MOSFETs (Q1 and Q2). The mounting areas for the MOSFETs are clear of solder masking to improve thermal contact and there are numerous vias between the two sides of this PCB to improve ventilation and heat transfer out of the case.

This PCB rear panel can be used for output currents up to about 5A. This should be more than adequate for the vast majority of layouts, including layouts running double-header (or even triple-header) locos with sound, steam and lighting.

For layouts requiring more than 5A (up to 8A maximum), it's best to use an aluminium rear panel for improved heatsinking (as in the prototype). You will have to cut this aluminium panel to size (134 × 32 × 1mm) and drill the holes yourself (details later). The original plastic panel supplied with the case is discarded.

Fig.4 shows the parts layout on the PCB. Begin by inspecting the board carefully for any defects (rare), then start the assembly by installing the 0.25W resistors. Table 1 shows the resistor colour codes, but you should also check each one using a digital multimeter before soldering it to the PCB.

Constructional Project

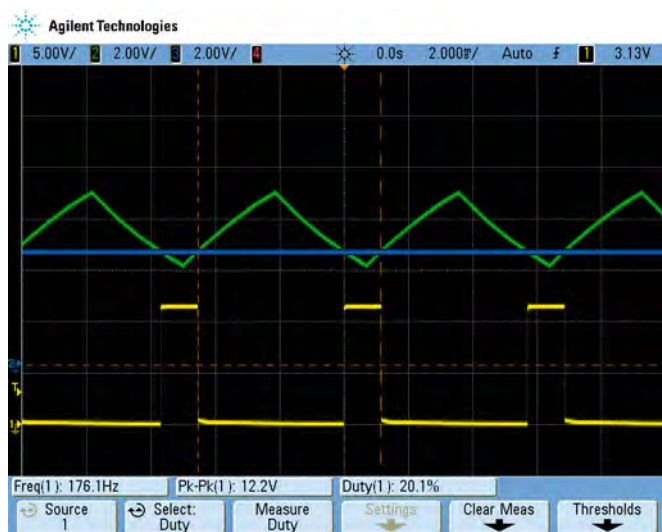


Fig.6: this scope grab shows the operation of IC1a and IC3b. The green trace is the triangle output from IC1a, while the blue trace is the DC voltage from speed pot VR1. The resultant pulse (yellow trace) from the output of IC3b is fed to the gate of MOSFET Q1. This is a low-speed setting.

The diodes (including ZD1 and ZD2) can go in next. Be sure to use the correct type at each location and make sure they are all oriented correctly. That done, install the capacitors and the two 0.1Ω 5W resistors (the latter can be mounted flush against the PCB, as they run only slightly warm). Take care with the orientation of the electrolytics – they all go in with their positive leads towards the rear of the PCB.

Follow with the trimpots, relay, piezo buzzer (watch its orientation), switches, potentiometer VR1 and the DC socket. Don't get the trimpots mixed up and be sure to trim VR1's shaft to suit the knob before soldering it to the PCB. The ICs can then be installed. Make sure their notched ends face the rear of the PCB, as shown on Fig.4.

Installing the MOSFETs

Regulator REG1 can now go in, followed by transistors Q3-Q6. Note that Q4 is a BC327 while Q3, Q5 and Q6 are BC337s. Don't get them mixed up.

MOSFETs Q1 and Q2 can now be installed. First, slip the PCB assembly into the case and secure it by installing the two rear mounting screws. That done, slide the rear panel into position, then mount the two MOSFETs on the PCB and temporarily fasten them, along with their insulating bushes, to the rear panel using machine screws and nuts (note: if you are using an aluminium rear panel, you will first have to download the artwork from the EPE website and use it as a template to drill the necessary holes).

Check that the rear panel is pushed all the way down into its case slot, then carefully tack solder the two outside

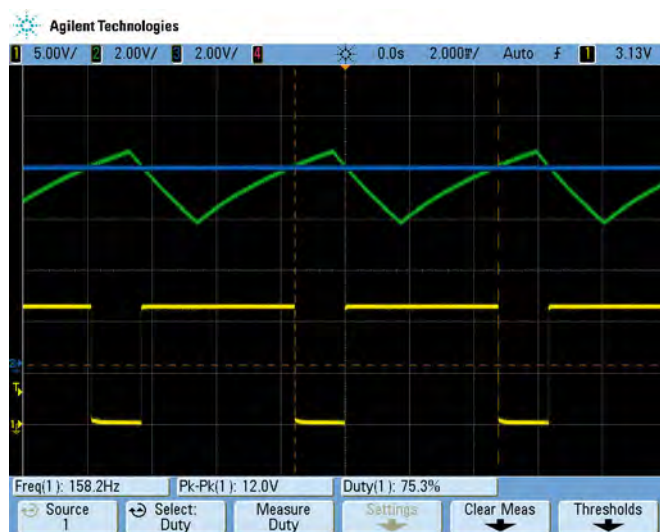


Fig.7: this scope grab shows the same signals as in Fig.6, but now the speed voltage from VR1 is higher, leading to wider positive output pulses from the output of IC3b. This corresponds to almost maximum speed. You can compare these scope grabs with the waveforms shown in Fig.2.

leads of each MOSFET to their pads on the top of the PCB. The PCB assembly can then be removed from the case and the MOSFET leads soldered on the underside.

The next step is to fit PC stakes to the four external wiring points and to the three test points (TP1, TP2 and TP GND). Follow with the two fuse clips, making sure that each goes in with its end stop towards the outside (otherwise you will not be able to install the fuse).

Table 2: Capacitor Codes

Value	μF Value	IEC Code	EIA Code
220nF	0.22μF	220n	224
100nF	0.1μF	100n	104
22nF	0.022μF	22n	223
10nF	0.01μF	10n	103

Table 1: Resistor Colour Codes

No.	Value	4-Band Code (1%)	5-Band Code (1%)
1	1MΩ	brown black green brown	brown black black yellow brown
1	470kΩ	yellow violet yellow brown	yellow violet black orange brown
2	220kΩ	red red yellow brown	red red black orange brown
6	100kΩ	brown black yellow brown	brown black black orange brown
2	47kΩ	yellow violet orange brown	yellow violet black red brown
9	10kΩ	brown black orange brown	brown black black red brown
5	4.7kΩ	yellow violet red brown	yellow violet black brown brown
3	2.2kΩ	red red red brown	red red black brown brown
2	1kΩ	brown black red brown	brown black black brown brown
2	470Ω	yellow violet brown brown	yellow violet black black brown
1	100Ω	brown black brown brown	brown black black black brown
1	10Ω	brown black black brown	brown black black gold brown
2	0.1Ω	not applicable	not applicable



The rear panel carries the four binding posts for the power supply and track connections. An on-board DC socket is also accessible via a hole in the rear panel and can be used instead of the red and black binding posts for currents up to about 4A.

Installing the LEDs

The PCB assembly can now be completed by fitting the three LEDs (LEDs1-3). Use the bi-colour LED for LED1 (Track), the red LED for LED2 (Reverse) and the green LED for LED3 (Power).

To install the LEDs, first orient each one in turn so that its anode lead is on the left (as viewed from the front), then bend its leads down by 90° about 8mm from its body. That done, solder the LEDs in place with their horizontal lead sections 5mm above the surface of the PCB (ie, in line with the switch centres).

The easiest way to achieve this is to cut a 5mm-thick cardboard spacer and simply push the LEDs down onto this before soldering their leads.

Final assembly

Now for the final assembly. The first step is to wind a nut onto VR1's threaded bush. Do this nut all the way up, then fit the front panel to the PCB assembly and secure it by fitting a second nut to VR1 (make sure the switches and LEDs all correctly protrude through the front panel before fitting this nut).

Next, fit the four binding posts to the rear panel – red for the +12-19V terminal, black for 0V and white for the two track posts. Once they're secure, attach a 45° 6.3mm chassis-mount spade terminal to each binding post and secure it using the two small end-nuts (see photo).

Making your own rear panel

An aluminium rear panel will be necessary if you intend using the *Li'l Pulser* to deliver currents above 5A. This panel should be 1mm thick and should be cut to 134 × 30mm.

Once you've cut the panel to size, download the rear-panel artwork (see Fig.10) from the *EPE* website. Print this out onto both plain paper and photo paper.

The paper version is used as the drilling template, while the photo paper version is used as the label. Use a pilot drill to start the holes, then enlarge them to size using larger drills and finish off with a tapered reamer.

The spade terminal ends close to the end-nuts should now all be trimmed so that the don't later interfere with the relay and the DC socket when it's all assembled in the case. This can be done using tin-snips and then filing them down. In addition, you will have to trim the ends of the posts so that they protrude no more than about 1.5mm beyond the end-nuts.

If you can only get double-ended spade terminals, just cut one side off.

Once the spade terminals are in place, they can be connected to their respective PCB stakes via short lengths of heavy-duty (8A) hook-up wire. Solder these wires to the PCB stakes first, then fit short lengths of heatshrink sleeving over

the connections and shrink it down. This will stop the leads from flexing and breaking at the stakes.

Once the holes have been drilled, the label can be affixed to the lid using a suitable glue or silicone and the holes cut out using a sharp hobby knife. Another alternative is to discard the case altogether and mount the PCB assembly under the layout. You could then mount the speed pot, switches and LEDs on a separate control panel and connect them back to the PCB via flying leads. The two MOSFETs can then either be mounted on an aluminium heatsink or fitted with small finned heatsinks.


The other ends of the wires are then soldered to the spade terminals.

That done, the completed assembly can be installed in the case and the PCB secured to the four corner pillars in the base using four M3 × 5mm screws. Don't worry if the positive binding post terminal touches the adjacent fuse clip, as these are connected together on the PCB anyway, so it doesn't matter.

Securing the MOSFETs

Regardless as to which type of rear panel is used (PCB or aluminium), MOSFETs Q1 and Q2 must both

Constructional Project

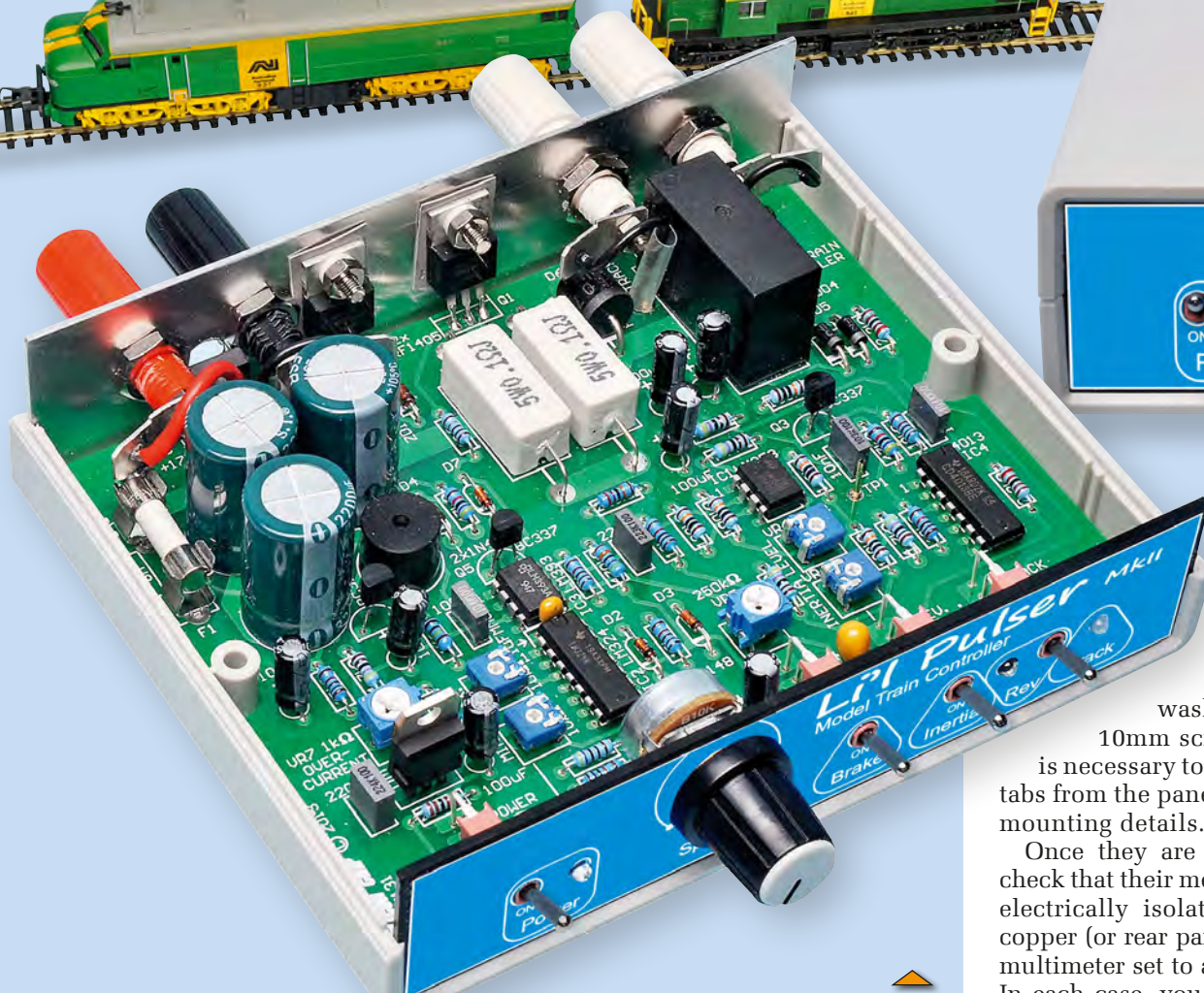

be attached using an insulating bush, insulating washer and an M3 × 10mm screw and nut. This is necessary to isolate their metal tabs from the panel. Fig.5 shows the mounting details.

Once they are secured in place, check that their metal tabs are indeed electrically isolated from the PCB copper (or rear panel) using a digital multimeter set to a high ohms range. In each case, you should get a high megohms (or open circuit) reading. If

Another view inside the prototype. MOSFETs Q1 and Q2 must be isolated from the rear panel, regardless as to the type of panel used (aluminium or PCB).

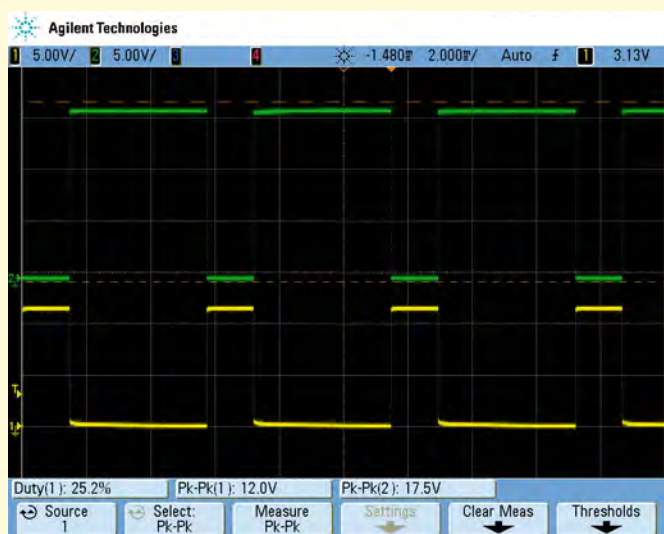


Fig.8: these scope waveforms were taken at the gate and drain of MOSFET Q1 to show its switching action. The yellow trace is the gate waveform from IC3b, while the green trace is at the drain and shows the pulses applied to the track, with a resistive load connected. Note that when the gate is positive, the MOSFET switches on and pulls its drain low.


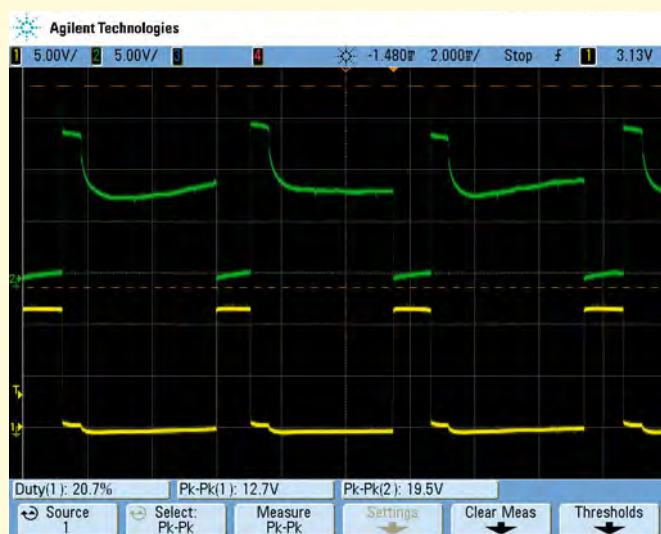


Fig.9: these scope waveforms are again from the gate and drain of MOSFET Q1 but with a 12V permanent magnet motor connected. The green trace shows that when the MOSFET switches off, the voltage at the drain immediately rises to about 17V, but then drops due to the back-EMF generated by the motor. At a higher throttle setting, the back-EMF would be higher, leading to a greater drop at Q1's drain.

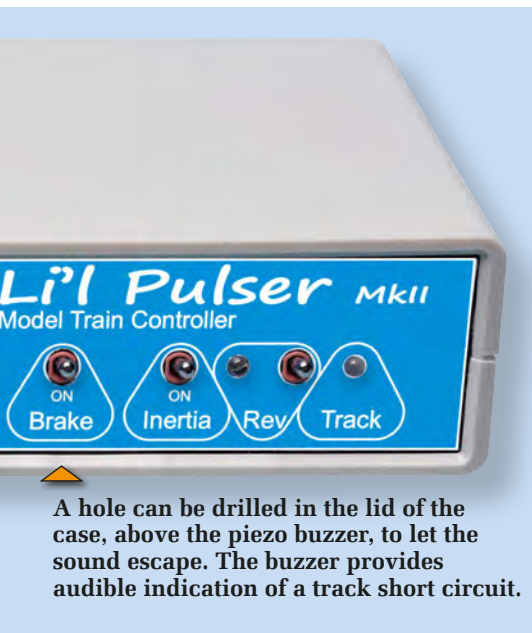

A hole can be drilled in the lid of the case, above the piezo buzzer, to let the sound escape. The buzzer provides audible indication of a track short circuit.

not, undo the assembly and locate the source of the problem.

Finally, a 6mm hole can be drilled in the lid of the case directly above the piezo siren, to let the sound out when an overload is detected. Be careful when marking out the position of this hole for drilling – the lid will only fit correctly in one direction.

Testing

As mentioned earlier, the *Li'l Pulser* train controller can be powered from a train power supply, a 12V battery charger or from a 15-19V switchmode laptop PC power supply. The current rating of the supply will depend on your individual requirements, but around 5A will be quite sufficient for most applications. However, you will need a supply with an 8A rating if you want the *Li'l Pulser* to deliver its maximum 8A output capability.

Before connecting the supply, go over your work carefully and check that all parts are in their correct locations and that all polarised parts are the right way around. That done, connect the supply to either the DC socket or to the red and black binding posts.

As stated, the DC socket is only rated up to about 4A. If your supply has a higher current rating, use the binding posts to make the supply connections.

The unit can now be checked out by following this step-by-step procedure:

- 1) Apply power and check that there is 12V between pins 8 and 4 of IC1.
- 2) Wind the speed pot (VR1) fully anticlockwise and adjust all trimpots to mid-setting.
- 3) Check that the brake, inertia and reverse switches are all off, then advance the speed pot and check that the track LED lights green. Check that it gets brighter as you wind up the throttle.
- 4) Leave the speed pot at a high setting, switch to reverse and check that the reverse LED (LED2) stays off (ie, because of the lockout).
- 5) Wind the speed pot down and check that the reverse LED lights when the pot is almost fully anticlockwise. Now wind the speed pot up again; track LED1 should now be lit.

If that all checks out, then the *Li'l Pulser* is working correctly and you can proceed to set the current limit. That's done as follows:

- 1) Connect a multimeter between TP2 and TP GND.
- 2) Adjust VR7 for a reading of 50mV for each amp of the required current limit. For example, adjust VR7 for a reading of 150mV for a 3A current limit. Similarly, a 400mV reading will give the maximum 8A current limit.
- 3) Short the output terminals and slowly advance the speed pot. Check that the piezo alarm sounds to indicate a short. Note that the fuse should be changed to a lower rating if the current limit (and/or the supply rating) is lower than 8A. Use a fuse rating that corresponds to the current rating of the supply

and set the current limit to be equal to or less than this value.

Final adjustments


The final adjustments involve adjusting the minimum track voltage setting, setting the maximum speed and adjusting the inertia and braking trimpots. The steps are as follows:

- 1) Set the speed pot (VR1) to minimum and connect the *Li'l Pulser* controller to length of track with a loco.
- 2) Monitor test point TP1 and adjust trimpot VR6 for a reading of 6V.
- 3) With the speed pot at minimum, adjust VR2 fully anticlockwise and then slowly clockwise until there is a small amount of track voltage as indicated by noise in the loco motor. Back off the trimpot just a little from that point.
- 4) Remove the loco from the track, wind the speed pot fully clockwise and measure the DC voltage across the track terminals. Adjust VR3 for the maximum required track voltage. This is usually set for 12V, but you may wish to make this lower to limit the maximum speed of the locos.
- 5) With the loco back on the track, check that it runs smoothly as the speed control is advanced. Adjust the inertia trimpot (VR4) and the brake trimpot (VR5) to give the required simulated inertia when accelerating and braking.

Note that advancing VR4 past its mid-setting can also have an effect on the minimum speed. That means you may need to readjust the minimum and maximum speed settings (steps 3 and 4 above) after adjusting VR4.

Reproduced by arrangement
with SILICON CHIP
magazine 2014.
www.siliconchip.com.au

Fig.10: this rear-panel artwork can be copied or downloaded from the *EPE* website and used as a drilling template for an aluminium rear panel. For output currents up to 5A, use the suggested PCB rear panel (see text).

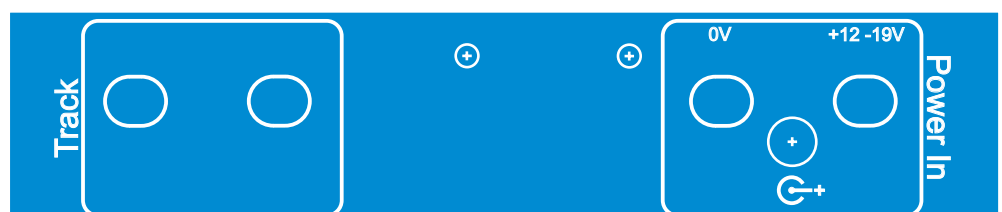

Fraudulent fridges and magic mushrooms

Is your icebox misbehaving? 'Titter ye not!' Not long ago a 'smart' refrigerator was involved in a massive cyber attack. It may sound ridiculous, but it's proof that the Internet of Things needs to be restrained. Mark Nelson reports.

THOSE OF YOU WITH LONG memories will recall that we discussed the Internet of Things back in the May issue, citing the benefits of integrating a vast plethora of Internet-enabled gizmos and gadgets into a network in order to let them communicate with one another. Now the downside of this arrangement has emerged.

Under the headline, 'More than 750,000 Phishing and SPAM e-Mails Launched From Thingbots', a Californian data security vendor by the name of Proofpoint set out its findings earlier this year. The company revealed that it had uncovered what may be the first proven Internet-of-Things-based cyber attack involving conventional household 'smart' appliances. The global attack campaign involved more than 750,000 malicious email communications coming from more than 100,000 everyday consumer gadgets such as home-networking routers, connected multi-media centres, televisions and at least one refrigerator. All these had been compromised and used as a platform to launch carefully targeted attacks.

Poor protection

According to Proofpoint, cyber criminals have begun to commandeer home routers, smart appliances and other components of the Internet of Things (IoT) and transform them into 'thingbots' to carry out malicious activities. Their task is made all the easier, since these poorly protected Internet-connected devices may be more attractive and easier to infect and control than PCs, laptops, or tablets.

The attack that Proofpoint observed and profiled occurred between 23 December 2013 and 6 January 2014. It featured waves of malicious email, typically sent in bursts of 100,000, three times per day, targeting companies and individuals worldwide. Misconfigured smart gadgets and the use of default passwords left devices completely exposed on public networks, available for takeover and use.

Consumers powerless

According to David Knight, general manager of Proofpoint's Information Security division, 'Consumers have virtually no way to detect or fix infections when they do occur. This is the first time that the industry has

reported actual proof of such a cyber attack involving common appliances – but it likely will not be the last example of an IoT attack. IoT includes every device that is connected to the Internet – from home automation products, including smart thermostats, security cameras, refrigerators, microwaves, home entertainment devices like TVs and gaming consoles, to smart retail shelves that know when they need replenishing and industrial machinery. But IoT devices are typically not protected by the anti-spam and anti-virus infrastructures available to organisations and individual consumers, nor are they routinely monitored or sent software patches to address new security issues as they arise.'

It gets worse. Michael Osterman, principal analyst at Osterman Research, comments, 'Consumers have little incentive to make IoT devices more secure, few vendors are taking steps to protect against this threat, and the existing security model simply won't work to solve the problem.' Clearly, industry and consumers need to keep an eye on this growing problem.

Mushrooms and mobiles – a valuable combination

Obsolete and damaged mobile phones are now worth a lot more than they used to be, thanks to a truly 'green' technique invented in Finland's VTT Technical Research Centre. The eco-friendly process, which involves the mycelium of mushrooms (hair-like growths normally found in the soil below the mushrooms), is claimed to recover up to 80 per cent of the gold found in scrap mobile phones and similar devices. This is part of the EU's 'Value From Waste' project, tasked with developing recovery processes on a more sustainable basis; to clean materials of impurities that reduce opportunities for further use; and to increase the amount of recovered materials.

Magic mushrooms

Fungi perform vital roles in ecosystems, probably the most important of which is to decompose organic compounds as they rot. They also have the potential to remove certain pollutants biologically from the soil environment, in a process that occurs entirely naturally. When employed artificially for industrial

purposes, 'mats' of fungal mycelium have the potential to act as biological filters, removing chemicals and microorganisms from soil and water.

Unwanted mobile phones contain precious and scarce metals, such as gold and copper. Using the intrinsic ability of mycelium to filter materials, VTT has developed a biological filter made of mushroom mycelium mats, enabling recovery of as much as 80 per cent of the gold in electronic scrap. In addition, extraction of copper from circuit board waste can be enhanced significantly by flotation of the crushed and sieved material.

Pre-treatment helps

VTT researchers have developed both biological and mechanical pre-treatment methods for efficient recovery of precious metals from electronic waste. Other methods developed by researchers included recovery of gold from dissolved materials by biosorption and extraction, using as few harmful chemicals as possible. In particular, the project has developed a method with high extraction capacity for gold recovery, using the newest environmentally friendly extraction reagents. In VTT experiments, it was possible to recover more than 90 per cent of the metal solution dissolved from a circuit board with the help of functional ionic liquid. The method facilitates extraction of target components from impurities. The uniqueness of the method lies in the structure of the biomass, which can be varied using different filament structures of mycelium mats to simplify further industrial processing of precious metals.

Well worthwhile

The potential value of recycling precious metals from e-waste is massive. One estimate considers that 100,000 life-expired cellphones contain 2.4kg of gold, more than 900kg of copper and 25kg of silver. Market prices for scrap vary, but the value could amount to £148,000. Olli Salmi, research professor at VTT, says that their ultimate goal is to make these techniques work on the same industrial scale as current recovery methods used. 'We have been most successful with gold so far, but we'll be working to recover other rare metals too', he comments.

**EPE
EXCLUSIVE**


Win one of two Microchip PICDEM 2 Plus Boards

EVERYDAY PRACTICAL ELECTRONICS is offering its readers the chance to win a Microchip PICDEM 2 PLUS Board. This board demonstrates the capabilities of Microchip's 8-bit microcontrollers, specifically, 18-, 28- and 40-pin PIC16FXXX, PIC16F1XXX, and PIC18 devices. It can be used as a standalone demonstration board with a programmed part. Alternatively, it can be used with an in-circuit emulator (for example, MPLAB Real ICE™) or with an in-circuit programmer/debugger (such as MPLAB ICD 3 or PICkit™ 3). Sample programs are provided to demonstrate the unique features of the supported devices.

Key features:

- Demonstration program displaying a real-time clock, ambient temperature and much more
- Demonstration program loaded on the installed PIC16F1937 (40-pin) MCU
- Sample kit with PIC16F1827 (18-pin), PIC16F1936 (28-pin) and PIC18F46K22 (40-pin) MCUs
- Source code for all programs
- Generous prototyping area

**WORTH
\$99.99
(approx. £59.00)
EACH**

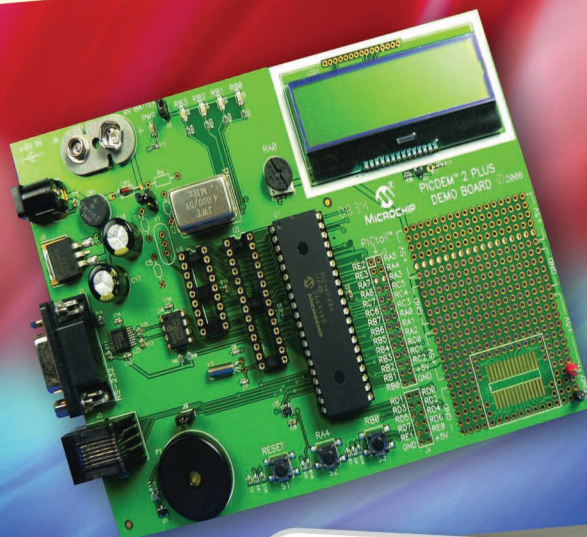

MARCH 2014 ISSUE WINNER
Ian Williams, who works at Sterling
Security Systems Ltd in UK

Ian won an LED Lighting
Development Board valued
at \$249.00

HOW TO ENTER

For your chance to win a PICDEM 2 Plus Board, please visit:

www.microchip-comps.com/epe-picdem2plus and enter your details in the online entry form.

CLOSING DATE

The closing date for this offer is 31 July 2014

Two demonstration circuits for human colour vision

By James Goding

THE HUMAN EYE can see millions of different colours, representing light with a range of wavelengths from about 680nm (deep red) down to about 390nm (deep violet). But we can be fooled into seeing many colours by a TV screen that contains just red, green and blue light emitters (RGB).

Why is that? And why do printers and artists use a different set of colours: cyan, magenta, yellow and black (CMYK)?

These two simple circuits aim to reveal the operation of the human eye and clear up the mysteries through practical demonstrations. Build them into little boxes and you will have a source of delight and amusement for children, and education for young and not-so-young adults.

The human eye contains two types of photo-receptor: around 120 million 'rods', which are concentrated around the edges and 6-7 million 'cones', which are mostly in the centre of the retina (the fovea). The cones allow us to see colour and most people have three types, with broad sensitivity peaks centred towards the red end of

the spectrum (560nm), green (530nm) and blue (420nm) – see Fig.1.

The perception of colour by the brain depends on the relative amounts of stimulation of each of these types of photo-receptor. Because the photo-receptors have persistence, rapidly alternating red and green light gives the effect of stimulating the red and green receptors simultaneously. The brain interprets this as yellow. And because the photo-receptor absorption peaks are broad, pure yellow light at 585-590nm also stimulates both red and green receptors.

This is demonstrated by the circuit of Fig.2. IC1 is a 555 timer which generates a quasi-sawtooth waveform with a frequency set using potentiometer VR1. This is buffered by op amp IC2b, half of an LMC6482 rail-to-rail op amp and then fed to the other half of this op amp, which acts as a comparator. VR2 is used to adjust the voltage which the sawtooth waveform is compared against, producing a variable-duty cycle PWM output at pin 1 of IC2a.

This output is used to drive the red element in LED1, which emits light at

625nm. The same signal is also fed to PNP transistor Q1, which acts as an inverter, turning on the green element (568nm) whenever the red one is off, and *vice versa*. So you can use VR2 to adjust the relative on-times of LED1 and LED2 while changing the frequency with VR1.

When the rate of flashing is slow and the duty cycle is set at about 50%, the viewer sees alternating red and green but as the flashing rate is increased, there comes a point where the LED appears yellow. Under conditions of rapid flashing, when the duty cycle knob is rotated, there is a smooth transition from red to orange to yellow and then to green. Slowing the flashing rate provides proof that no trickery is involved.

Note that the red and green cone sensitivity curves shown in Fig.1 overlap much more closely than do the green and blue. Despite this, we are still able to distinguish subtle variations in the shades between green and red because our brains are interpreting the differences in absorption between the two different types of cone cell.

We should point out that some 8% of Caucasian males have red/green colour blindness (dichromacy), mostly due to genetics. Because females have two X chromosomes and the genes to express colour vision are on this chromosome, they effectively have two copies of these genes and so are much less likely to develop colour blindness. While called 'blindness', in most cases the result is a reduction in the ability to distinguish between certain shades of red, yellow and green.

People with one of these conditions will perceive the transitions between red, green and yellow (if visible) at different points than those without. By the way, it is a myth that dogs and cats can't see colour – they have two types of cones, blue and yellow, giving

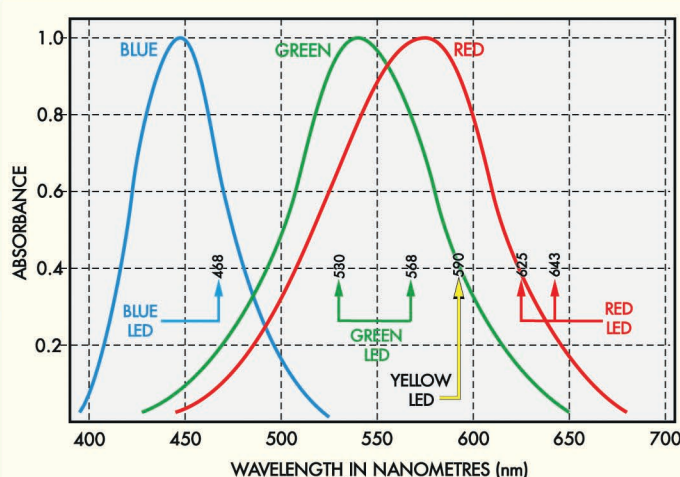


Fig.1: the human eye has three colour sensitivity peaks centred on 560nm (red), 530nm (green) and 420nm (blue).

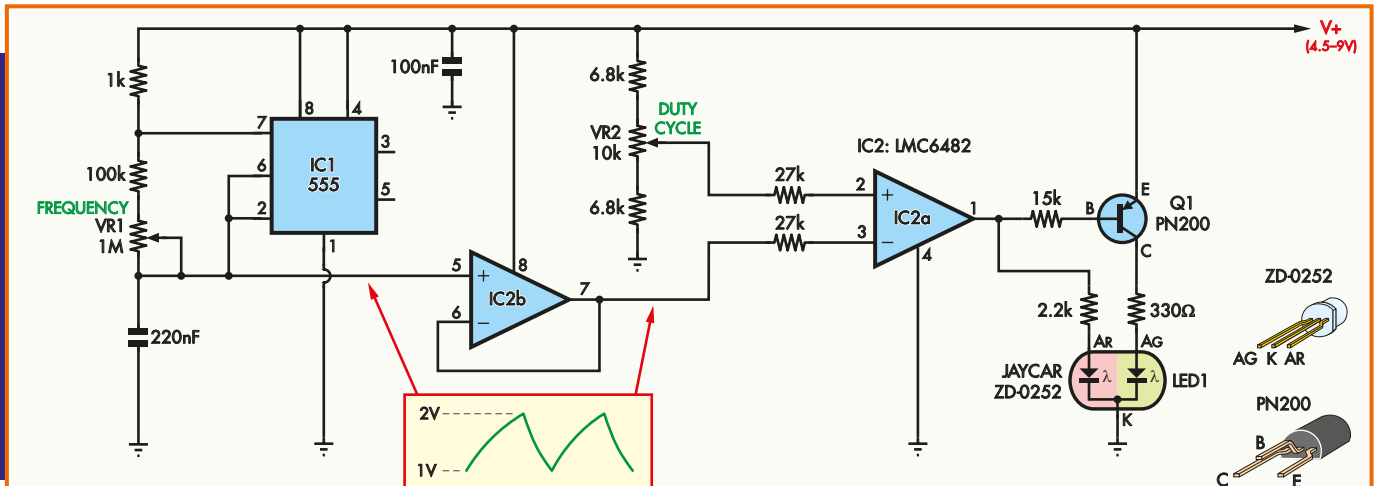


Fig.2: this demonstration circuit uses a 555 timer as a sawtooth oscillator. Its output is buffered by IC2b and compared in comparator IC2a with a voltage set by VR2. IC2a then directly drives the red section in a bi-colour LED (LED1) and the green section in LED1 via transistor Q1. VR2 adjusts the relative on-times of the two colours.

them similar (but not identical) vision to that of a human with dichromatic colour blindness.

Introducing blue

That brings us to the circuit shown in Fig.3, which uses an RGB LED (LED1), allowing you to experiment with any combination of red, green and blue light to see what colour the result appears. The Jaycar ZD0010 RGB LED used is a 'Tri 5 Superflux' with wavelengths of 468nm (blue), 528nm (green) and 643nm (red). The three LED elements are driven by three potentiometer-controlled constant-current sources.

LED2 can be virtually any low-cost red LED and should be positioned so that its lens is hidden. It is used not for its light but for its forward voltage; this is used to bias the bottom ends of the three pots so as to maximise their useful range of rotation. A 2.4V Zener diode would also work, but a red LED is easier to obtain.

If all three knobs are turned fully clockwise, the LED output appears approximately white, since each type of cone in your eye is being stimulated more or less equally. If the blue knob is turned down, the colour changes to yellow. If the red knob is turned down, the colour changes to turquoise (cyan) and if the green knob is turned down the colour changes to purple (magenta).

By manipulating different combinations of the settings of the knobs, any colour can be produced. For example, pink is produced by mixing a small amount of green with a small amount of blue and adding a slight excess of red. This is of course the equivalent of mixing red and white light.

Some limitations should be mentioned. Because the coloured elements of the LEDs are slightly displaced from each other, the colour merging is not quite perfect and the effects are best seen at a slight distance.

Finally, these toys are endlessly fascinating for children, but they forget to turn them off. To conserve battery life, a pushbutton switch could be used for the power.

Further experiments

Now let's look at the question we asked in the first paragraph: why do we use CMYK (cyan, magenta, yellow and black) inks rather than RGB (red, green and blue) like a TV or computer screen? The answer is that video displays create colour additively, just like our second circuit. But ink works by absorbing certain wavelengths of light that would otherwise be reflected from the white paper beneath, and so we combine inks in a subtractive manner.

Cyan ink absorbs red light, allowing green and blue to be reflected from the

white paper and the combination of the reflected green and blue light gives it its cyan hue. Similarly, magenta ink absorbs green light but reflects red and blue, while yellow ink absorbs blue light but not red or green.

So if we put a layer of cyan ink down on paper, then yellow, light that would stimulate the red and blue sensitive cones in our eyes is absorbed, leaving just green wavelengths and thus we see it as green. Similarly, red can be made with magenta and yellow inks and blue can be made with cyan and magenta inks.

Black can be made by combining cyan, magenta and yellow inks but black ink is usually used as well as the other three, since black is a common colour in printing and this reduces the total amount of ink used. There are also other benefits that we won't go into here.

Reproduced by arrangement with SILICON CHIP magazine 2014.
www.siliconchip.com.au

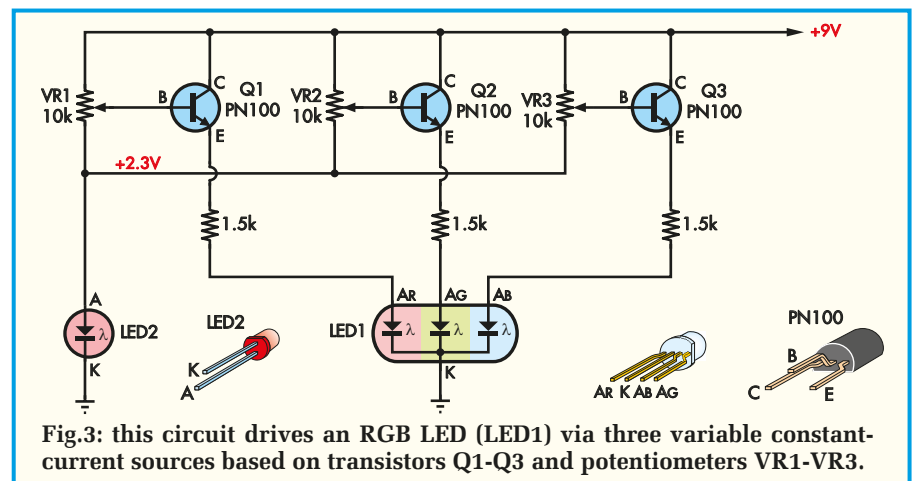


Fig.3: this circuit drives an RGB LED (LED1) via three variable constant-current sources based on transistors Q1-Q3 and potentiometers VR1-VR3.

Teach-In 2014



Raspberry Pi – Part 10

by Mike and Richard Tooley

Welcome to *Teach-In 2014* with Raspberry Pi. This exciting series has been designed for electronics enthusiasts wanting to get to grips with the immensely popular Raspberry Pi, as well as computer buffs eager to explore hardware and interfacing. So, whether you are considering what to do with your Pi, or maybe have an idea for a project but don't know how to turn it into reality, our *Teach-In* series will provide you with a one-stop source of ideas and practical information.

The Raspberry Pi offers you a remarkably effective platform for developing a huge variety of projects; from operating a few lights to remotely controlling a robotic vehicle through the Internet. *Teach-In 2014* is based around a series of practical exercises with plenty of information for you to customise each project to meet your own requirements.

The Raspberry Pi is no mean performer; it can offer you very similar performance to that which you might expect from a larger and much more expensive computer system, so don't be fooled by the relatively small price tag. By shopping around you can build a very effective computer system based on a Raspberry Pi for less than £100. However, if you are looking for something more modest and just want to take advantage of the Raspberry Pi as a single-board computer for a particular control application then you can be up and running for a very reasonable outlay.

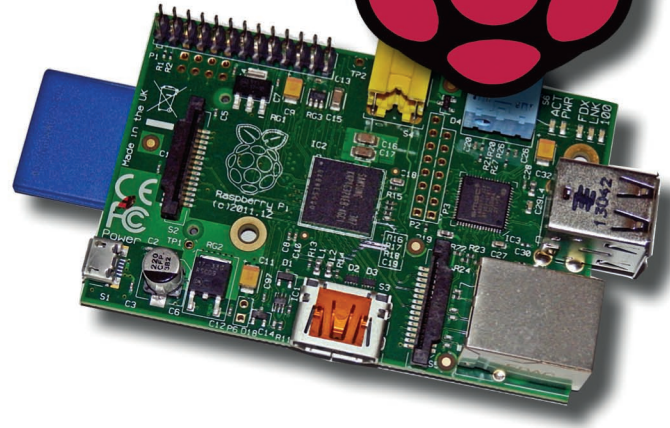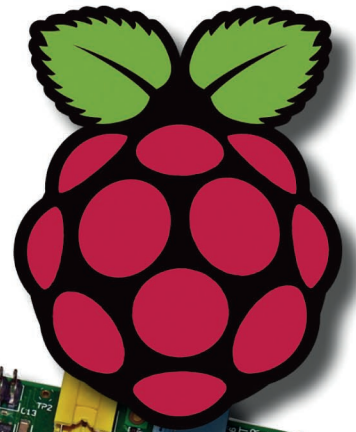

This series will teach you about:

- **Programming** – introducing you to the powerful Python programming language and allowing you to develop your programming skills
- **Hardware** – learning about the components and circuits that are used to interface microcomputers to the real world
- **Computers** – letting you get to grips with computer hardware and software and helping you understand how they work together
- **Communications** – showing you how to connect your Raspberry Pi to a network and control a remote device using Wi-Fi and the Internet.

So, what's coming up? Regular features of *Teach-In 2014* with Raspberry Pi will include:

- **Pi Project** – the main topic for each part will be a project that explores a particular use or application of the Raspberry Pi in the real world. Projects will include shopping for your Pi, set up, environmental monitoring, data logging, automation and remote control.
- **Pi Class** – each of our Pi Projects will be linked to one or more specific learning aims. Examples will include methods of representing and handling data, serial versus parallel data transmission and architecture of a microprocessor system.
- **Python Quickstart** – a short feature devoted to specific programming topics, such as data types and structures, processing user input, creating graphical dialogues and buttons and importing Python modules. We will help you get up and running with Python in the shortest time!
- **Pi World** – this is where we take a look at a wide range of Raspberry Pi accessories, including breadboards, prototype cards, bus extenders and Wi-Fi adapters. We will also help you build your Raspberry Pi bookshelf with a selection of recommended books and other publications.
- **Home baking** – suggested follow-up and extension activities such as 'check this out', a simple quiz, things to try and websites to visit.
- **Special features** – an occasional 'special feature'. For example, how to laser cut your own mounting plate – with additional downloadable resources such as templates and diagrams.

What will I need?

To get the best out of our series you will, of course, need access to a Raspberry Pi. If you don't already have one, don't worry – we will be explaining what you need and why you need it (we will also be showing you how you can emulate a Raspberry Pi using a Windows PC).

This month

In the final part of *Teach-In 2014*, our *Pi Project* features the construction of a real-time clock interface for the Raspberry Pi. This handy module can be used as an independent time reference for use with your own Python applications. It can also be configured so that it replaces the Pi's 'fake' hardware clock, thus providing you with an accurate, reliable and continuously available system clock. *Python Quickstart* will show you how tkinter can improve the user interface with labels and buttons. We'll also have the answers to our *Home Baking Quiz*. Finally, we will provide you with a comprehensive index of all ten parts of the series.

Python Quickstart

In last month's *Python Quickstart*, we showed you how you can use Python to create an HTML page that can be rendered in an ordinary web browser. This month, we will be looking at ways in which you can produce a more professional looking user interface by incorporating labels and buttons in your Python code. Once again, we will be using tkinter (supplied as standard with Python) as the basis of our GUI interfaces. For more information on tkinter you should refer back to Part 4 of *Teach-In 2014*.

Labels and the label widget

We briefly introduced tkinter's label widget in Part 4 and showed how we can display simple text strings in a window using simple code like this:

```
from tkinter import *
root = Tk()
w = Label(root, text="Teach-In with Raspberry Pi")
w.pack()
root.mainloop()
```

It's worth remembering that this code will remain in the event loop until we close the window (just click on the close button at the top right hand corner of the window). Not only does the event loop handle events from the user (such as the mouse click to close the window) but it also handles redraw messages allowing, for example, the window to be dragged, re-sized, minimised and maximised.

If you don't specify a size, the label window is made just large enough to hold its contents, but if you would prefer to set the size of the window you can use the widget's height and width options. These options define the size of the label in text units.

Labels can display multiple lines of text by including new line characters. You can also make use of the wraplength option to make the label wrap the text by itself. When wrapping text, the anchor and justify options provide greater control of how the text appears. In addition, you can set the foreground (fg) and background (bg) colour options to allow you to use different colours in the label. You can also select the font (choose from one of Tk's standard font descriptors) to use for the label text. As an example, the following code displays the copyright message shown in Fig.10.1. Note that we have selected Helvetica font with green text on a black background and that the label window has been sized automatically.

```
from tkinter import *
root = Tk()
copyright = """
Copyright (c) 2014 Everyday Electronics
Permission is hereby granted, free of charge,
to any person obtaining a copy of this
software and associated documentation files (the
"Software"), the rights to use, copy, modify,
merge, publish, distribute, sublicense, and/or
sell copies of the Software, and to permit any
person to whom the Software is furnished to do
so, subject to the following condition:
The above copyright notice and this permission
notice shall be included in all copies or
substantial portions of the Software.
"""
w = Label(root, text=copyright, anchor=W,
justify=LEFT, font='Helvetica', fg='green',
bg='black', wraplength=360)
w.pack()
root.mainloop()
```

Updating the text in a label

It is important to be aware that you can easily associate a variable with a label, so that when the text changes, the label

will automatically be updated. Here is a fragment of code that defines a variable that is used to hold a formatted time string and then allows its current value to be displayed as a label. Whenever the code is executed it will display current system time in hours, minutes and seconds format, as shown in Fig.10.2.


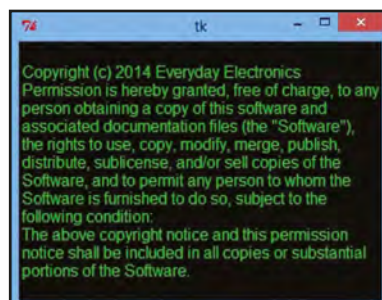


Fig.10.1. The copyright label produced using tkinter

```
from tkinter import *
import time
root = Tk()
v = StringVar()
Label(root, textvariable=v).pack()
time_now = time.strftime('%H:%M:%S')
v.set(time_now)
root.mainloop()
```

Fig.10.2. Label window displaying current time

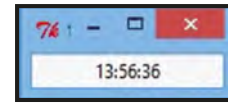

Bitmaps and images

The Label widget can also display a bitmap or an image. When displaying images, the widget's height and width options define the label size in pixels. The following example displays a GIF image as a label showing the sequence of a set of traffic lights (see Fig.10.3).

```
from tkinter import *
import time
root = Tk()
imgfile = PhotoImage(file="traffic_lights.gif")
w = Label(root, image=imgfile)
w.photo = imgfile
w.pack()
```

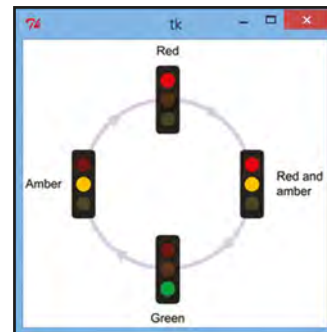


Fig.10.3. Displaying a GIF image in a label

Text and the Text widget

As you've seen, the label widget provides us with a convenient way of displaying text or an image on the screen. The label can only display text in a single font, but the text may span more than one line. The Text widget takes this further and provides us with a much more powerful way of displaying multi-line text, where we can place text in lines and columns and make use of multiple fonts.

The Text widget provides you with an easy way of formatting a text display. It allows you to display and edit text with various styles and attributes. The widget also supports embedded images and windows. The text widget is used to display text documents, containing either plain text or formatted text (using different fonts, embedded images, and other embellishments). It's worth noting that the text widget can also be used as a simple text editor.

By default, you can edit the text widget's contents using the standard keyboard and mouse bindings. To disable editing, set the state option to DISABLED (but if you do that, you'll also disable the insert and delete methods).

Buttons

In previous instalments of *Teach-In 2014* we've used check and radio buttons to provide a way for users to make a selection from one of several options. Conventional buttons provide another method for users to make a choice. Here's an example of how you can display several buttons grouped together in a frame. In a practical application, each button will be given a text string that explains its function. We've also included a function, `quit(self)`, which will allow the user to exit and which will also close the dialogue. Each button has an associated user-defined function (UDF) which is activated when the corresponding button is clicked. In this example program we will just print a message on the console indicating which of the buttons was pressed. If you need to use buttons in your own programs you might find it worth experimenting with

the example code, replacing the user-defined functions, `button1(self)`, `button2(self)` and so on, with your own functions. Fig.10.4 shows how the buttons appear in a Windows environment. Later, we will show you how you can use buttons in a simple Python application for the real-time clock (RTC) module described in *Pi Project*.

```
from tkinter import *

class App:
    def __init__(self, master):
        frame = Frame(master)
        master.wm_title("Select Option")
        frame.pack()
        self.button1 = Button(frame,
text="Button 1", command=self.button1)
        self.button1.pack(side=LEFT)
        self.button2 = Button(frame,
text="Button 2", command=self.button2)
        self.button2.pack(side=LEFT)
        self.button3 = Button(frame,
text="Button 3", command=self.button3)
        self.button3.pack(side=LEFT)
        self.quit = Button(frame, text=" QUIT
", fg="red", command=self.quit)
        self.quit.pack(side=LEFT)

    def button1(self):
        print("Button 1 clicked")

    def button2(self):
        print("Button 2 clicked")

    def button3(self):
        print("Button 3 clicked")

    def quit(self):
        print("QUIT button clicked and window
closed ...")
        root.destroy()

root = Tk()
app = App(root)
root.mainloop()
```

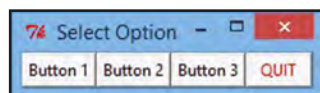


Fig.10.4. Displaying a frame with buttons using Python and tkinter

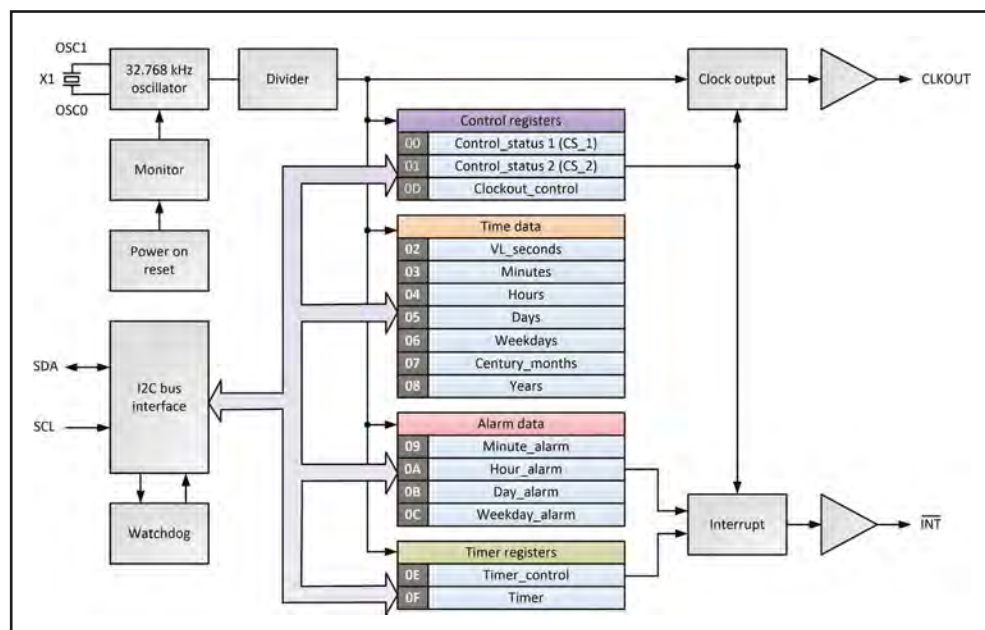


Fig.10.5. Internal architecture of the PCF8563 RTC chip

Pi Project

Last month, we described the construction of an infrared camera/lighting module for use with the Raspberry Pi's NoIR camera. This month, we will be showing you how you can build a real-time clock (RTC) module that can be used as an independent time reference or configured so that it replaces the Raspberry Pi's 'fake' hardware clock. The clock module makes use of a PCF8563 low-cost RTC chip.

PCF8563

The PCF8563 is a CMOS real-time clock (RTC) and calendar chip that is optimised for low-power operation. The chip provides a fully programmable clock which automatically keeps track of the time by storing and updating the year, month, day (and day of the week), hour, minute, and second. The PCF8563 chip is interfaced to a host controller using the standard two-line bidirectional I²C bus (see Part 6 of *Teach-In 2014*). The chip will operate at a maximum bus speed of 400kbps and the internal register address is automatically incremented after each byte that's written to, or read from, the chip. The device incorporates an internal time reference derived from an oscillator and a low-cost external 32.768kHz quartz crystal.

The PCF8563 operates from a supply voltage ranging from 1.0V to 5.5V and demands a current of a mere 0.25µA, or so, when operated from a nominal 3V backup supply derived from a battery or 'super capacitor'. The chip provides a clock output that can be programmed for operation at 32.768kHz, 1.024kHz, 32Hz, and 1Hz. It also offers comprehensive timer and alarm functions.

Register configuration

The PCF8563 contains sixteen 8-bit registers (see Fig.10.5) with an auto-incrementing register address, an on-chip 32.768kHz oscillator with one integrated capacitor, a frequency divider that provides the source clock for the real-time clock (RTC) and calendar, a programmable clock output, a timer, an alarm, a voltage-low detector, and a 400kHz I²C-bus interface. All 16 registers are addressable 8-bit parallel registers, although not all bits are implemented. The first two registers (memory address 00h and 01h) are used as control and/or status registers. Memory addresses 02h through to 08h are used as counters for the time function (seconds count up to years count). Address locations from 09h to 0Ch contain alarm registers that define the conditions for an alarm. Address 0Dh controls the CLKOUT output frequency. 0Eh and 0Fh are the time control and time registers, respectively.

The Seconds, Minutes, Hours, Days, Months, Years as well as the Minute_alarm, Hour_alarm, and Day_alarm registers all store data in binary-coded decimal (BCD) format. When one of the RTC registers is written or read, the contents of all time counters are frozen. Thus errors generated while writing or reading the chip during a carry condition are avoided.

Clock output

A programmable square wave is available at the CLKOUT pin. Operation is controlled by the register CLKOUT_control at address 0Dh. Frequencies of 32.768kHz (default), 1.024kHz, 32Hz, and 1Hz can be generated for use as a system clock, microcontroller clock, input to a charge pump, or for calibration of the oscillator. CLKOUT is an open-drain output and it is enabled at power-on. When disabled, CLKOUT takes on a high-impedance state. Later, we will show you how you can use a simple Python application to access the PCF8563's clock output.

During read/write operations, the time-counting circuits (memory locations 02h through 08h) are blocked. This prevents possible errors if reading the clock and

Table 10.1 PCF8563 register configuration

Register group	Address offset	Register name	Data bit							
			7	6	5	4	3	2	1	0
Control	00h	CS_1	TEST1	N	STOP	N	TESTC	N	N	N
	01h	CS_2	N	N	N	TI_TP	AF	TF	AIE	TIE
Time	02h	VL_seconds	VL	SECONDS (0 to 59)						
	03h	Minutes	x	MINUTES (0 to 59)						
	04h	Hours	x	x	HOURS (0 to 23)					
	05h	Days	x	x	DAYS (1 to 31)					
	06h	Weekdays	x	x	x	x	x	WEEKDAYS (0 to 6)		
	07h	Century_months	C	x	x	MONTHS (1 to 12)				
	08h	Years	YEARS (0 to 99)							
Alarm	09h	Minute_alarm	AE_M	MINUTE ALARM (0 to 59)						
	0Ah	Hour_alarm	AE_H	x	HOUR ALARM (0 to 23)					
	0Bh	Day_alarm	AE_D	x	DAY ALARM (0 to 31)					
	0Ch	Weekday_alarm	AE_W	x	x	x	x	WEEKDAY ALARM (0 to 6)		
Output	0Dh	CLK_control	FE	x	x	x	x	x	FD[1:0]	
Timer	0Eh	Timer_control	TE	x	x	x	x	x	TD[1:0]	
	0Fh	Timer	TIMER[7:0]							

Table 10.2 Example of HOURS data

Hours register (address offset 04h)	Bit					
	5	4	3	2	1	0
BCD data	1	0	0	0	1	1
Decimal equivalent	2		3			
Hours	23					

calendar. When a read/write register access is completed, the time circuit is released again and any pending request to increment the time counters that occurred during the read access, is then serviced. A maximum of one request can be stored; therefore, all accesses must be completed within one second. As a consequence of this, it is very important to perform a read or write access in one complete cycle, reading or writing the data in a continuous sequence from seconds through to years. Failing to observe this rule could result in the time data becoming corrupted. As an example, if the time (seconds through to hours) is set in one access and then in a second access the date is set, it is possible that the time may increment between the two accesses. A similar problem exists with reading; a roll over may occur between consecutive data reads. For example, when reading the minutes from one access and the hours from the next.

In Table 10.1, bit positions labelled 'x' are not relevant, but bit positions labelled 'N' should always be written with logic 0. If these bits are subsequently read they could be either logic 0 or logic 1, but their values have no particular significance. The VL_SECONDS register (address offset 02h) performs the dual function of providing a low voltage (VL) warning by means of bit-7 and also keeping a record of the SECONDS count using bits 0 to 6.

Data encoding

We mentioned previously that time data is encoded in binary format. For example, if the Hours register (address offset 04h) contains the data shown in Table 10.2, then the stored value is equivalent to a binary-coded decimal (BCD) value of 23 hours. Note that only the six least-significant bits (bit-5 to bit-0) are used to store the HOURS count. Finally, it is important to be aware that had the data been interpreted as natural binary rather than BCD the result would be 35 *not* 23!

Clock module

The complete circuit of the prototype PCF8563 RTC module is shown in Fig.10.6. The PCF8563 (IC1) is interfaced to the Raspberry Pi using the I²C bus (see *Teach-In 2014* Part 6 for more information). This requires two signal connections to the Pi's GPIO connector, along with ground (0V) and a +3.3V supply (the Pi's +5V supply must *not* be used). The two I²C single lines are labelled SDA and SCL for the I²C's serial data and serial clock respectively. The pin connections and signal functions for the 8-pin DIL version of IC1 are shown in Fig.10.7 and Table 10.5 respectively.

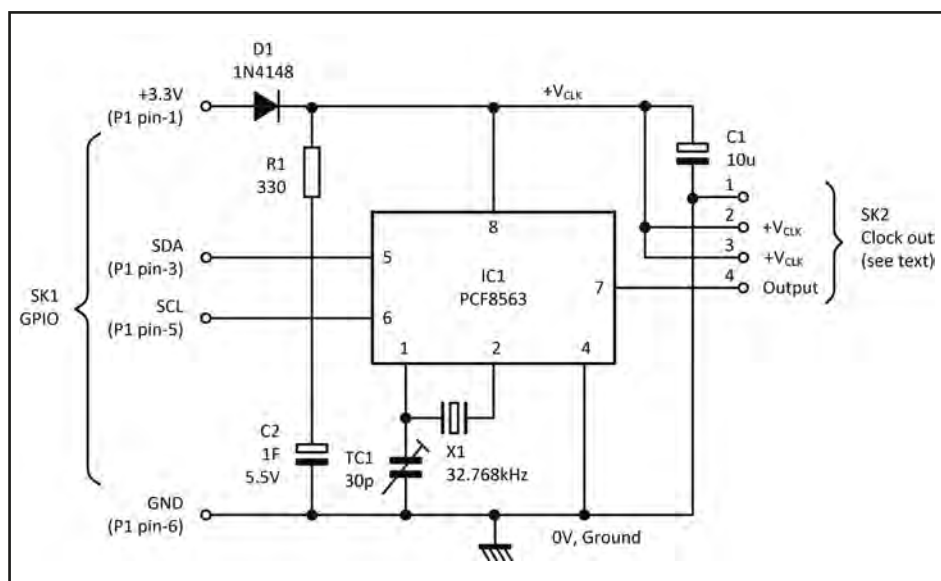


Fig.10.6. Complete circuit of the prototype PCF8563 clock module

Binary-coded decimal

Binary-coded decimal (BCD) provides us with an alternative way of encoding data in a form that can be readily converted from groups of four bits stored in a register. Using BCD, each four-bit group is converted to its corresponding decimal value before the decimal digits are assembled in columns of ascending powers of ten. Tables 10.3 and 10.4 provide you with a comparison of these two coding systems for the decimal numbers 0 to 16. BCD to decimal conversion (and vice versa) is fairly straightforward and can be accomplished with a few lines of Python code, as the following two examples show:

Our first example, BCD converter - 1, accepts an 8-bit BCD-encoded binary string and prints its equivalent decimal integer value. The second example, BCD converter - 2, accepts a decimal integer and returns its equivalent BCD string. Notice how both of these routines are based on user-defined functions and these may be copied and used in your own Python code whenever the need arises.

Table 10.3 Natural binary code

Decimal value	Natural binary
0	0000 0000
1	0000 0001
2	0000 0010
3	0000 0011
4	0000 0100
5	0000 0101
6	0000 0110
7	0000 0111
8	0000 1000
9	0000 1001
10	0000 1010
11	0000 1011
12	0000 1100
13	0000 1101
14	0000 1110
15	0000 1111
16	0001 0000

Table 10.4 Binary-coded decimal (BCD)

Decimal value	BCD
0	0000 0000
1	0000 0001
2	0000 0010
3	0000 0011
4	0000 0100
5	0000 0101
6	0000 0110
7	0000 0111
8	0000 1000
9	0000 1001
10	0001 0000
11	0001 0001
12	0001 0010
13	0001 0011
14	0001 0100
15	0001 0101
16	0001 0110

```
# BCD converter - 1
# Input: 8-bit BCD encoded binary string
# Output: Equivalent decimal integer
# Python 3.x
```

```
def int_to_bcd(x):
    bcdstring = ''
    while x > 0:
        nibble = x % 16
        bcdstring = str(nibble) + bcdstring
        x >>= 4
    return int(bcdstring)
```

```
# Get the BCD value from the user
print("BCD Converter")
user = input("Please enter 8-bit BCD: ")
# Convert the user's binary string to an integer
value = int((user), 2)
# Print the result
print("BCD equivalent = " + str(int_to_bcd(value)))
```

```
# BCD converter - 2
# Input: Decimal integer
# Output: Equivalent BCD encoded string
# Python 3.x
```

```
def bcd_to_int(x):
    binstring = ''
    while True:
        q, r = divmod(x, 10)
        nibble = bin(r).replace('0b', '')
        while len(nibble) < 4:
            nibble = '0' + nibble
        binstring = nibble + binstring
        if q == 0:
            break
        else:
            x = q
    return int(binstring, 2)
```

```
# Get the decimal integer from the user
print("BCD Converter")
user = input("Please enter decimal integer: ")
# Convert the user's decimal string to an integer
value = int(user)
# Print the result and strip the leading 0b
print("BCD equivalent = " + str(bin(bcd_to_int(value))[2:]))
```

Table 10.5 PCF8563 pin connections (8-pin DIL package)

Pin number	Signal	Function/notes
1	OSCI	Oscillator stage input
2	OSCO	Oscillator stage output
3	/INT	Interrupt output (active low, open drain)
4	VSS	0V ground
5	SDA	Serial data (input and output)
6	SCL	Serial clock input
7	CLKOUT	Clock output (open drain)
8	VDD	Positive supply voltage

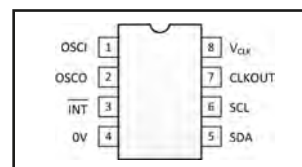


Fig.10.7. Pin connections for the PCF8563 (8-pin DIL package)

GPIO pin number	PCF8563 signal
1	Ground
3	SDA
5	SCL
6	Ground

Table 10.6 GPIO connections for the PCF8563 clock module

Clock reference

The PCF8563 uses an external quartz crystal, X1, to generate its fundamental clock reference signal at 32.768kHz. When divided by 32,768 (2 raised to the power 15) this produces a clock that 'ticks' every second. A low-value trimmer capacitor

(TC1) allows precise adjustment of the 32.768kHz clock. If required, this adjustment should be carried out in conjunction with the PCF8563's buffered clock output (see later) and a calibrated digital frequency meter. The connections to the Raspberry Pi's GPIO connector (P1) are shown in Table 10.6.

The Humble Pi prototyping board

As with many of our other *Pi Projects*, we built our prototype clock module using a Humble Pi prototyping board and the wiring layout shown in Fig.10.8. The Humble Pi prototyping board should be fitted with the 26-way connector (SK1) supplied with the Humble Pi. This connector mates with the male connector (P1) on the Raspberry Pi and it ensures that the Humble Pi board neatly sits piggy-back style above the Raspberry Pi. The pin connections for the clock output connector (SK2) are shown in Fig.10.9, while Fig.10.10 shows the complete Humble Pi prototype clock module.

As pointed out earlier in this series, there have been some recent changes to the pin labelling convention used on Humble Pi prototyping boards. The latest Version 1.3 boards use pin labelling based on the Broadcom (BCM) chip signals, while earlier versions were based on the earlier Raspberry Pi GPIO pin convention. Go to *Teach-In 2014 Part 7* for a detailed explanation of these changes.

Configuring the Raspberry Pi for use with the PCF8563 RTC

In order to initialise your Pi for operation with the PCF8563 RTC chip you will first need to register the RTC chip and allocate an I²C address to it. Assuming you've already set up your Raspberry Pi for use with I²C (see *Teach-In 2014 Part 6*) you will need to enter the following at the command line interface (e.g. LXTerminal):

```
sudo modprobe i2c-dev
sudo modprobe rtc-pcf8563
```

Next, you should set up root access before configuring the I²C adapter for use with the PCF8563 RTC.

```
sudo su
```

The Pi's usual system prompt should change to:

```
root@raspberrypi: /home/pi #
```

For Revision 1 boards, enter the following from the root prompt:

```
echo pcf8563 0x51 > /sys/class/i2c-adapter/i2c-0/new_device
```

Alternatively, if you have a Revision 2 board, you need to enter:

```
echo pcf8563 0x51 > /sys/class/i2c-adapter/i2c-1/new_device
```

If you omit the above commands the PCF8563 RTC module will not be recognised when you next boot the system.

Next, you should check that the RTC has been recognised by the Raspberry Pi. You can do this by entering the command:

```
ls /dev/rtc0
```

If all has gone well the RTC should now be ready for access via the I²C bus. Later, in *Home Baking*, we will show you how to use the PCF8563 RTC module as a replacement for the Pi's 'fake' hardware clock, but before we do that, we will use our new hardware clock as an independent time reference and general purpose clock that can be accessed using some simple Python code.


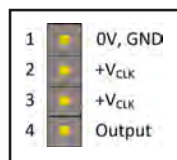


Fig.10.9. Pin connections for the clock output connector, SK2

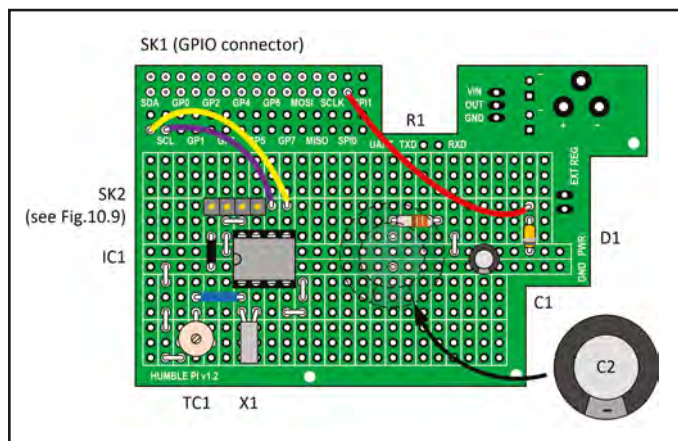


```

# Set PCF8563 clock
# For Python 2.x
from Tkinter import *
import smbus
import time
import subprocess

bus = smbus.SMBus(0)

root = Tk()

labell = Label( root, text="Time HH:MM:SS")
E1 = Entry(root, bd =5)

mytime = "00:00:00"

# Convert a decimal number to BCD
def dectobcd(n):
    bcdstring = ''
    if n < 10:
        bcdstring = '0000'
    for i in str(n):
        bcdstring += bcd digit(i)
    return int(bcdstring,2)
    return hex(int(bcdstring,2))

# Convert to BCD digit
def bcd digit(q):
    p = int(q)
    r = bin(p)[2:]
    return ('0000' + r)[-4:]

# Set the time
def setTime():
    mytime = E1.get()
    timelist = mytime.split(":")
    hours = (timelist[0])
    hournum = int(hours)
    minutes = (timelist[1])
    minnum = int(minutes)
    seconds = (timelist[2])
    secnum = int(seconds)

# Get new data to write back to the PC8563
    sec_data = str(dectobcd(secnum))
    min_data = str(dectobcd(minnum))
    hrs_data = str(dectobcd(hournum))

# Write data to the PCF8562 registers
    command_string = "i2cset -y 0 0x51 0x02 " +
sec_data
    return_code = subprocess.call([command_string],
shell=True)
    command_string = "i2cset -y 0 0x51 0x03 " +
min_data
    return_code = subprocess.call([command_string],
shell=True)
    command_string = "i2cset -y 0 0x51 0x04 " +
hrs_data
    return_code = subprocess.call([command_string],
shell=True)

submit = Button(root, text ="Update clock", command
= setTime)

labell.pack()
E1.pack()
submit.pack(side =BOTTOM)

root.mainloop()

```

Reading the time

The next Python program will allow you to read and display the current time from the PCF8563 RTC module. Once again, the code has been commented so it should be reasonably self-explanatory. In this example, rather than use sub-process calls we will simply read

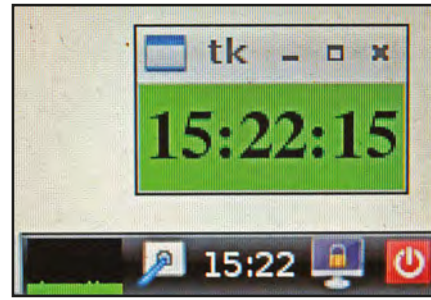


Fig.10.12.
The real time display (note the system clock at the bottom)

bytes from the respective registers within the PCF8563. Fig.10.12 shows the time displayed by this program alongside the system time that appears at the bottom right of the screen. Note that, in this example, the RTC time and system time are independent of one another. Later, in *Home Baking*, we will show you how to link the two together so that the system time is taken from the RTC rather than the Pi's 'fake' hardware clock.

```

# Digital clock using PCF8563
# For Python 2.x

from Tkinter import *
import smbus
import time

bus = smbus.SMBus(0)

root = Tk()
timenow = ''
clock = Label(root, font=('times', 20,
'bold'), bg='green')
clock.pack(fill=BOTH, expand=1)

def tick():
    global timenow
    # get the current local time from the RTC
    bus.write_byte(0x51, 0x80)
    time.sleep(0.1)
    cs1_data = bus.read_byte(0x51)
    cs2_data = bus.read_byte(0x51)
    sec_data = bus.read_byte(0x51)
    min_data = bus.read_byte(0x51)
    hrs_data = bus.read_byte(0x51)
    sec1 = ((sec_data >> 4) & 0x07)
    sec2 = (sec_data & 0x0f)
    min1 = ((min_data >> 4) & 0x07)
    min2 = (min_data & 0x0f)
    hrs1 = ((hrs_data >> 4) & 0x03)
    hrs2 = (hrs_data & 0x0f)

    seconds = (str(sec1) + str(sec2))[-2:2]
    minutes = (str(min1) + str(min2))[-2:2]
    hours = (str(hrs1) + str(hrs2))[-2:2]

    timenow = hours + ":" + minutes + ":" +
seconds
    clock.config(text=timenow)
    # update the clock display every 200ms
    clock.after(200, tick)

tick()
root.mainloop()

```

Using the clock output

The PCF8563's clock output (CLKOUT) can provide a useful test signal and may also be used for other purposes where an accurate and stable reference signal is required. The clock output can be programmed so that it provides a signal at 32.768kHz (the default), 1.024kHz, 32Hz, or 1Hz. This signal is available from pin-7 of the PCF8563, but since this pin is an open-drain connection, an external pull-up resistor is required, as shown in Fig.10.13. The

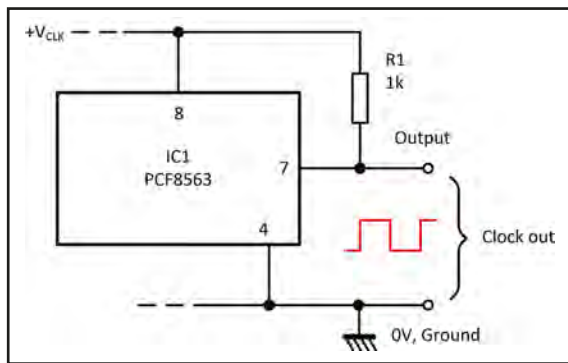


Fig.10.13. Accessing the CLKOUT signal

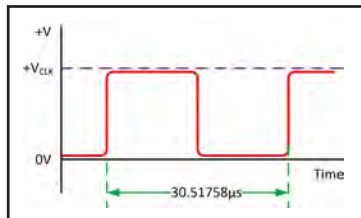


Fig.10.14. The default clock output

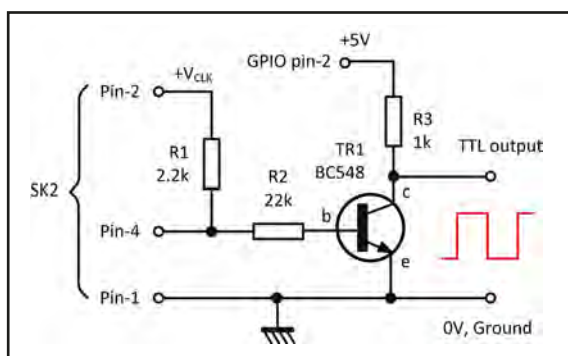


Fig.10.15. Simple TTL-compatible output interface

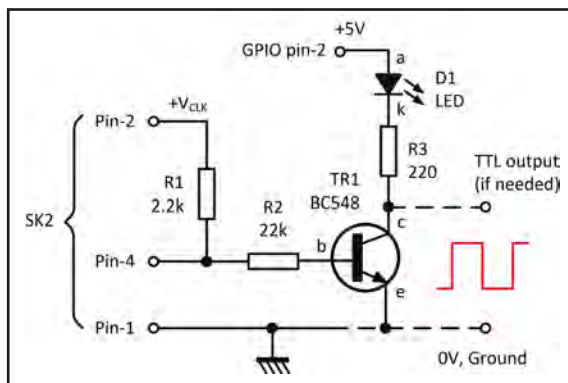


Fig.10.16. Clock-driven flashing LED indicator

CLKOUT takes the form of a square wave with an amplitude equal to the positive supply ($+V_{CLK}$ in Fig.10.6). The output waveform available from pin-7 in Fig.10.13 under the default-programmed condition is shown in Fig.10.14.

In order to produce a TTL-compatible signal suitable for general logic testing (and also for connecting a conventional digital frequency meter) a simple output interface like that shown in Fig.10.15 can be used. Fig.10.16 shows how an LED can be added to the interface in order to produce a clock-driven flashing LED indicator (set the clock output to 1Hz).

Programming the CLKOUT signal

Programming the CLKOUT signal is straightforward and is achieved by sending a data word to the CLK_control register (offset 0Dh).

The clock output can be easily programmed using some simple Python code, as the next



Fig.10.17. User interface for the clock output control program

example shows. Here we have produced a frame with five buttons (see *Python Quickstart*) and used sub-process calls to write the appropriate bit pattern for each clock frequency to the CLK_control register in the PCF8563. Fig.10.17 shows the user interface for the clock output control program.

```
# Set PCF8563 clock output frequency
# For Python 2.x
```

```
from Tkinter import *
import smbus
import subprocess

bus = smbus.SMBus(0)

class App:
    def __init__(self, master):
        frame = Frame(master)
        master.wm_title("Select Clock Output")
        frame.pack()
        self.button1 = Button(frame, text="32.768kHz",
            command=self.button1)
        self.button1.pack(side=LEFT)
        self.button2 = Button(frame, text=" 1024Hz ",
            command=self.button2)
        self.button2.pack(side=LEFT)
        self.button3 = Button(frame, text=" 32Hz ",
            command=self.button3)
        self.button3.pack(side=LEFT)
        self.button4 = Button(frame, text=" 1Hz ",
            command=self.button4)
        self.button4.pack(side=LEFT)

        self.quit = Button(frame, text=" QUIT  ",
            fg="red", command=self.quit)
        self.quit.pack(side=LEFT)

    def button1(self):
        return_code = subprocess.call(["i2cset -y 0
0x51 0x0d 0x80"], shell=True)

    def button2(self):
        return_code = subprocess.call(["i2cset -y 0
0x51 0x0d 0x81"], shell=True)

    def button3(self):
        return_code = subprocess.call(["i2cset -y 0
0x51 0x0d 0x82"], shell=True)

    def button4(self):
        return_code = subprocess.call(["i2cset -y 0
0x51 0x0d 0x83"], shell=True)

    def quit(self):
        root.destroy()

root = Tk()
app = App(root)
root.mainloop()
```

Table 10.7 Clock output configuration

CLK_control (address offset 0Dh)	Bit number								Hex equivalent
	7	6	5	4	3	2	1	0	
32768Hz	1	0	0	0	0	0	0	0	0x80
1024Hz	1	0	0	0	0	0	0	1	0x81
32Hz	1	0	0	0	0	0	1	0	0x82
1Hz	1	0	0	0	0	0	1	1	0x83

Home Baking

In our final *Home Baking* feature we will be dealing with the process of setting and reading the real-time clock and also how to configure your Pi so that it acts as a replacement for the Pi's 'fake' hardware clock.

Setting up the PCF8563 RTC as the Pi's 'real' hardware clock

By default, the Raspberry Pi uses a 'fake' hardware clock, but this can be replaced with a 'real' hardware clock based on the PCF8563 RTC module that we described earlier. Note, however, that when the PCF8563 RTC module is dedicated to providing system clock functions it will no longer be available for use with the Python applications that we described earlier in *Pi Project*.

Manually setting the Raspberry Pi's date and time

Before we begin (and if you've already not done so) it's important to know how to manually set the Raspberry Pi's system clock. This is achieved using the `Linux date` command, which requires super user privileges and needs to be following by a date/time string having the following format:

```
MMDDhhmmYYYY
```

where MM is the month number (01 to 12), DD is the day of the month (01 to 31), hh is the hour (00 to 23), mm is the minute (01 to 59) and yyyy is the year (eg, 2014). As an example, to set the time and date to 10:27 on Monday, 7 April 2014, the required command will be:

```
sudo date 040710272014
```

The system will then echo the date back to you. In the case of our example, this will appear as:

```
Mon Apr 7 10:27:00 BST 2014
```

To read the date from the operating system you can just enter:

```
sudo date
```

This should produce a similar date/time string:

```
Mon Apr 7 10:27:00 BST 2014
```

The hwclock utility

The `hwclock` utility is a program that will allow you to read or set the hardware clock (either the 'fake' clock or from a 'real' hardware clock based on an RTC clock chip like the PCF8563). You can display the current time (using `hwclock -r`), set the hardware clock to the current system time (using `hwclock -w`), or set the system time from the hardware clock. You can also run `hwclock` periodically to add or subtract time from the hardware clock to compensate for systematic drift (where the clock consistently loses or gains time at a certain rate when left to run). Finally, to set the hardware clock to a specific date/time (for example, 16:09 on 7 April 2014), you can use:

```
hwclock --set --date="2014-04-07  
16:09:30"
```

The chrony utility

Chrony provides a pair of programs that work together in order to keep your default 'fake' hardware clock accurate; `chronyc` provides the command-line interface to `chronyd`, a background (daemon) program that uses an external time reference source. These sources can be RFC1305 NTP servers, human (via keyboard and `chronyc`), or the computer's real-time clock at boot time. The background program, `chronyd`, can determine the rate at which the computer gains or loses time and compensate for it while no external reference is present. Using the command line interface, `chronyc`, the use of NTP servers by `chronyd` can be switched on and off to provide support for computers with dial-up/intermittent access to the Internet. The software can also act as an RFC1305-compatible NTP server.

The main function of `chronyd` is to obtain measurements of the true (UTC) time from one of several sources, and correct the system clock accordingly. It also determines the rate at which the system clock gains or loses time and uses this information to keep it accurate between measurements from the reference.

To install chrony you need to use:

```
sudo apt-get install chrony
```

The installation process should, by now, be familiar but note that during installation you will be informed that the NTP server is being temporarily stopped. Messages will then appear informing you that the current version of `chrony` is running and on-line. To start the command line interface to `chronyd` you need to enter the following command (once again using super user privileges):

```
sudo chronyc
```

To check your clock against the time from an NTP server (and also determine the current accuracy of your clock and what's needed to compensate for the error) you need to use the tracking option, as shown in the following example:

```
chronyc> tracking
```

```
Reference ID      : 193.227.197.2 (yikes.bl2.tolna.net)  
Stratum          : 3  
Ref time (UTC)   : Mon Apr 7 09:53:16 2014  
System time      : 0.000000235 seconds slow of NTP time  
Frequency        : 42.852 ppm fast  
Residual freq    : 7.319 ppm  
Skew             : 53.437 ppm  
Root delay       : 0.133704 seconds  
Root dispersion  : 0.089000 seconds
```

Further information on using `chrony` is available from: <http://chrony.tuxfamily.org>. A useful source of information on Network Time Protocol (NTP) is available from: www.eecis.udel.edu/~ntp

Configuring the system

If you've not already set up the Raspberry Pi so that it recognises the PCF8563 RTC connected via the I²C bus you will need to use a similar procedure to that which we described earlier in *Pi Project*. You will first need to enter the following super user commands at the command line interface:

```
sudo modprobe i2c-dev  
sudo modprobe rtc-pcf8563
```

Next, you should set up root access before configuring the I²C adapter for use with the PCF8563 RTC.

```
sudo su
```

For Revision 1 boards you should enter:

```
echo pcf8563 0x51 > /sys/class/i2c-adapter/i2c-0/  
new_device
```

For Revision 2 boards you should enter:

```
echo pcf8563 0x51 > /sys/class/i2c-adapter/i2c-1/  
new_device
```

To set your 'real' hardware clock using the PCF8563 RTC with the current system time you should enter:

```
hwclock --systohc
```

To read the current date and time from the 'real' PCF8563 hardware clock you should use:

```
hwclock -r
```

Finally, to set the Linux/Debian system time to the value in the 'real' hardware clock you can use:

```
hwclock -r
```

Having set up the PCF8563 RTC for use as the system clock (replacing the 'fake' hardware clock with your own 'real' hardware) you will no longer be able to access the PCF8563 using the Python software that we described earlier (or at least until the system is next restarted).

Making the changes permanent

If you are happy with the changes (and don't need to access an independent time reference) you can add the RTC kernel module to the `/etc/modules` list, so that it is loaded whenever the Raspberry Pi boots. Run `sudo nano /etc/modules` and add `rtc-pcf8563` at the end of the list.

Next, create the PCF8563 device at boot time by editing `/etc/rc.local` using:

```
sudo nano /etc/rc.local
```

For a Revision 1 board you will need to add this line to the file:

```
echo pcf8563 0x51 > /sys/class/i2c-adapter/i2c-0/new_device
```

For Revision 2 boards you will need to add this line:

```
echo pcf8563 0x51 > /sys/class/i2c-adapter/i2c-1/new_device
```

Next, add the following line:

```
sudo hwclock -s
```

Note that these lines should appear immediately before the final `exit 0`. Last, it is important to be aware that if you subsequently attempt to access the PCF8563 RTC while it is providing the system clock function you will encounter an I/O error which will inform you that the 'Device or resource is busy'. Because of this you will no longer be able to run the programs that we described earlier in *Pi Project*.



Teach-In 2014 index

A

ADC	4-40
ASCII characters	6-39
ATX power connector	6-45
Accessories	2-41
Alphanumeric input	6-39
Analogue input	4-40
Android VNC	4-47
Apache	7-44
Auto start file	4-45

B

BCM channel	2-45
BCM2835	1-40, 1-41
Base conversion	7-37, 7-38
Binary	7-37, 7-38
Boot	1-43
Browsers	9-37
Bus master	4-42
Bus slave	4-42

C

CPU	1-40, 1-41
CSI connector	1-40, 9-39
CSV file	5-37, 5-41, 5-42
CS0 and CS1	4-42
Calculator	2-41
Calculator mode	1-45
Capacitive loads	2-44
Central processing unit	1-40
Check box	8-43
Chrony	10-44
Clock	1-41
Codecs	1-44
Command line	1-43, 1-45
Comparison operators	2-50
Compiled language	1-45
Config.txt	1-39, 1-43, 1-44
Configuration	1-43
Connector	1-40
Cooling	5-44
Count-down timer	2-49
Counting events	5-38
Creating a new file	4-44
Custard Pi	9-42, 9-43, 9-44

D

DAC	6-40, 6-42
DDNS	7-46
DHCP	7-45
DNS	7-45, 7-46, 8-46
DSI connector	1-40
Darlington transistor	3-42
Data logging	5-41
Debian Reference	2-41
Default password	1-43
Denary	7-37
Dialogue box	9-42
Digital ohmmeter	5-40
Dillo	2-42
Disk image	1-42

E

Emulating the Pi	2-43
Ethernet	1-40
Ethernet lead	1-39
Expander	7-39

F

File creation	4-44
File manager	2-41, 4-44
File object (Python)	5-37

First boot	1-43
For loop (Python)	2-49
Full-step mode	8-38

G

GPIO	2-43, 3-43
GPIO configuration	2-44, 9-40
GPIO connector	1-40
GPIO header	2-44
GPIO initialisation	3-43
GPIO library	2-44
GPIO signals	2-44
GUI	1-41, 1-43, 4-30
GUI dialogue box	9-41

H

HDMI-to-VGA adapter	1-38
HDMI video connector	1-40
HTML	9-37
Half-step mode	8-38
Heatsink	5-44
Hexadecimal	7-37, 7-38
High	2-43
Humble Pi	3-42, 4-41, 7-40, 7-41, 8-41
Hwclock	10-44

I

I/O	1-41
I/O port expander	7-39
I ² C	6-41, 6-42, 6-44, 7-41
I ² C tools	6-41, 7-41
IDC connector	2-45
IDLE	1-46, 4-47
IP address	4-46, 4-48, 7-44, 7-45, 7-46, 8-46
IR camera	9-38
Image viewer	2-41, 2-42
Images	9-37
Infrared emitter	9-39, 9-40
Input (Python)	6-38, 6-39
Interpreted language	1-45
Interrupt	7-39

J

JTAG header	1-40
-------------	------

K

Keyboard	1-39
----------	------

L

L165	6-43, 6-44
LD05V	3-43
LD33V	4-41
LDR	5-39
LED	9-38, 9-40
LED interface	2-47
LED test load	3-43
LXTerminal	2-41, 2-42
Label widget (tkinter)	4-39
Latin Alphabet No.1	6-39
Leaf Pad	2-41
Light level sensing	5-39
Light sensing	5-40
Logic levels	2-43
Login	1-43
Loop (Python)	2-49
Low	2-43

M

MCP23017	7-39, 7-40, 7-42
MCP3008	4-40, 4-41
MCP3202	9-44
MCP4725	6-40, 6-44
MCP4822	9-42
MISO	4-42
MOSI	4-42
Memory settings	1-44

Microcomputer system	1-40, 1-41	Radio button	8-43	Ultra VNC	4-46, 4-47
Microcontroller	1-40, 1-41	Ramp generator	6-43	Unicode	6-39
Microlithography	1-41	Raspbian	2-40, 2-41	Uninstalling software	2-51
Microstep mode	8-38	Raspi-config	1-43, 4-45	Unpickle (Python)	5-37
Midori	2-42, 9-37	Read binary	5-37	Updating software	2-50
Model A	1-38, 1-40	Remote access	4-43	User-defined function	3-40
Model B	1-38, 1-40	Revision	6-44		
N		Revision number	2-45, 2-46	V	
NJM2671	8-39, 8-40	Ribbon cable	2-45, 8-43	VGA adapter	1-38
NORP12	5-39	Root file system	1-43	VLSI	1-41
Net Surf	2-42, 9-37	Root user	3-44	VNC	4-44, 4-46, 4-47
Networking adapter	1-40	Router	7-45	Versions	2-45
NoIR camera	9-38, 9-39	S		Video resolution	1-38
Number base	7-37	SCL	6-41, 7-41	Video settings	1-44
Numeric input	6-38	SCLK	4-42	Virtual network	4-44
O		SD card	1-38, 1-40, 1-42	Voltage regulator	1-41
Octal	7-37, 7-38	SDA	6-41, 7-41		
Operating system	1-41, 1-42	SMB	7-41	W	
Output driver	3-42, 3-43	SPI	4-41, 4-42, 6-41	Wait loop (Python)	2-49
Overclocking	1-44	SSH	4-43, 4-44, 7-44	Web browsers	9-37
P		Scratch	2-41, 2-42	Web server	7-44, 7-46
PHP	7-44	Scripting language	7-44	Webcam	8-45, 8-46
PNG files	9-37	Secure shell	4-43	Wi-Fi	1-39
Passing parameters	3-41	Shutting down	1-44	Win32 Disk Imager	1-42
Password	1-43	Sink current	2-44	Write binary	5-37
Peripheral connector	1-40	Slave address	7-42		
Pi camera	8-43, 8-44	Software	2-51	X	
Pickle (Python)	5-37	Software updating	2-50	X11vnc	4-44, 4-45
Plug and play	1-39	Squeak	2-41	Xpdf	2-42
Port expander	7-39	Stepper motor	8-36, 8-37, 8-38	Z	
Port mapping	7-45	String formatting	5-43	Zip file	1-42
Potentiometer input	4-41	Strings	6-39		
Power supply	1-38, 6-45	Sub-processes	6-42		
Preferences	2-42	Sudo	3-44		
Print function (Python)	5-43	Supply	1-38		
Processes	6-42	Supply voltage	1-41		
Processor	1-40	Switch interface	2-48, 5-38		
Program menu	2-41	System configuration	1-43		
PuTTY	4-43	System tools	2-42		
Python	1-45, 5-39	T			
Python libraries	1-47	TIP31	9-38		
Python modules	1-47	TMP35	5-41		
Python script	1-46	Temperature	5-41		
Python shell	1-45	Terminal	2-41		
Python statements	1-45	TightVNC	4-47		
Python variables	1-46	Timing	5-38		
Python versions	1-45, 5-43	Tkinter	4-39		
Q		Traffic lights interface	2-48		
Quartz crystal	1-40, 1-41, 10-38	U			
R		UDF	3-40, 5-40, 9-41		
RAM	1-40, 1-41	ULN2803	3-42		
ROM	1-40, 1-41	USB battery pack	1-38		
		USB hub	1-39		
		UTF-8	6-39		

Home Baking Quiz – Answers

Finally, here are	1.	b
the answers to	2.	b
last month's Home	3.	c
Baking quiz.	4.	c
If you have	5.	a
managed to score	6.	b
15 or more then	7.	b
we reckon that	8.	a
you've become	9.	c
an experienced	10.	c
Raspberry Pi.	11.	c
Home Baker, but,	12.	c
whatever your	13.	c
score, we hope that	14.	b
you've enjoyed the	15.	a
series and that you	16.	c
get many hours of	17.	c
enjoyment from	18.	a
your Raspberry Pi.	19.	a
	20.	a

ELECTRONICS TEACH-IN 5

On sale NOW from WHSmiths

ONLY
£8.99!

Also available from our Direct Book Service priced £8.99 including P&P

Tel: 01202 880299

Or order your copy from our online shop at:

www.epemag.com

Get ready for

EAGLE V7

Buy now and upgrade for free!

Valid for new license purchases only. Terms & Conditions:
www.cadsoftusa.com/conditions-freeupgrade



Get the answer you've been looking for



Vist the EPE Chat Zone
www.epemag.com

www.rkeducation.co.uk
electronic projects and components

RKAT40



**Prototype PCB designed for
use with Atmel MCUs**

- Designed for use with 40 pin Atmel
- Large prototyping area with power rails
- SO8 breakouts and tactile switch I/Ps
- Power supply circuit
- Interface header for FT232 cable
- ICSP and JTAG headers
- **Only £9.99**

Available now online from,
www.rkonlinestore.co.uk

A wide range of electronic projects are available



Max's Cool Beans

By Max The Magnificent

From San Jose...

I was speaking at the EELive! Embedded Systems Conference and Exhibition in San Jose, California, a few weeks ago. My nametag displayed my name as: 'Max the Magnificent.' In fact, the conference organisers even had me billed with this moniker on seven-foot posters associated with what they called 'The Fantastical Theatre of Engineering Innovation.' What can I say? – if you've got it, then you have to flaunt it!

...to Hawaii

I was run off my feet giving two or three presentations a day on different topics (the real trick is to get me to stop talking). One of the great things when you get to be my age is that you no longer have to wear suits and shirts and ties and suchlike. In fact, I no longer even own a suit; all I ever wear these days is Hawaiian shirts (along with jeans or shorts, of course).

Since you've gotten me on this topic, about a year ago I decided to simplify my life. One of the strange things about Hawaiian shirts is the way they shrink over the years. I know this to be true, because some of the little beauties that used to fit quite comfortably had become uncomfortably tight. Strangely, this also appears to be the case with non-Hawaiian shirts, but this is something I no longer have to worry about because I gave all of mine away.

One weekend, I went through my entire wardrobe with extreme prejudice. It's amazing how hard it can be to let go of things, even if you no longer use them. For example, I'd pick up a jacket and say 'That wasn't cheap, I really should keep it.' But then I'd kick myself and say 'But you haven't worn it for 10 years and you have no intention of ever wearing it again.' The end result was that I piled the vast majority of my wardrobe into the back of my truck and donated it to a local charity shop. I noticed last summer that an awful lot of people in the less salubrious parts of town were sporting Hawaiian shirts.

I subsequently replenished my Hawaiian shirt collection with some newer, larger models. Now my clothes occupy just a small portion of our walk-in closet (much like Mother Nature, my wife abhors a vacuum, so she's been more than happy to expand into the empty space). All I now own, in addition to things like socks and handkerchiefs and suchlike, is two pairs of sneakers, a pair of hiking boots, three pairs of jeans, four pairs of shorts, around twenty Hawaiian shirts, and a handful of T-Shirts. Each day commences with choosing the

Hawaiian shirt *du jour*, which always puts a smile on my face.

I didn't even know I wanted it...

But that's not what I wanted to tell you about. On the way back from the conference, while I was stooging around the San Jose airport, my attention was captured by some flashing LEDs in one of those mini-stores that sells electronic 'stuff' that you didn't even know existed, but having once seen it you know you can no longer live without it.

The product in question was a Bluetooth-based cylindrical loudspeaker about 9-inches tall whose entire surface acted as a multi-coloured spectrum analyser. 'That's interesting,' I thought, so I ambled over to chat with the lad behind the counter. Once I'd managed to drag his attention away from texting his girlfriend, he grudgingly informed me that the speaker in question cost \$199.99. 'Hmmm, it's not that interesting,' I told myself, so I ambled off into the sunset.

...but I did!

But the seed had been planted. Show me a flashing LED, and I'll show you a man drooling. I discovered that I really, really want a multi-coloured spectrogram representation of my music. And not just a piddly little display like that nine-inch loudspeaker. No! I want a man-sized display they requires a truck to transport it from one venue to another. Thus was born the idea for my 'Bodacious Acoustic Diagnostic Astoundingly Superior Spectromatic' (BADASS) display.

Just to give you an idea of where I'm going with this, take a look at some videos on YouTube: <http://youtu.be/LIOUXr9v2RI> and <http://youtu.be/4NJDgvV8RZw> and <http://youtu.be/DUoX9fDibYk>. Come on, you must admit these look interesting.

For my first-pass implementation, I've decided to work with a $16 \times 16 = 256$ array of tri-colored LEDs. As a starting point, I'll be controlling the display itself using my Arduino Mega (<http://bit.ly/1gEbS2r>), and I'll be implementing the columns of LEDs using NeoPixel Strips from Adafruit (<http://bit.ly/1kDOXnd>).

Prototyping the display

Now, before I start constructing a project like this, I first like to throw a rough prototype together out of things like paper and cardboard, as shown in the accompanying photo. In the real implementation, the cardboard will be replaced by a sheet of plywood stained to look like old wood. Meanwhile, the main display panel and the smaller control panel will be formed out of hardboard painted to look like antique brass.



Max in formal attire – poised to start his next presentation

Each of the LEDs will be presented behind a one-inch diameter countersunk brass washer (these look so tasty). The plywood will be milled down so that the hard-board panels are flush with its surface – also, these panels will be attached to the main plywood panel using brass acorn nuts. I want the final display to have a ‘Steampunk’ look-and-feel; that is, I want it to look like it wouldn’t be out of place in a Victorian setting.

I’m actually moving along rapidly with this. I have the NeoPixel strips and the brass washers and acorn nuts; I’ve shaped the hard-board panels; and I’ve routed out the plywood to accommodate these panels. The next step is to drill the 256 holes for the LEDs, along with the holes for the bolts associated with the acorn nuts.

I’ll show you what the final result looks like in my next column. Also, we will start considering how we are going to take the audio stream from my iPad and extract its spectrum data in a form that is suitable for presenting on the display. Until next time, have a good one!



Max holding his cardboard prototype in a ‘Kilroy was here’ pose

**TO ADVERTISE IN
EVERYDAY PRACTICAL ELECTRONICS
PLEASE CONTACT**

Stewart Kearn on 01202 880299

**or email
stewart.kearn@wimborne.co.uk**

TPI

WIDEBAND SIGNAL GENERATOR

35MHz - 4.4GHz !

BUFFERED Reference Output
 External 10MHz Reference Input
 and Internal 1.5ppm TCXO
 Excellent Phase Noise

USB POWERED with both LabView and Tcl
 interface with many powerful features
 65dB Calibrated **LINEAR RANGE** (+10dBm to -55dBm)
 just add a 40dB fixed attenuator for -95dB range

Don't lug around 50 pound units when this unit
 will do what you need for under 1 pound

Buy it today for \$280

FM Modulation
 Morse Code and Beacon Mode for
 Amateur radio and HAM operators

**Mention this Advertisement and we will
 include a FREE USB cable and RF Semi-rigid.**

Email: Robert@rf-consultant.com for details
 and specifications

More Options at www.rf-consultant.com



Project construction – the big picture

THE articles in this series usually focus on one specific area of electronic project construction, but this month an overview of project building will be provided. This should give complete beginners a good idea of exactly what is involved in building an electronic device, the tools and skills required, and whether it is something they would like to try. I think it is only fair to point out from the start that electronic project construction is not really quite like any other hobby. In addition to the skills associated with building and testing the electronics, it contains elements of other pastimes or crafts.

For example, in the course of building electronic gadgets you might need computing, metalworking, general craft, and woodworking skills. Building electronic projects can involve a wider range of abilities than practically any other hobby. Modern do-it-yourself electronic gadgets cover a wide range of applications, including some quite unusual ones, and sometimes a bit of ingenuity and improvisation can be required.

The right ingredients

Having decided to build a project the next step is to obtain all the components. Unfortunately, this is no longer a matter of going along to your local radio and electronics shop with a list of parts. These days the vast majority of electronic components are purchased via mail, telephone, or usually online ordering. The large electronic component retailers such as Farnell and RS Components are primarily suppliers to commercial and educational customers. However, they will supply to private individuals via their online ordering systems, and they represent important sources of supply for amateur users – eBay can also be a useful source of supply. Without Internet access and online ordering it could be impossible to obtain all the components for most projects.

The range of electronic components currently available is truly massive. In fact, it is so vast that it can be difficult for even experienced users to keep abreast of things, and it certainly makes life difficult for beginners. Before actually buying anything it is essential to study some printed or online component catalogues. These contain photographs of components together with a great deal of useful information about them. Familiarising yourself with the main types of electronic components should greatly reduce the risk of buying the wrong thing.

While some electronic components have been available for many years,

and will probably be on sale for many more, some are more ephemeral. Specialised components tend to come and go relatively quickly these days. Some integrated circuits and other semiconductor devices, whether highly specialised in nature or not, are suddenly discontinued. This makes it important to ensure that all the components for a project are still available before you buy any of them.

This is all the more important when building a project from an article that was not published recently. If a project from a few years or more ago requires anything out of the ordinary, it is unlikely that all the components will still be available now. There are specialist suppliers of obsolete parts, and elusive components can sometimes be obtained via auction sites, but the prices tend to be quite high. When ordering the components do not overlook items of hardware such as bolts, battery connectors, control knobs, and the case.

The right one

When selecting your first electronic project it is tempting to opt for something elaborate that will impress your family and friends, but it is more sensible to select something relatively simple and straightforward. It is best to avoid anything that is awkward to build as far as the mechanical side of construction is concerned. With plenty of new things to learn when dealing with the electronics, it is advisable to concentrate your efforts on these and avoid getting sidetracked by the difficult or time-consuming mechanical aspects of construction. Selecting a gadget that has relatively simple electronics minimises the risk of making a mistake and maximises your chances of getting the device to work first time.

Nuts and bolts

Once all the components have been obtained it is time to start building. It does not matter too much whether you start with circuit board or the mechanical side of construction. Here we will consider the ‘nuts and bolts’ side of things first, and this may consist of little more than drilling some holes in the case. The switches, indicator lights, sockets and the like are fitted in these holes. Further holes to facilitate mounting the circuit board in the case might also be needed. The circuit board is then hard-wired to the controls and sockets in the final stages of construction. With modern projects, and especially the smaller types, an alternative approach is often used. The controls and sockets are

fitted at one edge of the circuit board, and their fixings then provide the mounting for the circuit board as well.

If you have a good selection of do-it-yourself tools such as drills, saws and files, these might be all you need when preparing the case for some projects. However, it is likely that before too long some additional tools will be required. It is probably best to buy any additional tools as and when they are required, rather than splashing out on a selection of tools, some of which you might never need.



Fig.1. Small pliers and wire cutters/strippers should be part of the initial toolkit. The wire cutters on the right here can also act as insulation strippers, and can be adjusted to suit various wire sizes

There are some tools that will certainly be needed right from the start, and these include some small electricians' screwdrivers, wire cutters, small pliers (Fig.1 – left) and insulation strippers. Wire cutters and strippers can be obtained as separate tools, but initially an inexpensive combined wire cutter and stripper tool (Fig.1 – right) should suffice. Use the right tools and do not improvise with scissors, penknives, or whatever, as this is likely to harm the tools, the wires, and yourself! If your fingers are not particularly nimble it is worth obtaining straight and angled tweezers (Fig.2), which can make life much easier when dealing with tiny components.

Holes in metal and plastic cases are made using HSS twist drills, and the woodworking variety is unlikely to be of much use in the current context. Provided they are used carefully, medium or even low-cost drill bits are adequate for use on aluminium and plastic cases, which are relatively soft materials. Good quality drill bits are needed for work on steel panels. A power drill is suitable, but ideally it should be mounted in a good quality drill stand. A small cordless power drill or even a hand drill is often a better choice for what will usually be small scale work. A set of miniature files ranks as one of useful things to have when working on cases. Any holes that are not quite right can be 'fine tuned' using these tools, and they can also be used to make rectangular and other non-circular mounting holes.

In the likely event that no dedicated work room is available, it will be necessary to resort to a garage, kitchen, or anywhere that can provide a reasonably large and well lit area with a table or workbench. When using a part-time work area it will probably be necessary to improvise a temporary work surface from a piece of MDF, plywood or



Fig.2. Angled and straight tweezers can be very useful when dealing with miniature components


chipboard so that damage to the tabletop is avoided. The work area should always be thoroughly cleaned once the work has been completed. This is particularly important after working on steel cases, since any pieces of swarf produced are likely to have some sharp edges.

Anti-zap

Before starting on the electronic side of project construction it is important to realise that many modern semiconductors are vulnerable to damage from static charges in the environment. We are not necessarily talking in terms of large charges that produces noticeable sparks and 'clicks' as they discharge. Some semiconductors can be damaged by relatively small charges that give no obvious clues to their existence. There is insufficient space available here for a detailed description of anti-static handling precautions and equipment, but a few simple rules should be observed.

If in doubt, always assume that a semiconductor is a type that is easily damaged by static charges. Handle semiconductors as little as possible, and try to avoid touching the leads or pins. Semiconductors are normally supplied in some form of anti-static packaging, and they should be left in this until it is time to fit them on the circuit board. Keep semiconductors away from any likely sources of static electricity, and do not wear clothes that are known to be prone to static generation when constructing circuit boards. Earthed wrist bands are available from electronic component suppliers and from shops that sell computer parts. Any static charge in your body is quickly leaked away to earth when you wear one of these. They are not expensive and it is worth having one of these as part of your initial tool kit. If you build electronic gadgets more than very occasionally it is worth obtaining an earthed mat for the work area.

All or most of the electronic components are fitted on a board that is made from an insulating material such as fibreglass. The board has holes to take the pins and leads of the components, and in its most simple form there are copper pads and tracks on one side of the board. The components are mounted on the opposite surface of the board, which is generally considered to be the top side. The leads are trimmed to length before they are soldered to the copper

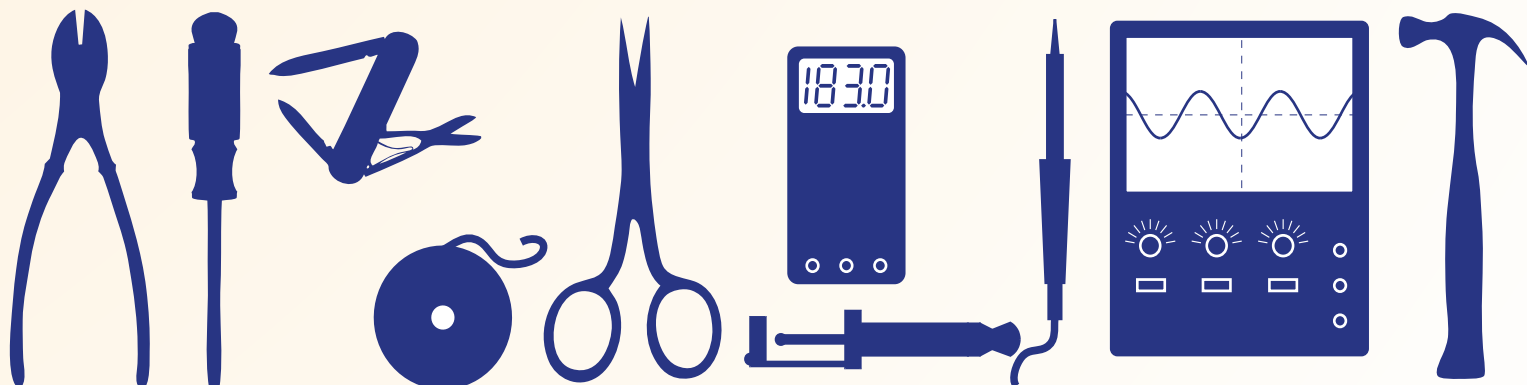

pads on the underside of the board. There are no connecting wires as such, but the copper tracks on the underside of the board carry all the required interconnections.

This is the fundamental type of printed circuit construction, and there are some variations on this basic scheme of things such as double-sided boards. These have copper tracks on both sides of the board, but in most cases the components are still fitted on one side. Additional holes carry connections through the board, and the connections weave across the board, crossing over other tracks and avoiding unwanted connections to them. Another type of board lacks holes for the pins and leadout wires, and is used with special surface mounting components that are soldered onto the copper pads (Fig.3). A further variation uses a combination of conventional printed circuit and surface-mount construction. Due to the minute size of the components, any form of surface-mount construction is not a good starting point, and is probably best avoided by beginners.

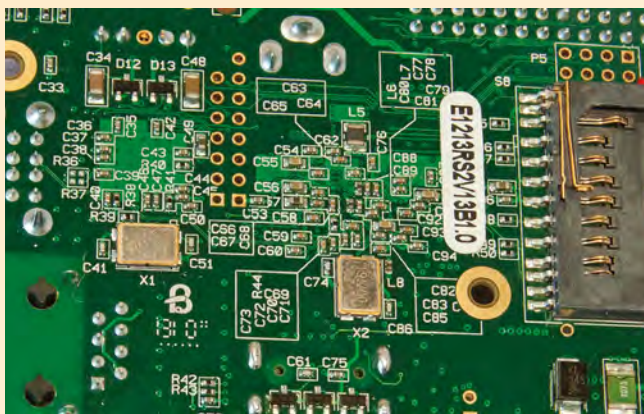


Fig.3. Part of a complex double-sided board that has components and tracks on both surfaces. Projects that use surface mounted components are not a good starting point

A normal printed circuit board is only suitable for one particular circuit, but there are various types of proprietary printed circuit board that are designed to accommodate practically any circuit. Stripboard (Fig.4) is the only one of these that is currently used to any extent for electronic project construction. It is a single-sided board that has numerous small holes on a 2.54mm x 2.54mm matrix. Copper strips on the underside of the board run along the rows of holes for the full length of the board.

Stripboard is used in the same basic fashion as a custom single-sided board, but it is usually necessary to make breaks in some of the copper strips so that they can handle more than one set of interconnections. Link wires are normally needed on the component side of the board to connect various copper strips. In fact, link wires are sometimes needed with custom boards, and they provide a simple alternative to using relatively expensive double-sided boards. Stripboard is less straightforward to use than a custom printed circuit board, giving more scope for making errors. Initially it is probably better to opt for projects where you can use a ready-made custom board.

Hot stuff

Good quality soldered joints are needed to make reliable electrical connections between the various electronic components, and to give the circuit board physical resilience. There is no need to use an expensive thermostatically controlled soldering iron, an inexpensive iron with a rating of about 15W to 20W is sufficient. It should be fitted with a small bit of about 2.0-2.5 millimetres in diameter. For safety reasons the iron should have a proper stand, and this will also act as a heatsink to prevent it from overheating. It should be possible to obtain a soldering kit that includes a small soldering iron, a matching stand, and some solder of the appropriate type for electronic work.

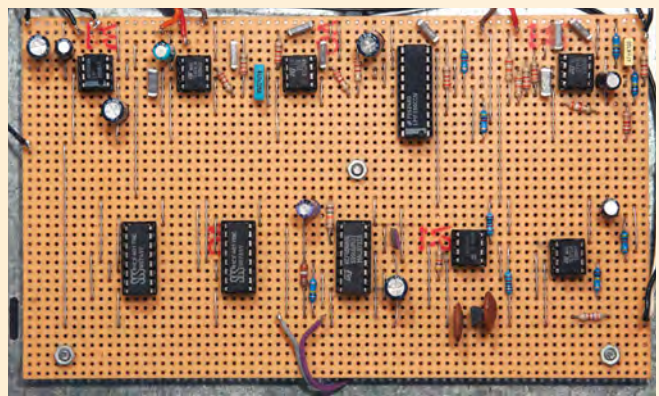


Fig.4. The top side of a circuit board based on a piece of stripboard. The copper strips run horizontally on the other side of the board

A guide to soldering goes beyond the scope of this article, but there is an excellent soldering guide by Alan Winstanley available on the EPE website, and any soldering kit will almost certainly come complete with detailed instructions. I would definitely advise against starting construction of a circuit board without gaining some soldering experience first. Obtain some stripboard and a few cheap resistors and practice soldering before moving on to your first project.

Finishing touches

With the completed board fitted in the case, it is just a matter of adding any remaining wiring. This is sometimes termed the 'hard wiring', and it is perhaps less straightforward than building a circuit board. The article should include a wiring diagram that clearly illustrates each connection, and there should be no problems provided this is followed carefully, making sure that no wires are omitted. A thin insulated multi-core wire such as the 7/0.2 type (seven cores of 0.2mm wire) is suitable for most connections. A heavier type, such as 16/0.2 is needed for wiring that carries higher currents, and it is advisable to equip yourself with both types of wire right from the start.

Double check

Avoid the temptation to immediately switch on a newly constructed project. Checks for errors should be made as construction progresses, but it is still a good idea to thoroughly check the finished unit before testing it. Provided you build a project carefully it will probably work first time, but there is bound to be the occasional project that is reluctant to co-operate. The problem is usually caused by a minor mistake somewhere, and some further checking will usually get things sorted out. You are then ready to start looking for your next project!



Laser

Why tolerate when you can automate?



X-10
Home Automation



C-Bus Shop
C-Bus and
C-Bus Wireless



KAT5
KAT5 AV transmission
and IR control system



Barix
Barix Ethernet based
MP3, communications
and control systems

www.laser.com

*Integrators, Installers, Trade
and Retail customers welcome*

www.cbushop.com

Laser Business Systems Ltd
Tel: +44 (0) 20 8441 9788
Fax: +44 (0) 20 8449 0430
Email: info@laser.com
16 Garthland Drive, EN5 3BB

Revisiting the kitchen timer

AFTER many months of hardware and software development we approach the original intended destination of these articles – a development board supporting the 'C' programming language, with a decent software development environment. It's still a good environment for writing assembly language programs, but the PIC18F processor family lives in an interesting 'sweet-spot' of low power, low-cost, easy-to-solder devices that can be used effectively with 'C', and that's what we are going to concentrate on for now.

This month, we re-visit the kitchen timer application created last year and re-engineer it in 'C', in part to see what the difference a high level language makes to the code size, and also to see just how much easier the development process is (you may remember us commenting on how laborious it was, coding the user interface in assembler.)

To set the scene, a quick reminder of how the kitchen timer works. The original assembly language template files were extended by adding the file **kitchen.asm**, which holds the logic of the application. **Interrupts.asm** was modified to include the use of a timer decrement routine **decTimer**.

The **lcd.asm** file was extended to include routines to convert binary values to ASCII, and display them as two digits on the LCD display.

The **main.asm** file has a very small change – placing the processor in sleep mode when the timer is inactive, and otherwise just calling the application's 'handler' routine, which gets called either every two seconds when the timer is inactive, or constantly when it is running:

```
call    kitchenInit

mainloop:
    call    timerAsleep
    btfsc   STATUS, Z
    sleep
    call    kitchenHandler
    goto    mainloop
```

Creating the application

We start by creating a copy of the template 'C' project files, including the main directory that ends with the characters '.X'. The template files were created as part of June's article, and can be found on the magazine's website. Once you have copied the files, rename the .X directory to something meaningful, such as **kitchen-C.X**. Always keep the extension '.X' the same – it is required by MPLAB-X.

Run MPLAB-X, and once it has started up close any open projects (File->Close All Projects) and open the project that is in your new directory. The project itself will still be called by the old name 'template', and you should change that by right-clicking over the project name in the Projects explorer tab (it has a small IC icon next to it) and then, from the drop-down list, select 'Rename...' Fig. 1 shows what we mean. Give the project the name '**kitchen-C**'.

Next, we add the two new files to the project; **kitchen.c**, and its header file **kitchen.h**. To do this, right-click over the line 'Header Files' within the Project explorer tab, select 'New', and then 'C Header File'. Give the file the name **kitchen**, and select 'Finish'. Next, right-click over the line 'Source Files', select 'New', and then 'C Source File'. Give the file the name **kitchen**, and select 'Finish'.

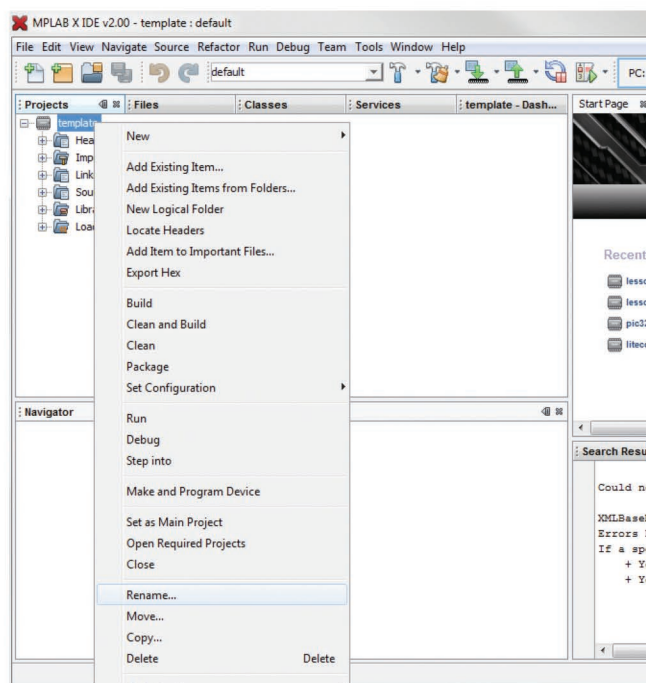


Fig.1. Renaming a project

Now we have our project source files generated, the next thing we do is create the three functions **kitchenInit**, **timerAsleep** and **kitchenHandler**. The **kitchenInit** and **kitchenHandler** routines do not take any parameters nor return any, so their function definitions in **kitchen.h** are very simple:

```
void kitchenInit(void);

and

void kitchenHandler(void);
```

The function **timerAsleep** returns a value indicating whether the timer is running; it only needs to be a yes/no indication, so we will use a single unsigned character type:

```
unsigned char timerAsleep(void);
```

These three functions were added to the new source files, with no code inside them – **timerAsleep** set to return a dummy value of zero, as it must return *something*, or the compiler will complain that you have made an error. We will fill the proper code in shortly.

Back in the file **main.c** we add an include directive at the top of the file to make use of the kitchen application functions:

```
#include <stdio.h>
#include <stdlib.h>
#include <pic18.h>
#include 'config.h'
#include 'timers.h'
#include 'interrupts.h'
#include 'hardware.h'
#include 'kitchen.h'
```


and add the calls of the kitchen application handler, mimicking the assembly language version:

```
kitchenInit();

do {
    if (!timerAsleep())
        SLEEP();
    kitchenHandler();
} while (1);
```

That's it for **main.c**. Let's take stock of the resource utilisation so far, looking on the dashboard tab of the project explorer window in MPLAB-X: 33 bytes of RAM used, and 720 bytes of Flash. The assembly version of the complete kitchen timer used 16 bytes of RAM and 1830 bytes of Flash. So we have blown our RAM budget already, and we haven't even started!

The next port of call was **hardware.c**, fleshing out the **HardwareInit** routine. The assembly language version is littered with instructions changing the RAM memory bank, as various SFRs in different banks are configured. It's so nice not having to care about which memory bank an SFR is in with the 'C' language; the compiler handles this for us, and never makes the mistake of forgetting to change the bank registers. That feature alone is a good enough reason to use the 'C' language!

Only a few, minor changes were required to the **interrupts.c** file, leaving just **kitchen.c** and **lcd.c** to be updated.

The original **lcd.asm** had various functions for displaying binary data; we will take a simpler approach, and make use of the 'C' Library's **sprintf** function to convert data into a string. All we need to provide is a raw string print routine. This is a very simple piece of code, that make use of the **LCDWrite** function:

```
void LCDWriteStr(unsigned char *ch)
{
    while (*ch)
        LCDWrite(ch++);
}
```

We also added two functions to turn the cursor on and off.

So now it was time to focus on the main application file, **kitchen.c**.

The keyboard functions were easy to translate directly into 'C', but we now had a decision to make: how to store, increment, decrement and display the timer value. There are three common approaches, each with their positives and negatives:

Store the value as BCD

This is the approach we took in the original implementation, and it works well in assembly language. The code is a bit fiddly to write, but is fast and efficient on code size.

Store the timer as a single decimal value

Here, we store the timer value as the number of seconds in a single, unsigned long variable. This storage method will be the easiest to manipulate, but requires some slightly more complex maths to display the value as three separate values.

Store the timer as three separate values

Here, we store the hours, minutes and seconds in their own unsigned char variables. This is slightly more complicated to store and manipulate (you have to handle the 'carry' from 59 to 00 for example) but it is slightly easier to display.

The second option appears to be the best approach; It's better to *store* data in the most appropriate format. Converting the single value to a display string is not that complicated, and although it won't be very quick, it will certainly be quick enough. Plus, the 'C' programming language has several features and functions to help us with the conversion.

So, we create a variable thus:

```
unsigned long timerVal = 0;
```

The implementation of the **decTimer** function now looks like this:

```
unsigned char decTimer(void)
{
    return (--timerVal);
}
```

That's a single line of code, compared with 80 lines of assembler!

Moving on to the display of the timer, that is just two lines of code now:

```
sprintf(line1,timeStr, timerVal/3600,
(timerVal/60)%60, timerVal%60);
LCDWriteStr(line1);
```

Now, here is the rub – those two lines of code tripled our Flash memory usage to 4860 bytes! The reason for this is the use of the **sprintf** function; we had not used that before, so the compiler added the code for that function into our project. **sprintf** is a 'Swiss army knife' function, it can convert all kinds of data formats to strings, and that flexibil-

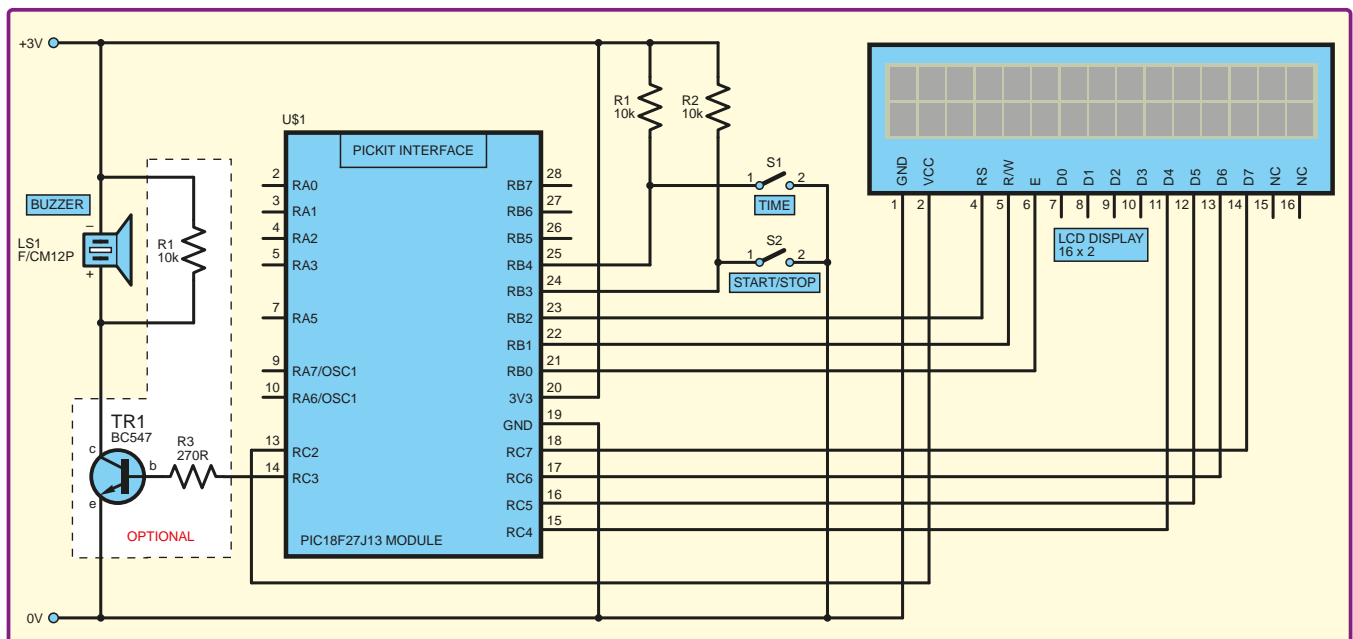


Fig.2. Circuit diagram matching the template files

ity comes at a cost: code size. The good news, however, is that this is a one-off cost; The next time we use `sprintf` the same copy will be used, so the program won't grow in size so much.

Converting the final function, `KitchenHandler`, went reasonably smoothly, taking about 30 minutes to complete. There were several bugs found in the subsequent tests, but these were quickly identified and fixed using the PICKIT3 debugging capabilities.

So in the end, the program took 137 bytes of RAM (compared to 16 bytes for the assembly version) and 6702 bytes of Flash (compared to 1830); over three times the size.

Although a relative size comparison looks bad, one has to remember that this is a small project. For a bigger project, the gap converges a little, as the relatively large C language library functions included in our project get re-used. The main difference, however, is the effort involved. Creating the 'C' version of this project was trivial, and it will be a lot easier to understand than the assembly version (go ahead – compare the two!)

Fig. 2 shows, again, the circuit used for this project – the same as before.

'C' Startup

One of the questions that comes up time and time again is: 'how does the processor know to transfer control to the `main()` function on startup?'

It's a great question, an obvious one to those of us used to programming in assembly language; we know that the processor starts at the reset vector (0x0000 on the PIC) and we are immediately in control of the processor from that point. So who or what is causing the processor to jump to the `main()` function?

With the 'C' programming language, the compiler provides some code to

us that performs a little housekeeping following the power-on reset. That code is called 'cstartup' (or 'crt0' by some compilers,) and is responsible for initialising our global variables to a defined state – either zero, or a value we specified in the code. Something has to do it!

Some compilers provide different versions of `cstartup`, enabling you to reduce the language overhead even further if you need to (you can disable bss initialisation and variable loading in MPLAB-X if you wish) but care should be taken when modifying the normal 'C' language features. Things may not work as you expect.

The source code for this project can be downloaded from this month's section of the magazine's website: www.epemag.com

Next month

Next month, we introduce some SPI communication routines into our template code, and demonstrate using them to hook the board up to a low-cost colour LCD panel.

Kickstarter

As I write this article, the Kickstarter project is in its final hours of 'funding.' After launching 45 days ago over 400 boards have been ordered by 186 people – many thanks to everyone who has joined in. Going through the Kickstarter project – developing the idea, creating promotional media, answering questions – has been a fantastic learning experience and I can't wait to do another!

Not all of Mike's technology tinkering and discussion makes it into print. You can follow the rest of it on Twitter at @MikeHibbett, and from his blog at mjhdesigns.com

Technobots

Electronic & Mechanical Components

Est. 2001

Components
Project Kits

Motors
Controllers



Controller Boards
Sensors

Electronics

Bearings
Couplings

Wheels
Fixings

Gears
Tools

Shafts

Sprockets



Mechanical

New Website!

MFOS Analogue Synths
Amplifiers



Soundtronics

Livid Instruments
MIDI Thru Box



MIDI Keyboards

Technobots Online has recently expanded into three brand new websites, each focussing on an area of our products. The first to be launched is Soundtronics, fulfilling all of your audio needs. The range of products available will continue to grow, we currently stock:

MIDI - Microphones - Speakers - Connectors - Leads
Amplifiers - Audio Switches - Sounders - Test Gears
Tools - Knobs - Hardware - Storage - Headphones

Visit the new website for full product listings:
www.Soundtronics.co.uk

sparkfun.
ELECTRONICS
MFA/COMO DRILLS

Pololu
Robotics & Electronics

Official orders from UK Schools, Colleges and Universities welcome.

Kitronik

MaxBotix
Canakit
Electronic Kits & Modules

www.technobotsonline.com

With over 8,300 products available to order online, Technobots provides one of the widest ranges of components available to the electronics and engineering enthusiast.



Looking to advertise?




Contact Stewart Kearn on:

01202 880299

or email

stewart.kearn@wimborne.co.uk

AUDIO OUT

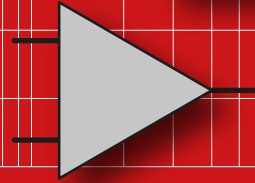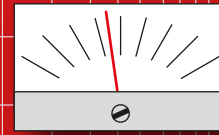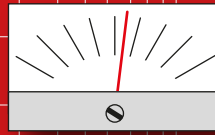

By Jake Rothman

Working for yourself in electronics

Jake Rothman is an analogue electronic music technology designer, lecturer, science communicator, and manufacturer. He studied and graduated in the 1980s with an HND in Electronics for the Music Industry, and later received a teaching certificate. He has designed valve amplifiers and Theremins, and written numerous articles for *EPE* and *The Modern Electronics Manual*. Here, he describes the trials, tribulations and rewards of running a small electronics business for the last 23 years.

Microbusiness

No, I'm not talking microprocessors here, a microbusiness is a very small business, usually consisting of one person or a sole-trader. My company designs and manufactures Colorsound guitar pedals, Theremins and all manner of hand-made boutique 'music tech'. I'm located in a part of Wales where big private-sector employers are rare and microbusinesses form a large part of the economy.


Self-employed, or self-delusional?

I was possibly deluded when I went fully self-employed, like most entrepreneurs I was irrationally over optimistic. I gave up my university lecturing and property in the south of England and left for pastures new. That was the trouble, the endless fields; I fell asleep at the wheel a couple of times coming back from lecturing on The University of Glamorgan's Music Tech BSc, a 140-mile round trip. So I decided to go self-employed full-time.

That was a conscious decision, but of course self-employment can happen at any time if you lose your job. Either way, multinational financial services company Morgan Stanley says 80% of all employment gains in the UK since 2007 have been in self-employment.

Word to the wise

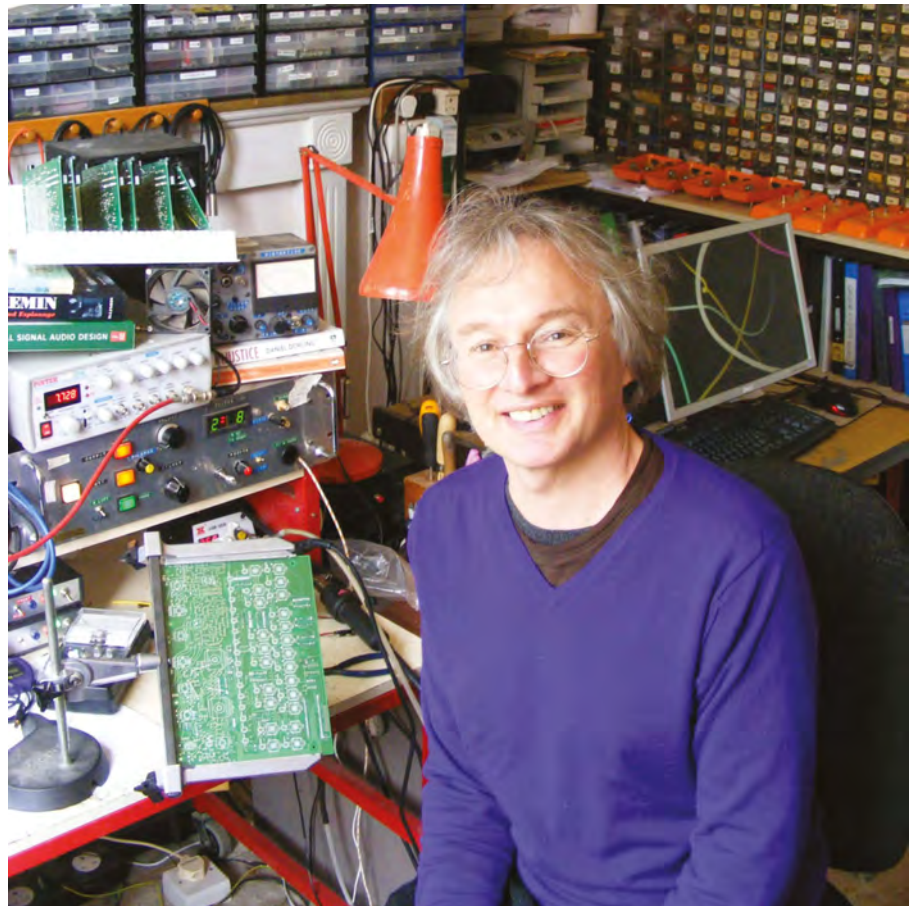Being self-employed is no picnic, and unless you hit upon a wildly successful product or idea, then it's certainly no



Jake Rothman at home in his office / workshop / general business HQ

route to riches. In fact, you are likely to earn less than working for a good employer. However, it can be very rewarding being your own boss and running your own business. You do get nice little extras – all your purchases for the business are tax-deductible expenses, including your *EPE* subscription! So despite earnings being low, if it's a choice of designing a new guitar effect or selling insurance for £6.30 an hour, I know what I would rather do.

Working in electronics

Electronics is still one of the best areas for self-employment, since it is infinitely scalable – from stuffing PCBs in your bedroom to building another Foxconn in China. It has real

advantages over, say bricklaying, because you can leverage your work. For example, if I design a good pre-amp circuit I can put it in several products: an article in *EPE* and then use it in a lecture (put on the net for publicity of course). Finally, I might use it as a demonstration prop on 'Lab in a Lorry' for the Institute of Physics when I work as a STEM (science, technology, engineering and mathematics) ambassador to enthuse school children. Hence, it's possible to get paid at least five times for the same piece of work. Later on, I may be the only person who can fix it, generating more revenue!

On the production side, I prefer doing R&D and testing, so I tend to out-source PCB assembly and the drilling

of cases. However, I still do an hour of tidying and a couple of hours of administration a day. Also, one's home/workplace has to be heated all day – there are many such overlooked tasks and costs when being self-employed.

Intellectual property

Large companies can afford to patent designs, and, more importantly, enforce the patents. I often just have to be content with a few sales and basking in the glory of seeing a successful artist, such as Alison Goldfrapp, use one of my circuits. It can be useful to put a design into a journal, since it can prove you did it first. I have used this to protect myself when some large corporations have accused me of infringing their patents. But publishing a circuit will probably end any hope of a patent; I often wonder how the late Peter Baxandall felt every time he saw an amplifier with bass and treble controls, knowing he had put the circuit in *Wireless World* in November 1952.

Hoarding and advertising

The Internet has greatly reduced the amount of space needed. I used to have hundreds of catalogues and data sheets, now I just use Google. It is the same with components – just a few clicks and a part arrives the next day. Actually, that's a bit of a fib! Since I do retro 1970s analogue electronics and being an ancient 51, I store vast amounts of cellulose-based data and obsolete components. But it doesn't have to be that way for you!

One of the best forms of advertising is via your own website, and if you have the right skills you will get noticed, as one link leads to another. Specialised technologies now have a global reach, so there is room for almost any unique service. Find a stable niche where there is no competition and you can do well. On the other hand, if Yamaha or China do it, forget it.

Discrete hand-made electronics is an artisan craft. Most mass-produced stuff is often just 'clip-art' soldered together. Funding large tooling costs and surface-mount PCB runs is now easier with new business models based on crowdsourcing. There is always somebody to be found doing kits and parts for desirable old products, long out of production. An example would be the Roland TB303 Bass Line by adafruit.com

Oh my RoHS!

Along with the liberation of the net, have come increased costs due to regulation, such as RoHS. The requirement to use lead-free solder has

been a real disaster for my field, since my products are expected to last 30 years and are priced accordingly. Unleaded solder is fragile and has poor wetting, resulting in shorter life, especially where single-sided PCBs are used with through-hole components. Unlike military electronics, the professional audio industry never did sufficient lobbying to get an exemption. Now, European regulation treats us like we make musical Christmas cards that go straight into the waste stream. There is no such thing as an RoHS-compliant germanium transistor, and old components generally need to be soldered with SnPb solder. All I can do is get the leads treated to get the lead tinning removed at huge cost, convert all the PCBs to plated-through-hole and hand solder in a pure nitrogen atmosphere.

Safety is also paramount when selling to the public, especially when it comes to mains wiring and power supplies. At first, I avoided this issue by buying in approved 'wall-wart' PSUs. The CE emissions side I got round by documenting how I took measures to comply, effectively self-declaration. I finally got a fellow lecturer at a university to put my Theremins through their EMC testing facility.

Inflation

As far as start-up costs go, a home-based electronic business is cheap to set up. Most people already have a computer, printer, Internet connection and domestic hand tools. The basic additional workshop stuff for hardware development, soldering iron, side cutters, multi-meter, power supply, 'scope, signal generator and drawers full of general components, will generally come in at less than £1000. Since analogue electronics is a mature technology, there is plenty of second-hand equipment and NOS (new old stock) components available. Many a time I have set up students with the complete workshop contents of a deceased Radio Ham, often called a 'silent-key' sale at radio rallies.

There is, however, the spectre of rising costs in electronic parts for the first time in 30 years. The deflation in component prices enabled me to



New old stock – NOS – is a great way to bulk buy cheaply

hold and even reduce prices for years. Those days are now over, as anyone who has ordered from the big distributors recently will realise. Traditional analogue parts, such as pots, switches, solder, cable and tools, based on my invoices, have gone up 40% in the last few years. Surprisingly, Farnell will negotiate and Rapid also give me end-column prices because I buy every month. I've also sent a few college accounts their way. One new supplier I'm using is Tayda, who are very good value for guitar pedal parts.

Even Chinese electronic costs are now inflating, killing with it the throw-away culture, and allowing repair businesses to become viable again. Analogue music gear is now expensive and desirable – like a good mechanical chronometer – and of course consumers expect it to last, just like well-made furniture.

Tantalising tales

Ironically, I recently bought a boot load of AVX and Kemet tantalum capacitors from the Flight Refueling radio-rally destined for land-fill because they were non-RoHS. I thought surely it is better they be used in some audio gear for 30 years first before they become toxic waste? After all, I was constantly replacing dried-up wet electrolytic capacitors in pro-audio gear and motherboards as part of the repair side of my business. Identifying such failed caps is easy, half the failures are visual and the others can be identified with a Peak ESR meter. The capacitor 'plague' affecting Taiwanese electrolytics, where an industrial spy forgot the corrosion inhibitors in the formula he stole from the Japanese, didn't help either!

Next month, I'll talk about 'how I got the wet electrolytics out of my designs' and knocked the failure rate right down.

Parallel batteries

ATHOUGH most *Circuit Surgery* articles are based on posts in the EPE Chat Zone (www.chatzones.co.uk) we are also happy to receive questions or suggestions for topics by email (editorial@wimborne.co.uk) and will use them if they are suitable, like the following email from Godfrey Manning.

The question is about power supplies in parallel. I've drawn batteries for simplicity, but it could be regulated DC supplies, transformer secondaries in parallel, etc.

The batteries represent perfect voltage sources and the resistors above them are their internal impedance. I've got both supplies (batteries) in parallel and feeding current into a load resistor (the rightmost resistor). The required nominal supply voltage appears at the measuring point.

Assume the internal impedances are low and similar. Let's start with the off-load voltage from the left battery being very much greater than that of the right battery. To my mind, that's a battery charger. The leftmost battery will charge the right-hand one.

Now alter the batteries until they are closely similar in voltage and assume the small internal impedances are also closely similar. These power sources tend to share the current demanded by the load resistor (Kirchhoff's law applies as always).

It's as if, at some point in the experiment, the rightmost battery's increasing volts now become so similar to the left-hand battery's that current flows out of both and goes into the load. This is a reversal of the current going out of the left battery and into the right-hand one in order to charge it.

How is this calculated? At what point does load-sharing begin, as distinct from the right lower-voltage battery itself loading (drawing charging current from) the left battery?

Paralleling of power sources is a common practice. It provides additional current capacity which is not available from an individual unit, whether that is a small battery cell or a large AC generator. As indicated in Godfrey's question, parallel (voltage) power sources must be matched, balanced and synchronised in order for the combination to be an efficient and effective power source.

Avoiding damage

The point at which the sources are first connected together is important as significant mismatch may result in excessive currents and consequent damage. This is even the case if there is a possibility of eventual self balancing, for example, via battery changing, as described by Godfrey. For DC sources, matching is primarily about the voltages not being too different. For transformers (AC output) the voltage and phase must match. This was discussed recently in *EPE* in the context of the *Rugged Battery Charger* constructional project (pages 10-11, May 2014 issue).

AC sources in parallel

For AC generators, the voltage, phase and frequency must be matched prior to connecting their outputs together. This means their speed of rotation must be matched. If generators are connected in parallel while out of phase they will experience strong mechanical stresses as they are forced to synchronise quickly. This and/or high current flow may cause damage. There are numerous other potential problems, but techniques and procedures are well established in the industries where this is done. A device called a synchroscope can be used to measure the degree to which two generators are synchronised (in phase and frequency).

Basic cell technology

Batteries are often formed by connecting basic electrochemical cells in parallel to increase current capacity. Cells can also be connected in series to increase output voltage and combinations of cells in both series and parallel are often used. Battery packs based on technologies such as lithium-ion typically contain battery management circuitry which helps

maintain the required balance between the cells.

Circuit theory

Before looking at the specifics of parallel batteries we will discuss some of the circuit theory and simulator usage which might help us calculate what is happening. We need to be sure we can find out which direction the current is flowing to answer Godfrey's question.

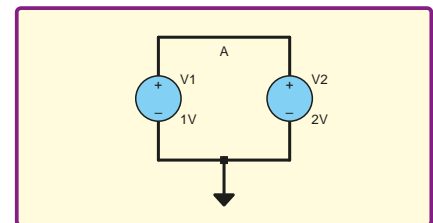


Fig.2. Two ideal voltage sources connected together

Godfrey mentioned perfect voltage sources and it is worth considering what this means. If we connect two ideal voltage sources together, as in Fig.2, what happens? One answer which springs to mind is that we have a voltage drop across zero resistance, so using Ohms law $I = V/R$ with non-zero V and zero R , we get an infinite current. A perhaps more fundamental view is that the schematic itself is meaningless. Ideal voltage sources define the voltage between two points and the schematic in Fig.1 is effectively saying that the voltage between point A and ground is both 1V and 2V. This contravenes the basic concept of what voltage is – you cannot have two different voltages between the same two points.

When we draw a schematic we intuitively understand that the lines between components will become the wiring of a physical circuit, however, this is not what the schematic really represents from a circuit theory perspective. Each connected set of 'wires' on a schematic represents a single point, called a node, which at any point in time has a single voltage (measured to some fixed reference point, usually ground) associated with it. This is illustrated in Fig.3, which shows a version of Godfrey's schematic with its three nodes labelled and highlighted.

In Fig.3 we have used voltage source symbols rather than battery symbols

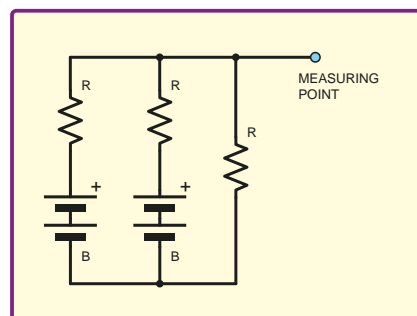


Fig.1. Godfrey's schematic

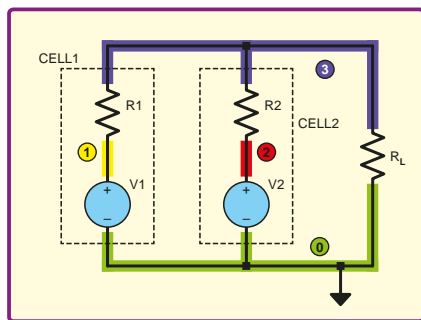


Fig.3. Redrawn with voltage sources and with nodes labelled

because the voltage source and resistor together represent a battery cell. When analysing 'batteries' we should use the term 'cell' for the individual electrochemical cells and battery for a combination of cells wired together. The parts of the schematic representing the two cells are indicated by dashed boxes in Fig.3

From the node-based perspective in Fig.3 we can redraw the schematic in the form shown in Fig.4, which is called a 'circuit graph'. Here, each set of 'wiring' collapses to a dot (the node). The components are represented by branches connecting the nodes. This format for drawing a circuit closely relates to circuit theory and the mathematical models of circuits used by simulators such as SPICE. It better represents that a node is just a point at a specific voltage and, unlike components, does not have other characteristics or parameters. The reference point (ground) from which voltages are measured is always labelled as node 0.

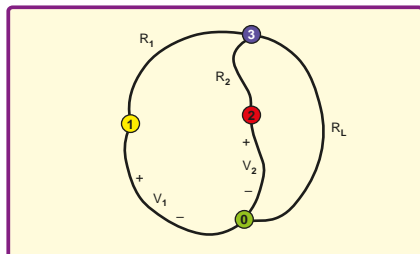


Fig.4. Circuit graph of schematic in Fig.3

Schematics can be used as an instruction on what circuit to physically build and as a mathematical representation of a real circuit. In both cases the information is incomplete. For building, the schematic does not, for example, directly define the placement of components on a board. As a mathematical representation, the schematic only takes account of a certain level of detail about the real physical circuit. If we want to include something in an analysis we have to include it in the schematic as a 'component', or as part of the mathematical model of a component (referred to as its characteristics equation).

Building simulation components

The most basic mathematical model of a resistor is the same as Ohm's law $V=IR$. This does not account for all the

behaviour of a real resistor, for example the resistance may change with temperature and applied voltage. We can write a more complex equation to represent this and then any calculation or simulation will be more accurate; that is, assuming we have the right numbers (eg, temperature coefficient) to put into it.

Using a different equation for a basic component is not the only way to obtain a better representation of reality. We can replace a physical component with two or more basic components in what is referred to as an equivalent circuit. This is exactly what Godfrey has done by including the internal resistance of the cells in his schematic. A real cell can be modelled as an ideal voltage source plus a resistor in series. These components are just representations; they not physically separable and we cannot directly measure the voltage at nodes 1 and 2 in Fig.3.

The source plus resistor model of a cell is useful to some degree for the analysis of parallel batteries, but only to a limited extent, as we will see later. Before proceeding with some calculations and simulations we will have a quickly look at Kirchhoff's laws, as Godfrey also mentioned them.

Introducing Kirchhoff

Kirchhoff's voltage law (KVL) states that the sum of the voltages, taking direction into account, around any closed loop in a circuit, is zero. KVL allows us to formulate equations relating the voltages within the circuit.

Kirchhoff's current law (KCL) states that the sum of the currents into a node is zero. Currents are taken as positive if they flow in and negative if they flow out. If we designate the wrong direction for a current at a node we will get a negative value if we calculate it when analysing the circuit. KCL allows us to write equations relating currents within the circuit. For example, at node 3 in Fig.4 we can write:

$$I_{R1} + I_{R2} - I_{R3} = 0$$

We note that I_{R3} is subtracted because we have designated it as flowing out. The graph form of the circuit (Fig.4) makes the idea of 'currents into a node' clearer than a schematic, where the connection may be a convoluted path with many joins.

KVL and KCL deal with just voltages and just currents separately. Voltage and current are related by the characteristic equations of the components in the circuit, such as $V=IR$ for a basic resistor.

Simulation

Although we can perform circuit analysis by hand it may be quicker to use an analogue simulator like LTSpice

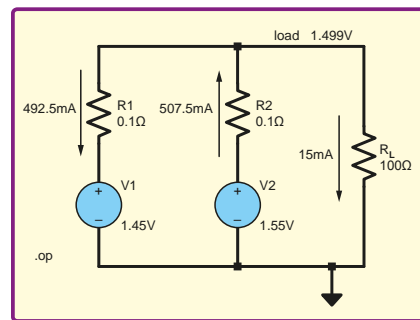


Fig.5. Example cell voltages

--- Operating Point ---

V(n001):	1.45	voltage
V(n002):	1.55	voltage
V(load):	1.49925	voltage
I(R1):	0.0149925	device_current
I(R2):	-0.507496	device_current
I(R1):	0.492504	device_current
I(V2):	-0.507496	device_current
I(V1):	0.492504	device_current

to do the work for us. The situation described by Godfrey can be analysed using an operating point simulation (.op directive) in SPICE. The result is simply a list of the currents and voltages in the circuit. For example, the result for the circuit in Fig.5 is shown above. The values used in Fig.5 are not meant to represent any type of real battery, but just serve to illustrate interaction between two voltage sources in parallel.

In these results, some of the resistor currents are positive and others are negative. This sometimes causes confusion when interpreting SPICE results. There are a couple of key things which help with understanding this. First, remember that SPICE circuits are actually described by a text file called a netlist, not directly by the schematic. Second, in any circuit analysis, as mentioned above, we may choose to designate an arbitrary current direction through any component (which we then assume is the current direction in our analysis). If the actual current is in the opposite direction to our designation the calculation will yield a negative value.

SPICE designates current direction in accordance with the order of the connections in the netlist, however this is not visible on the schematic. If you view the netlist for the circuit in Fig.6 (View > SPICE Netlist on the menu), it will be something like the following:

```
V1 N001 0 1.45
V2 N002 0 1.55
R1 load N001 0.1
R2 load N002 0.1
RL load 0 100
.op
* V
* V
.backanno
.end
```

If you use the schematic editor to rotate R_1 by 180 degrees and view the netlist again, the line for R_2 will change to:

```
R2 N002 load 0.1
```


and the sign of the current will change if you rerun the operating point simulation.

If you are uncertain about the actual direction of the current through a resistor in SPICE look at the voltages on both sides. The current flows from the more positive to the more negative voltage. From a netlist perspective the current is designated from the first connection (node) to the second (for example from node load to node N001 for R_1 in the netlist above) and the result will be negative if the actual flow is opposite to this.

Simulating the battery question

LTSpice is able to print current and voltage values from an operating point analysis on the schematic. To do this, right-click a blank part of the schematic and select View > Place .op Data Label. Place the label, right click it and edit the text in the expression box. For example, to print the current in R_2 use $I(R2)$. You can also print the result of mathematical expressions based on the data values. By default, LTSpice prints many digits, but this can be reduced using rounding expression, for example:

```
round(I(R2)*1k)/1k
```

In Fig.5 there is a 0.1V voltage difference between the internal voltage of the two cells, and each has the same internal resistance of 0.1Ω . Ignoring the load for a moment, we see that the voltage difference is 0.1V and the resistance between the two sources is 0.2Ω , so we would expect the current between the sources to be about 500mA ($I = V/R = 0.1/0.2$). This is confirmed by the simulation results. In general, battery cells will have low internal resistance, so even quite small voltage difference can result in very high currents when they are first connected.

In the situation in Fig.5, the cell represented by V_1 and R_1 (cell 1) would be charged by the cell represented by V_2 and R_2 (cell 2), as described by Godfrey. That is, if the currents were not too high for the cells to cope with and cell 1 was able to accept charge. Cell 2 also provides current to the load.

One question that might arise is, can both cells provide current to the load if their voltages are not equal? The answer is yes if the load resistance is small enough. We can calculate the point from which this occurs by working out the load for which the current in/out of the cell with the lowest voltage is zero. This requires the voltage at the load to be equal to the lower source voltage.

If the current in V_1 and R_1 is zero then we can think of R_2 and R_L as a potential divider which is not loaded/affected by V_1 and R_1 . If there is no current in R_1 then there is no voltage drop across it, so the voltage at the load must be equal to V_1 . Using the potential divider formula this will be:

$$V_{\text{load}} = \frac{R_L V_2}{R_2 + R_L} = V_1$$

which we can rearrange to give:

$$R_L = \frac{R_2 V_1}{V_2 - V_1}$$

For our example this is $(0.1 \times 1.45)/(1.55 - 1.45) = 1.45\Omega$. Simulation results for this situation are shown in Fig.7. More generally, this equation shows that the closer the cell voltages are together the larger the load resistance to which they will both contribute current.

The example we have just looked at is a kind of 'reversal' point, to use Godfrey's term, but this is related to the load not the interaction between the cells. The approach we have used so far models the cells in terms of ideal voltage sources with internal resistance. This approach cannot explain what happens with batteries' cells in detail because an ideal voltage source cannot be charged or discharged like a cell; however, looking at the circuit like this has provided some insights into the behaviour of parallel voltage sources.

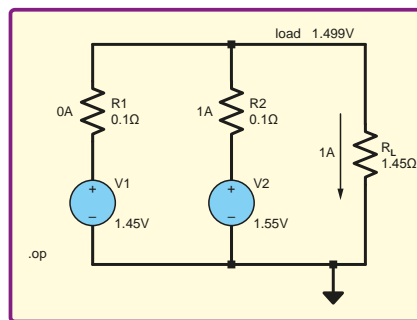


Fig.6. Further example cell voltages

When real rechargeable cells are connected in parallel one will charge the other until a balance point is reached. This process will take a certain amount of time to complete. However, the circuits we have used so far do not model this. If we run a time-based (transient) simulation of the circuits in Fig.5 and Fig.6 nothing will change. The model of the cells

used in these circuits does not include the charge/discharge process. The simulations in Fig.5 and Fig.6 show us the situation which would occur for the first instant in time after we simultaneously connected the two cells and the load, but that is all they show.

State of charge

A key cell parameter which we have not mentioned so far is the state of charge (SOC) which is usually defined as the proportion of its total energy capacity that the cell is currently holding. Typically, the cell voltage will decrease as its SOC decreases, but battery designers try to keep the voltage as constant as possible over a wide range of SOC and for many cells the voltage does not decrease significantly until the cell is close to being fully discharged. Despite this, if we have nominally identical cells the one with the higher SOC will have the higher voltage and current will flow from the higher SOC cell to the lower one until the SOC's equalise.

Cell behaviour

If we just consider two cells of the same type connected together (ie, with no load) the voltage at the connection point will immediately go to the average of internal voltage of the cells. For the cells in Fig.3 this is $(1.45+1.55)/2 = 1.5V$. The movement of charge between the cells will cause their individual internal voltages to move towards the average, but the voltage at the connection point will not change.

The initial current will depend on their voltage difference and internal resistance. For the cells in Fig.3, this is 500mA, as calculated earlier. This current will not be maintained, but will decrease as the SOC of the cells, and hence their voltages, equalise. If we assume the cells' internal resistances do not change much, the change in current is entirely due to change in voltage difference. Decreasing current

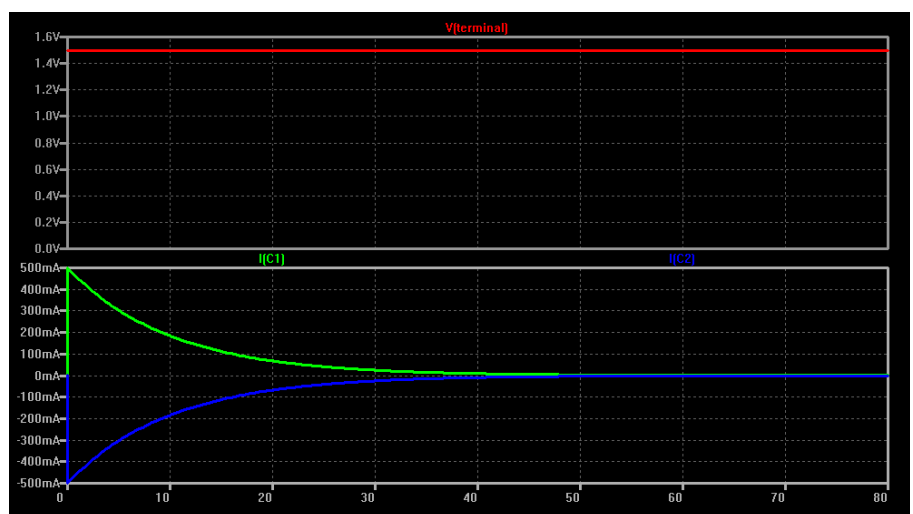


Fig.7. Plot of cell current (cell 1 – C1 and cell 2 – C2) over time for the two cells shown in Fig.3 connected at time=0 (with no load). The voltage at the connection point (V(terminal)) remains constant at the average cell voltage. The graph has arbitrary time units

will mean the rate of change of SOC and hence the rate of change of internal cell voltage will decrease as time progresses. Cells should only be connected when their SOC's are similar to avoid excessive initial current, which might damage them.

Fig.7 is a graph showing what happens over time if the two cells from Fig.3 are connected together with no external load. The voltage at the connection point, $V(\text{terminal})$, remains constant at 1.5V and the currents decrease towards zero from 500mA. This plot does not represent any specific real cell, so the time units are arbitrary.

The graph in Fig.7 was obtained in LTSpice by substituting the voltage sources with capacitors and using an initial condition to set the voltage. Actually, capacitors are a poor approximation for cells because their voltage changes steadily with SOC, unlike cells, which more or

less maintain their voltage. However, the graph in Fig.7 has about the right shape for the current curves.

The time taken for the cells to balance will depend on a number of factors, particularly: the SOC at which the cells are first connected and the degree to which they are already balanced; the internal resistance of the cells; the SOC-to-voltage relationship of the cells; the temperature; and the point closeness of SOC which is deemed to constitute balance. The exact behaviour will also depend on the cells' age and the number of charge/discharge cycles they have been through. Characteristics such as amount of capacity (energy available at 100% SOC) and internal resistance change with age. It is possible, but not necessarily easy, to model all these details for simulation purposes and discussion of this can be found in academic papers and technical websites.

Radio Bygones



The magazine for all vintage radio enthusiasts.

Covers:

- Domestic radio and TV
- Amateur radio
- Military, aeronautical or marine communications
- Radar or radio navigation
- Broadcasting
- Radio systems

Subscribe to Radio Bygones
(available by postal subscription):

1 year (6 issues)

UK £27.00

Europe £29.00

Rest of the World £34.00

OR

Download your PDF copies,
only £12.00 for one year

Tel: 01202 880299 or visit:

www.radiobygones.com

Imagine this...

- a small and inexpensive
- USB or ethernet device
- with a rich set of features
- including PLC functionality and 3- or 8-axis stepper motor controller
- all accessible via free .NET, ActiveX or C++ library
- cross-platform
- configurable with free software

PoKeys



Or this...

- Smallest USB 2.0 portable 1MS/s oscilloscope
- Data acquisition of analog and digital signals
- Data recording
- Export to CSV, XLS, PDF and HTML
- Simple usage of advanced features
- Examples for C++, VB, Delphi and LabView
- Free software and updates

PoScope Mega1+



Polabs



Visit us at

www.poscope.com

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS

ELECTRONICS TEACH-IN 2

ELECTRONICS TEACH-IN 2 CD-ROM USING PIC MICROCONTROLLERS A PRACTICAL INTRODUCTION

This *Teach-In* series of articles was originally published in *EPE* in 2008 and, following demand from readers, has now been collected together in the *Electronics Teach-In 2* CD-ROM.

The series is aimed at those using PIC microcontrollers for the first time. Each part of the series includes breadboard layouts to aid understanding and a simple programmer project is provided.

Also included are 29 *PIC N' Mix* articles, also republished from *EPE*. These provide a host of practical programming and interfacing information, mainly for those that have already got to grips with using PIC microcontrollers. An extra four part beginners guide to using the C programming language for PIC microcontrollers is also included.

The CD-ROM also contains all of the software for the *Teach-In 2* series and *PIC N' Mix* articles, plus a range of items from Microchip – the manufacturers of the PIC microcontrollers. The material has been compiled by Wimborne Publishing Ltd. with the assistance of Microchip Technology Inc.

CD-ROM Order code ETI2 CD-ROM £9.50

ELECTRONICS TEACH-IN 3

ELECTRONICS TEACH-IN 3 CD-ROM

The three sections of this CD-ROM cover a very wide range of subjects that will interest everyone involved in electronics, from hobbyists and students to professionals. The first 80-odd pages of *Teach-In 3* are dedicated to *Circuit Surgery*, the regular *EPE* clinic dealing with readers' queries on circuit design problems – from voltage regulation to using SPICE circuit simulation software.

The second section – *Practically Speaking* – covers the practical aspects of electronics construction. Again, a whole range of subjects, from soldering to avoiding problems with static electricity and identifying components, are covered. Finally, our collection of *Ingenuity Unlimited* circuits provides over 40 circuit designs submitted by the readers of *EPE*.

The CD-ROM also contains the complete *Electronics Teach-In 1* book, which provides a broad-based introduction to electronics in PDF form, plus interactive quizzes to test your knowledge, TINA circuit simulation software (a limited version – plus a specially written TINA Tutorial).

The *Teach-In 1* series covers everything from Electric Current through to Microprocessors and Microcontrollers and each part includes demonstration circuits to build on breadboards or to simulate on your PC.

CD-ROM Order code ETI3 CD-ROM £8.50

ELECTRONICS TEACH-IN 4

ELECTRONICS TEACH-IN 4 CD-ROM

A Broad-Based Introduction to Electronics.

The *Teach-In 4* CD-ROM covers three of the most important electronics units that are currently studied in many schools and colleges. These include, Edexcel BTEC level 2 awards and the electronics units of the new Diploma in Engineering, Level 2.

The CD-ROM also contains the full *Modern Electronics Manual*, worth £29.95. The Manual contains over 800 pages of electronics theory, projects, data, assembly instructions and web links.

A package of exceptional value that will appeal to all those interested in learning about electronics or brushing up on their theory, be they hobbyists, students or professionals.

CD-ROM Order code ETI4 CD-ROM £8.99



ELECTRONICS TEACH-IN BUNDLE – SPECIAL BUNDLE PRICE £14 FOR PARTS 1, 2 & 3

CD-ROMs

Order code ETIBUNDLE

Bundle Price £14.00

FLOWCODE 6

Now you can develop complex electronic and electromechanical systems with ease

Flowcode is one of the world's most advanced environments for electronic and electromechanical system development. Engineers use Flowcode to develop systems for control and measurement based on microcontrollers, on rugged industrial interfaces or on Windows compatible personal computers



PRICES Prices for each of the items above are: (Order form on third page)

(UK and EU customers
add VAT to 'plus VAT'
prices)

Chip Pack (Hobbyist/Student)
Pro-pack (Schools/HE/FE/Industry)
Flowkit

Flowcode 6

PICMICRO/AVR/DSPIC/PIC24 & ARM Download only

£94.80 inc. VAT
£299.00 plus VAT
£64.90 plus VAT

Please note: Due to popular demand, Flowcode PICmicro, AVR, DSPIC, PIC24 & ARM V6 are now available as a download. Please include your email address and a username (of your choice) on your order. A unique download code will then be emailed to you. If you require the CDROM as a back-up then please add an extra £14 to the above price.

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

PICmicro Multiprogrammer Board and Development Board

Suitable for use with the three software packages listed below

This flexible PICmicro microcontroller programmer board and combination board allows students and professional engineers to learn how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40 pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the MLoader utility that is free to download when you buy the multiprogrammer board. For those who want to learn, choose one or all of the packages below to use with the hardware.

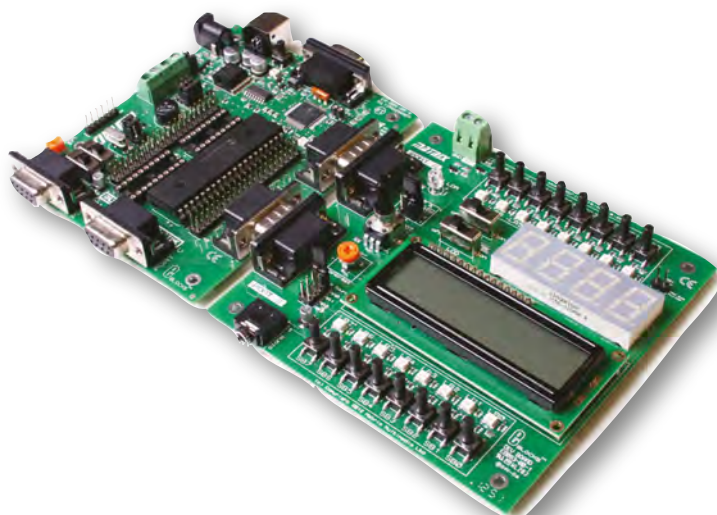- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual LEDs, quad 7-segment display and alphanumeric LCD display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Compatible with the E-blocks range of accessories



£167 including VAT and postage, supplied with USB cable and free to download programming software

SOFTWARE


ASSEMBLY FOR PICmicro V5

(Formerly PICtutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes.

The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller, this is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed, which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

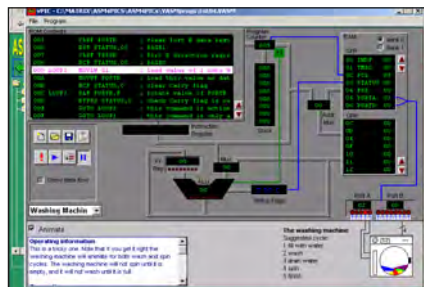


'C' FOR 16 Series PICmicro Version 5

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD-ROM contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

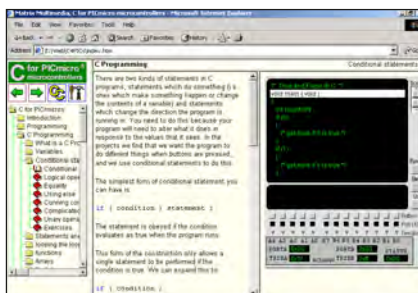- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.
Flowcode will run on XP or later operating systems

FLOWCODE FOR PICmicro V6 (see opposite page)

Flowcode is a very high level language programming system based on flowcharts. Flowcode allows you to design and simulate complex systems in a matter of minutes. A powerful language that uses macros to facilitate the control of devices like 7-segment displays, motor controllers and LCDs. The use of macros allows you to control these devices without getting bogged down in understanding the programming. When used in conjunction with the Version 3 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols
- Full on-screen simulation allows debugging and speeds up the development process.
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- 16-bit arithmetic strings and string manipulation
- Pulse width modulation
- I2C.

Features include panel creator, in circuit debug, virtual networks, C code customisation, floating point and new components. The Hobbyist/Student version is limited to 4K of code (8K on 18F devices)



PRICES

Prices for each of the CD-ROMs above are:
See previous page for Flowcode Hobbyist/Student prices (Order form on next page)

(UK and EU customers add VAT to 'plus VAT' prices)


Hobbyist/Student	£58.80	inc VAT
Professional (Schools/HE/FE/Industry)	£150	plus VAT
Professional 10 user (Network Licence)	£499	plus VAT
Site Licence	£999	plus VAT
Flowcode 10 user (Network Licence)	POA	plus VAT
Flowcode Site Licence	POA	plus VAT

CIRCUIT WIZARD

Circuit Wizard is a revolutionary software system that combines circuit design, PCB design, simulation and CAD/CAM manufacture in one complete package. Two versions are available, Standard or Professional.

By integrating the entire design process, Circuit Wizard provides you with all the tools necessary to produce an electronics project from start to finish – even including on-screen testing of the PCB prior to construction!

- * Circuit diagram design with component library (500 components Standard, 1500 components Professional)
- * Virtual instruments (4 Standard, 7 professional)
- * On-screen animation
- * Interactive circuit diagram simulation
- * True analogue/digital simulation
- * Simulation of component destruction
- * PCB Layout
- * Interactive PCB layout simulation
- * Automatic PCB routing
- * Gerber export
- * Multi-level zoom (25% to 1000%)
- * Multiple undo and redo
- * Copy and paste to other software
- * Multiple document support

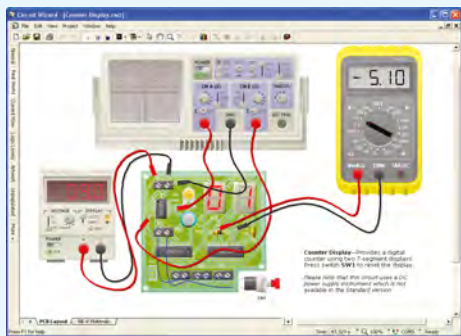

This software can be used with the *Jump Start* and *Teach-In 2011* series (and the *Teach-In 4* book).

Standard £61.25 inc. VAT Professional £91.90 inc. VAT

GCSE ELECTRONICS



Suitable for any student who is serious about studying and who wants to achieve the best grade possible. Each program's clear, patient and structured delivery will aid understanding of electronics and assist in developing a confident approach to answering GCSE questions. The CD-ROM will be invaluable to anyone studying electronics, not just GCSE students.

- * Contains comprehensive teaching material to cover the National Curriculum syllabus
- * Regular exercises reinforce the teaching points
- * Retains student interest with high quality animation and graphics
- * Stimulates learning through interactive exercises
- * Provides sample examination questions with model solutions
- * Authored by practising teachers
- * Covers all UK examination board syllabuses
- * Caters for all levels of ability
- * Useful for self-tuition and revision

SUBJECTS COVERED

Electric Circuits – Logic Gates – Capacitors & Inductors – Relays – Transistors – Electric Transducers – Operational Amplifiers – Radio Circuits – Test Instruments

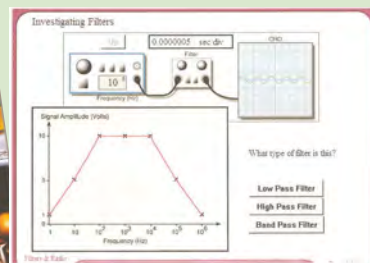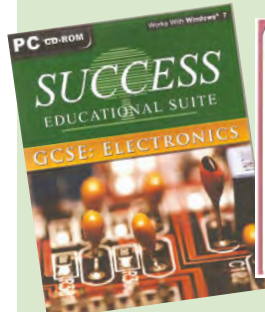Over 100 different sections under the above headings



£12.50 inc. VAT and P&P

Please send me: CD-ROM ORDER FORM

- ☐ Assembly for PICmicro V5
- ☐ 'C' for 16 Series PICmicro V5

- Version required:
- ☐ Hobbyist/Student
 - ☐ Professional
 - ☐ Professional 10 user
 - ☐ Site licence

- ☐ Flowcode for PICmicro V6 (DOWNLOAD ONLY)
- ☐ Flowcode for AVR V6 (DOWNLOAD ONLY)
- ☐ Flowcode for ARM V6 (DOWNLOAD ONLY)
- ☐ Flowcode for dsPIC V6 (DOWNLOAD ONLY)
- ☐ Flowcode for PIC24 V6 (DOWNLOAD ONLY)
- ☐ Flowkit

- Version required:
- ☐ Chip pack (Hobbyist/Student)
 - ☐ Pro pack (Schools/HE/FE/Ind.)

Email:

Username:

Note: The software on each version is the same, only the licence for use varies.

- ☐ PICmicro Multiprogrammer Board and Development Board V4 (hardware)

- ☐ Circuit Wizard – Standard
- ☐ Circuit Wizard – Professional
- ☐ GCSE Electronics

- ☐ Teach-In 2
- ☐ Teach-In 3
- ☐ Teach-In 4
- ☐ Teach-In Bundle

Full name:

Address:

Post code: Tel. No:

Signature:

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

☐ Please charge my Visa/Mastercard/Maestro: £

Valid From: Card expiry date:

Card No: Maestro Issue No.

Card Security Code (The last 3 digits on or just under the signature strip)



Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 2000/ME/XP, mouse, sound card, web browser.

ORDERING ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard/Hobbyist Version price includes postage to most countries in the world
EU residents outside the UK add £5 for airmail postage per order

Professional, Multiple User and Site License Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add VAT at 20% or provide your official VAT registration number).

Send your order to:
Direct Book Service
Wimborne Publishing Ltd
113 Lynwood Drive, Merley,
Wimborne, Dorset BH21 1UU

To order by phone ring

01202 880299. Fax: 01202 843233

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.com

PicoScope[®]

PC-OSCILLOSCOPES

For every application there's a PicoScope

- Bandwidth from 5 MHz to 1 GHz
- Sampling from 10 MS/s to 5 GS/s
- Memory from 8 ks to 2 GS

PICOSCOPE 6000 SERIES

Ultimate performance,
now USB 3.0



PICOSCOPE 5000 SERIES

Flexible resolution
oscilloscopes




PICOSCOPE 4824

8 Channels,
high resolution



PICOSCOPE 3400 SERIES

High-performance
oscilloscopes

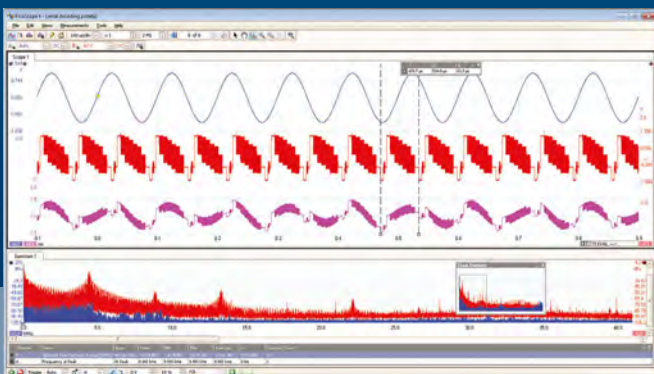

ALL MODELS INCLUDE FULL SOFTWARE AND 5 YEAR WARRANTY. SOFTWARE INCLUDES MEASUREMENTS, SPECTRUM ANALYZER, SDK, ADVANCED TRIGGERS, COLOR PERSISTENCE, SERIAL DECODING (CAN, LIN, RS232, I²C, I²S, FLEXRAY, SPI), MASKS, MATH CHANNELS, ALL AS STANDARD, WITH FREE UPDATES.


www.picotech.com/PS233

Programmable Electronics


Upgrade your Programmable Electronics to the Next Generation with

TinyDuino

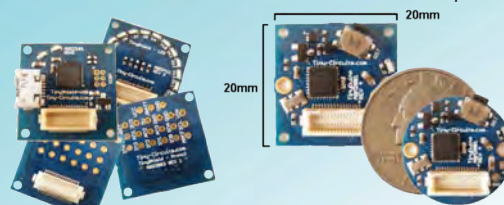As powerful as the Arduino Uno but smaller than a 2 pence coin.



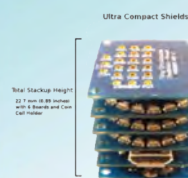All the power of the Arduino in a fraction of the space, great for building intelligence in to your projects.



Complete with a wide and growing range of **TinyShields** - where will your next project take you?

Move up to the Next Generation!

Fantastic for schools especially D&T and Computing, meets the new requirements



As an authorised reseller with an educational and training focus we can support all aspects of this outstanding piece of kit!

Get yours today via our **eShop**

ICSAT

www.eshop.icsat.co.uk

e CRICKLEWOOD ELECTRONICS


Established 1981



Frustrated with your supplier?
Visit our component packed
website for a vast range of
parts - old and new,
many unavailable elsewhere!
www.cricklewoodelectronics.com

1000's OF PRICES REDUCED!

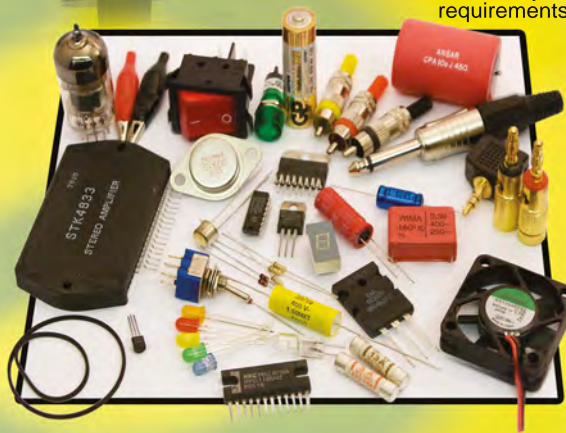Alternatively phone us on
020 8452 0161 with your
requirements.



Visit our Shop, Call or Buy online at:
www.cricklewoodelectronics.com

020 8452 0161 Visit our shop at:
40-42 Cricklewood Broadway
London NW2 3ET




NET WORK

by Alan Winstanley

Feeling vulnerable

DOUBT if any Windows XP user has avoided the marketing onslaught that reminds them that XP has reached the end of the road, at least as far as downloading security updates and patches is concerned. To quote Microsoft directly, 'PCs running Windows XP after April 8, 2014 should not be considered to be truly protected.' However, it would be fair to say that PCs running XP or any other system before that date were not truly protected, either. Microsoft Internet Explorer is stuck at version 8 in Windows XP, and it gets the blame for harbouring potential security vulnerabilities. An ever-present risk that web surfers face is that suspicious or dodgy websites could cause malicious code to be executed in the browser, which could then allow access to the operating system, personal data or it could wreak havoc over an attached network. To overcome these risks, Microsoft implores users to upgrade to Windows 7 or 8 to 'help protect your computer from malicious attacks'. While these are indeed fine operating systems, an upgrade still does not mean that users will then enjoy 'true protection'. It's just that it is more viable to patch flaws in modern operating systems when new threats come to light.

Microsoft, having finally pulled the plug on the ancient OS, has however relented on the idea that no further updates to XP or IE8 would be supplied after 8 April, at least for one exception anyway. On 1 May, another vulnerability in Internet Explorer was discovered that Microsoft classed as 'critical'. Their Security Bulletin MS14-021 describes how the issue affects all browsers from IE6 up to IE11 and a patch is available via Windows Update – and that *includes* Windows XP. Microsoft decided to include XP because the patch came so soon after the XP cut-off, as explained in the official Microsoft Blog at <http://tinyurl.com/n86y7sp>. Perhaps bolting an XP patch onto the latest Windows Update was trivial, but it seems highly unlikely that any further such patches will be supplied. Visit: update.microsoft.com for details. As usual, the website will detect your current OS and genuine Windows licence holders can then download the patch.

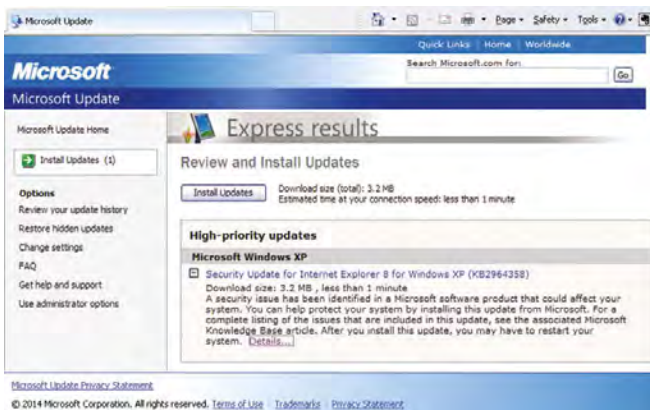

Visit update.microsoft.com to fetch the final patch for Windows XP. Later versions access Windows Update via the Start button



Almost certainly the last ever Microsoft update for Windows XP and IE8

Not just browsers

This type of problem is not restricted to web browsers – it affects other common software tools used by everyday web surfers, notably Adobe Flash and Adobe Reader, which view PDFs. A regular stream of patches helps guard against malicious exploits that can find their way onto a user's system, sometimes without the user's knowledge. It is strongly recommended that readers ensure that both Adobe Reader and Flash are always kept up to date by visiting the Adobe website. These products are often taken for granted, but need regular maintenance. For surfing, users of Windows XP are recommended to switch to Firefox, Google Chrome or Opera (see last month) as these receive constant updates and are likely to be more secure. Firefox is currently at Version 28.0 and runs very well in Windows XP, even on an old machine.

Vulnerabilities in software take many forms and the upkeep of security is a never-ending game of cat and mouse. It is a moot point whether much of the talk is simply alarmist, with little if any practical risk actually being posed to ordinary web users. After all, the chances of a web surfer stumbling upon, say, an obscure Chinese or Brazilian website that hosts a dangerous new exploit that's just been released into the wild are probably slim, but you never know. Of course, it's good practice to be vigilant and to keep browsers and software as up to date as you possibly can, and back up any critical data on disk or online. It is more likely that ordinary email poses a greater danger, especially if a friend's address book is hacked and used to broadcast spam or viruses to everyone else on the list, sent from a recognised email address. Social engineering techniques can also be used to trick people into clicking a link or opening a file.

It is feasible for an attacker to infiltrate via a back door as well, perhaps posing as an email attachment or lurking on a USB stick. Router firewall protection will not help when malware sneaks in from behind, and some exploits can even attack the router (especially if the default admin password is used!). Such attacks can cause a network's DNS settings

to be altered; for instance, a web browser could be tricked into reaching out to a malicious carbon copy of a banking website where some logins can be captured by criminals.

Countdown to Zero


A so-called 'Zero Day' vulnerability is one that exists either in the wild, or in theory, and is presently unpatched. The race is then on for software vendors to release a fix. Vulnerabilities are tabulated through the 'US Government Common Vulnerabilities and Exposures' list. Such is the tidal wave of exploits that are emerging that a new indexing system had to be introduced this year to keep up with demand, allowing more than 10,000 a year to be reported. For example, CVE-2014-1776 covers the Internet Explorer vulnerability described earlier, and it appears on the US National Vulnerability Database (NVD) at <http://nvd.nist.gov>. Its database search engine lists software flaws (CVEs) all the way back to 1997. For Internet Explorer, incidentally, the first reports shown covers IE 3.01 running under Windows 95. A more user-friendly front end is available at <http://cve.mitre.org>

A recent software flaw that has caused widespread alarm goes by the name of CVE-2014-0160, or 'Heartbleed'. It was discovered by staff at Google Security and describes a bug in the encryption program OpenSSL that is found on many Internet servers. Put simply, a hacker could ask a server a simple question that elicits a brief answer, but due to the Heartbleed bug the affected server actually sends back much more information, little by little, including private encryption keys or portions of other data held in memory at the time. At the time of writing, the author is aware of only one confirmed case where Heartbleed caused data to be compromised: at the Canada Revenue Agency some Social Security numbers were stolen (900 stolen over six hours). It was reported that some versions of Android (4.1.1) may also suffer and a number of free Heartbleed Scanner apps can be fetched from Google Play to check this.

Last month, I also mentioned the Synology NAS, an excellent disk-drive unit that attaches to a network to offer RAID-like storage. Following a disk problem I updated the drive to use two Western Digital 'Red' hard disks that are intended for Enterprise or NAS use, being near silent in operation and seemingly running cooler than previous disks. My Synology NAS also updated itself automatically with the latest patch to guard against Heartbleed. There has been worldwide coverage of Heartbleed and surfers have been implored to change all their passwords, just in case. After many years of practical experience I can strongly recommend Roboform password management software and an alternative service from lastpass.com is also worth investigating.

Intelligent lighting

Opto-electronics is one of the most exciting branches of electronics technology, and many promising new developments are in the pipeline as the problems of LED heat dissipation and efficiency are gradually overcome with each successive generation. In May's *Net Work*, my item on Philips Hue wireless LED lighting showed what's in store for intelligent and highly efficient lighting that can be controlled by a smartphone or tablet. Hard on its heels comes a new range of white 'smartbulbs' from South Korea's LG (formerly Lucky Goldstar). Again, a tablet or smartphone (iOS or Android) app can control the bulb's intensity, but apart from claiming to offer direct Wi-Fi control the 10W (60W equivalent) smart bulbs also have Bluetooth built in. Security modes, gentle wake-up and sound-to-light disco modes (Android) are offered. Currently available only in Korea, the price is approximately \$35-\$40 per bulb. Keep an eye out for new LED bulbs from Samsung too, who are expected to offer PAR-style LED bulbs and fluorescent-tube form-factor bulbs – again, with Bluetooth built in to allow direct smartphone control. An intriguing website that monitors technology and media over the border in DPRK (North Korea) is at: www.northkoreatech.org, which gives another perspective of life and events in that part of the Korean peninsula.

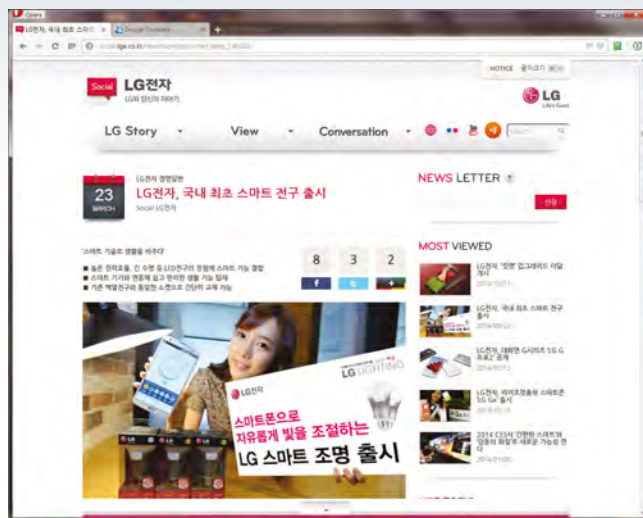

LG Smart Bulb website pictured – Google Translate can convert Korean dialect into acceptable English

Smart home

In the future smart home, the domestic deep freezer will hook onto the network and will be controllable using a tablet or smartphone app. In years to come it might adjust itself automatically depending on the weather forecast provided by another app, or warn of forthcoming power failures due to scheduled network maintenance. However, the deep freezer cannot directly track the throughput of frozen food as no data is captured about food usage or stocks. That's one step too far, but the next best thing is already on the horizon.



Currently on trial in the US, Amazon Dash is a Wi-Fi scanner that adds food or produce to your shopping list automatically

In my day, a shopping list could be phoned through to the village grocer who delivered the week's groceries in his car: rifling through the box of goodies was a great adventure for a small boy. Fast forward half a century and we have online ordering and deliveries to our door in the time slot of our choice. Amazon is showing the way ahead with the latest device to hook onto the home network: Amazon's Dash is a six-inch wand scanner that works on Wi-Fi and scans the barcodes of fresh produce. Customers can scan an order and add it to their AmazonFresh shopping list ready for home delivery, and if barcode scanning is just too tiresome then voice recognition is built into each wand as well. It's designed to help with stocking up everyday household staples and groceries. Couple it with the promise of Amazon drone aircraft (Prime Air – see: www.youtube.com/watch?v=98Blu9dpwHU) currently under trial, then maybe there is the long-term prospect of having regular replenishments of groceries dropping in from the sky. In Britain, a highly-tuned transport network is already very well honed in making doorstep deliveries to consumers, and perhaps Amazon's Dash – or any other supermarket scanner – may eventually become as routine as phoning the grocer was 50 years ago. Amazon Dash is currently on trial in the US for invited customers only.

You can email the author at alan@epemag.demon.co.uk

DIRECT BOOK SERVICE

NEW BOOKS

AN INTRODUCTION TO THE NEXUS 7

This book is intended for the new user of the Nexus 7, although much of it will also apply to the Nexus 10. It is easy to understand being written in plain English and avoiding technical jargon wherever possible.

Among the many useful topics covered are: An overview of the main features of the Nexus 7; setting up the Nexus 7; charging the battery; connecting to the Internet and signing up for Gmail; touch-screen operation and navigating around the various screens; installing Apps from the Google Play Store; setting a password and other precautions to keep your files safe; connecting accessories such as a USB Drive, mouse and keyboard; enjoying entertainment such as eBooks, games, music and videos; searching the Internet, including speaking in keywords; using e-mail, Skype and social networking; installing the free Google Drive app to save your documents in the cloud; using Google Docs free word processing and spreadsheet software; printing a document using Google Cloud Print; Exporting Nexus 7 files to laptop and desktop computers; and much more besides....

Even if you are a complete beginner, this book will help you to easily acquire the skills needed to understand and make the most of the Nexus 7.

118 Pages

Order code BP744

£8.99

KINDLE FIRE HDX EXPLAINED

This book is written to help users get to grips, quickly and easily, with the amazing Kindle Fire HDX tablet. You will be guided through the configuration and use of the Kindle Fire HDXs facilities and functions. This book was written using the 7" HDX but it is also applicable to the 8.9" model.

Among the many topics covered are: An overview of the Kindle Fire HDX. Charging and setting up, connecting to a Wi-Fi network, registering the device and connecting to Social Networks; setting up and using the 1-Click Amazon account for buying and downloading books, music and other content that you have searched for. Explaining the use of the Carousel. Starting screen Apps. Web and Device settings and the May-day facility; browsing the web with Silk Internet explorer, using Bookmarks and History, printing web pages, documents and messages; connecting to a server to send and receive e-mail messages, using and saving attachments. Creating and organising your Contacts and Calendar appointments; using the Kindle Fire camera to take photos and videos. Watching TV, listening to music you bought, imported and from the radio. Using the X-ray feature with books and other media; Using the OfficeSuite to view your documents, upgrading to OfficeSuite Professional 7 to allow both viewing and creation of Word documents. Excel spreadsheets and PowerPoint presentations. And more besides....

This book will help you acquire the skills needed to understand and make the most of your Kindle Fire HDX.

118 Pages

Order code BP743

£8.99

WINDOWS 8.1 EXPLAINED

Windows 8.1 is the latest version of Microsoft's operating system. It is installed on all new Windows Desktop, Laptop and X86 tablet computers and is also available as a free upgrade. Whether you choose to use the touch screen Tile interface or the mouse operated Desktop interface, a good working knowledge of the operating system is essential to get the most from your computer and this book will help you to do just that.

The book applies to Windows 8.1, Windows 8.1 Pro and the vast majority of Windows 8.1 Enterprise. Also parts of the book should be applicable to windows RT 8.1 which is built on the same foundation as Windows 8.1 but is a restricted version designed specifically for ARM tablets.

Among the many topic covered are: An overview of the Tile Interface, Desktop, Taskbar, Tray Notification Area, Charms bar and running Apps; managing Windows settings, personalising your PC and creating User Accounts; using the Desktop File Explorer, SkyDrive, Internet Explorer and the E-mail App; working with and organising digital photographs, using Media Player to play and store music and to burn CDs and installing Media Center to play DVDs; connecting to wireless networks, setting up a HomeGroup, sharing a printer and networked PCs; using mobility tools to keep your laptop running while away from home; accessibility features should you have dexterity or eyesight problems; keeping your computer healthy and backing up important files; And much more besides.....

180 Pages

Order code BP747

£10.99



ELECTRONICS TEACH-IN 5

ELECTRONICS TEACH-IN 5

Jump Start – 15 design and build circuit projects dedicated to newcomers or those following courses in school and colleges. The projects are: Moisture Detector, Quiz Machine, Battery Voltage Checker, Solar-Powered Charger, Versatile Theft Alarm, Spooky Circuits, Frost Alarm, Mini Christmas Lights, iPod Speaker, Logic Probe, DC Motor Controller, Egg Timer, Signal Injector Probe, Simple Radio Receiver, Temperature Alarm.

PLUS:

PIC'N MIX – starting out with PIC Microcontrollers and PRACTICALLY SPEAKING – the techniques of project construction.

FREE CD-ROM – The free CD-ROM is the complete Teach-In 2 book providing a practical introduction to PIC Microprocessors plus MikroElektronika, Microchip and L-Tek PoScope software.

160 Pages

Order code ET15

£8.99

FREE
CD-ROM

MICROPROCESSORS

INTERFACING PIC MICROCONTROLLERS

Martin Bates

298 pages

Order code NE48

£30.99

PROGRAMMING 16-BIT PIC MICROCONTROLLERS IN C – LEARNING TO FLY THE PIC24 Lucio Di Jasio (Application Segments Manager, Microchip, USA)

496 pages +CD-ROM

Order code NE45

£38.00

INTRODUCTION TO MICROPROCESSORS AND MICROCONTROLLERS – SECOND EDITION John Crisp

222 pages

Order code NE31

£29.99

THE PIC MICROCONTROLLER YOUR PERSONAL INTRODUCTORY COURSE – THIRD EDITION. John Morton

270 pages

Order code NE36

£25.00

PIC IN PRACTICE (2nd Edition) David W. Smith

308 pages

Order code NE39

£24.99

MICROCONTROLLER COOKBOOK Mike James

240 pages

Order code NE26

£36.99

PROJECT CONSTRUCTION

IC 555 PROJECTS

E. A. Parr

167 pages

Order code BP44

£5.49

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

135 pages

Order code BP392

£5.99

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

132 pages

Order code BP374

£5.45

THEORY AND REFERENCE

PRACTICAL ELECTRONICS HANDBOOK – Fifth Edition. Ian Sinclair

440 pages

Order code NE21

£32.50



STARTING ELECTRONICS – 4th Edition

Keith Brindley

296 pages

Order code NE100

£18.99

ELECTRONIC CIRCUITS – FUNDAMENTALS & APPLICATIONS – Third Edition Mike Tooley

400 pages

Order code TF43

£25.99

FUNDAMENTAL ELECTRICAL AND ELECTRONIC PRINCIPLES – Third Edition C.R. Robertson

368 pages

Order code TF47

£21.99

A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R.A. Penfold

142 pages

OUT OF PRINT BP332

£5.45

UNDERSTANDING ELECTRONIC CONTROL SYSTEMS

Owen Bishop

228 pages

Order code NE35

£36.99

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the next page.

FOR A FULL DESCRIPTION OF THESE BOOKS AND CD-ROMS SEE THE SHOP ON OUR WEBSITE

www.epemag.com

All prices include UK postage



RASPBERRY PI

RASPBERRY PI MANUAL: A practical guide to the revolutionary small computer

176 pages

Order code H001

£17.99

RASPBERRY PI USER-GUIDE

262 pages

Order code JW001

£12.99

PROGRAMMING THE RASPBERRY PI

192 pages

Order code MGH4

£10.99

GETTING STARTED WITH RASPBERRY PI

164 pages

Order code OR01

£11.50


FAULT FINDING AND TEST EQUIPMENT

GETTING THE MOST FROM YOUR MULTIMETER R. A. Penfold

96 pages Order code BP239 £5.49

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING Robin Pain

274 pages Order code NE22 £41.99

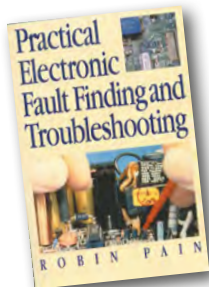

HOW ELECTRONIC THINGS WORK - AND WHAT TO DO WHEN THEY DON'T Robert Goodman

394 pages Order code MGH3 £21.99

OSCILLOSCOPES - FIFTH EDITION Ian Hickman

288 pages Order code NE37 £36.99

HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT R.A. Penfold

104 pages Order code BP267 £5.49

AUDIO & VIDEO

VALVE AMPLIFIERS - Second Edition Morgan Jones

288 pages Order code NE33 £40.99

BUILDING VALVE AMPLIFIERS Morgan Jones

368 pages Order code NE40 £29.00

QUICK GUIDE TO MP3 AND DIGITAL MUSIC Ian Waugh

60 pages Order code PC119 £7.45

MAKING MUSIC WITH YOUR COMPUTER Stephen Bennett

92 pages Order code PC120 £10.95

QUICK GUIDE TO DIGITAL AUDIO RECORDING Ian Waugh

208 pages Order code PC121 £7.95

ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS R.A. Penfold

109 pages Order code BP356 £5.45



COMPUTING AND ROBOTICS

NEWNES INTERFACING COMPANION Tony Fischer-Cripps

295 pages Order code NE38 £41.00

HOW TO BUILD A COMPUTER MADE EASY R.A. Penfold

120 pages Order code BP707 £8.49

EASY PC CASE MODDING R.A. Penfold

192 pages + CDROM Order code BP542 £8.99

FREE DOWNLOADS TO PEP-UP AND PROTECT YOUR PC R.A. Penfold

128 pages Order code BP722 £7.99

WINDOWS XP EXPLAINED N. Kantaris and P.R.M. Oliver

264 pages Order code BP514 £7.99

THE INTERNET - TWEAKS, TIPS AND TRICKS R. A. Penfold

128 pages Order code BP721 £7.99

eBAY - TWEAKS, TIPS AND TRICKS R. A. Penfold

128 pages Order code BP716 £7.50

AN INTRODUCTION TO eBAY FOR THE OLDER GENERATION Cherry Nixon

120 pages Order code BP709 £8.49

COMPUTING FOR THE OLDER GENERATION Jim Gatenby

308 pages Order code BP601 £8.99

ANDROIDS, ROBOTS AND ANIMATRONICS Second Edition - John Iovine

224 pages Order code MGH1 £16.99

ROBOT BUILDERS COOKBOOK Owen Bishop

366 pages Order code NE46 £26.00

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS Robert Penfold

288 pages + Order code BP901 £14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS - Robert Penfold

298 pages Order code BP902 £14.99

HOW TO FIX YOUR PC PROBLEMS R. A. Penfold

128 pages Order code BP705 £8.49

WINDOWS 7 - TWEAKS, TIPS AND TRICKS Andrew Edney

120 pages Order code BP708 £8.49

GETTING STARTED IN COMPUTING FOR THE OLDER GENERATION Jim Gatenby

120 pages Order code BP704 £8.49

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £3 per book. Surface mail can take up to 10 weeks to some countries. For the rest of the world airmail add £4 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard or Maestro to: **DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LIMITED, 113 LYNWOOD DRIVE, MERLEY, WIMBORNE, DORSET BH21 1UU.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery - more for overseas orders. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a full description of these books please see the shop on our website.
Tel 01202 880299 Fax 01202 843233. E-mail: dbs@wimborne.co.uk

Order from our online shop at: www.epemag.com

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

☐ Please charge my card £ Card expiry date:

Card Number Maestro Issue No.

Valid From Date Card Security Code (The last three digits on or just below the signature strip)

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary

PCB SERVICE

CHECK US OUT ON THE WEB



Basic printed circuit boards for most recent *EPE* constructional projects are available from the *PCB Service*, see list. These are fabricated in glass fibre, and are drilled and roller tinned, but all holes are a standard size. They are not silk-screened, nor do they have solder resist. Double-sided boards are **NOT plated through hole** and will require 'vias' and some components soldering to both sides. * **NOTE: PCBs from the July 2013 issue with eight digit codes** have silk screen overlays and, where applicable, are double-sided, plated through-hole, with solder masks, they are similar to the photos in the relevant project articles.

All prices include VAT and postage and packing. Add £2 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 113 Lynwood Drive, Merley, Wimborne, Dorset BH21 1UU. Tel: 01202 880299; Fax 01202 843233; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.com.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (**Payment in £ sterling only**).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.

Back numbers or photocopies of articles are available if required – see the Back Issues page for details. WE DO NOT SUPPLY KITS OR COMPONENTS FOR OUR PROJECTS.

PROJECT TITLE	ORDER CODE	COST
MAY '13		
Electronic Stethoscope	898	£9.72
PIC/AVR Programming Adaptor Board (d'ble-sided)	899	£23.33
Jump Start – Signal Injector Probe	900	£8.16
JUNE '13		
USB Breakout Box	901	£7.97
Jump Start – Simple Radio Receiver	902	£8.94
Mix-It	903	£11.28
JULY '13		
6-Decade Capacitance Substitution Box	04106121	£18.00
6-Decade Capacitance Substitution Box Panel/Lid	04106122	£18.00
SoftStarter For Power Tools	10107121	£9.00
High-Current Adaptor For Scopes And DMMs	04108121	£18.00
Jump Start – Temperature Alarm	904	£7.97
AUGUST '13		
Driveway Sentry	03107121	£18.00
Build A Vox	01207111	£22.00
Milliohm Meter Adaptor For DMMs	04102101	£18.00
SEPTEMBER '13		
MiniReg Adjustable Regulator	18112111	£6.00
USB Stereo Recording Interface	07106111	£18.00
Digital Sound Effects Module	09109121	£9.00
OCTOBER '13		
High-Temperature Thermometer/Thermostat	21105121	£22.00
LED Musicolour	16110121	£22.00
NOVEMBER '13		
Mains Timer For Fans Or Lights	10108121	£9.10
CLASSIC-D Amplifier (inc. 3 Rockby Capacitors)	01108121	£26.50
– Speaker Protector	01108122	£9.10
DECEMBER '13		
CLASSIC-D Amplifier – Power Supply	01109111	£16.66
USB Instrument Interface	24109121	£26.38
– Front Panel	24109122	£28.54
JANUARY '14		
Champion	1109121/2	£8.88
Simple 1.5A Switching Regulator	18102121	£5.53
FEBRUARY '14		
2.5GHz 12-Digit Frequency Counter – Display PCB	04111122	£12.88
– Main PCB	04111121	£27.13
– Front Panel	04111123	£22.38
High-Energy Electronic Ignition System	05110121	£9.10
Mobile Phone LOUD Ringer!	12110121	£9.10
MARCH '14		
Extremely accurate GPS 1pps Timebase For A		
Frequency Counter	04103131	£8.88
Infrasound Detector – Pre CHAMP PCB	01107941	£5.54
– CHAMP PCB	01102941	£5.54

PROJECT TITLE	ORDER CODE	COST
Automatic Points Controller (inc. 2 sensor PCBs)	09103132	£13.42
Automatic Points Controller – Frog Relay	09103133	£5.54
APRIL '14		
A Capacitor Discharge Unit For Twin-Coil		
Points Motors	09203131	£9.10
Deluxe GPS 1pp Timebase For Frequency		
Counters	04104131	£16.66
Jacob's Ladder	05110121	£9.10
MAY '14		
The CLASSIC-D ±35V DC-DC Converter	11104131	£16.66
JUNE '14		
Mini Audio Mixer	01106131	£22.06
Cranial Electrical Simulation Unit	99101111	£16.66
Teach-In 2014 – Part 9 Pi Camera Light	905	£13.44
JULY '14		
Verstile 10-Channel Remote Control Receiver	15106131	£16.66
IR to 433MHz UHF Transceiver	15106132	£9.10
Li'l Pulser Model Train Controller Main PCB	09107134	£16.66
– Front & Rear Panel Set	09107132	£17.20
	09107133	

* See NOTE above left regarding PCBs with eight digit codes *

Please check price and availability in the latest issue.

A large number of older boards are listed on, and can be ordered from, our website.

Boards can only be supplied on a payment with order basis.




EPE SOFTWARE

★ All software programs for *EPE* Projects marked with a star, and others previously published can be downloaded free from the Library on our website, accessible via our home page at: www.epemag.com

PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our website (www.epemag.com); go to the 'Library' section.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code	Project	Quantity	Price
.....			
Name			
Address			
.....			
Tel. No.			
I enclose payment of £ (cheque/PO in £ sterling only) to:			
Everyday Practical Electronics			
  			
Card No.			
Valid From		Expiry Date	
Card Security No.		Maestro Issue No.	
Signature			

Note: You can also order PCBs by phone, Fax or Email or via the Shop on our website on a secure server:

<http://www.epemag.com>

CLASSIFIED

ADVERTISEMENTS

If you want your advertisements to be seen by the largest readership at the most economical price our classified page offers excellent value. The rate for semi-display space is £10 (+VAT) per centimetre high, with a minimum height of 2.5cm. All semi-display adverts have a width of 5.5cm. The prepaid rate for classified adverts is 40p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. **VAT must be added.** Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, 113 Lynwood Drive, Merley, Wimborne, Dorset, BH21 1UU. Phone: 01202 880299. Fax: 01202 843233. Email: stewart.kearn@wimborne.co.uk. For rates and information on display and classified advertising please contact our Advertisement Manager, Stewart Kearn as above.

Everyday Practical Electronics reaches more UK readers than any other UK monthly hobby electronics magazine, our sales figures prove it.

We have been the leading monthly magazine in this market for the last twenty-six years.

AUDIO TRANSFORMERS & ACCESSORIES

For full range Visit Section 5

www.partridgeelectronics.co.uk

**ADVERTISE HERE FOR
JUST £25 +VAT CALL
STEWART KEARN
ON 01202 880299
STEWART.KEARN@WIMBORNE.CO.UK**

BOWOOD ELECTRONICS LTD

Suppliers of Electronic Components

Place a secure order on our website or call our sales line

All major credit cards accepted

Web: www.bowood-electronics.co.uk

Unit 10, Boythorpe Business Park, Dock Walk, Chesterfield,

Derbyshire S40 2QR. Sales: 01246 200222

Send 60p stamp for catalogue

BTEC ELECTRONICS TECHNICIAN TRAINING

NATIONAL ELECTRONICS
VCE ADVANCED ICT
HNC AND HND ELECTRONICS
FOUNDATION DEGREES
NVQ ENGINEERING AND IT
DESIGN AND TECHNOLOGY


LONDON ELECTRONICS COLLEGE
20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: (020) 7373 8721
www.lec.org.uk

CANTERBURY WINDINGS

UK manufacturer of toroidal transformers
(10VA to 3kVA)

All transformers made to order. No design fees.
No minimum order.

www.canterburywindings.co.uk
01227 450810



Robot Bits
Robots, Arduino & more!

www.RobotBits.co.uk
0845 5 191 282

MISCELLANEOUS

KITS, TOOLS, COMPONENTS. S.A.E. Catalogue. SIR-KIT ELECTRONICS, 52 Severn Road, Clacton, CO15 3RB, <http://sir-kit.webs.com>

PIC DEVELOPMENT KITS, DTMF kits and modules, CTCSS Encoder and Decoder/Display kits. Visit www.cstech.co.uk

VALVES AND ALLIED COMPONENTS IN STOCK. Phone for free list. Valves, books and magazines wanted. Geoff Davies (Radio), tel. 01788 574774.

ADVERTISERS INDEX

BETA LAYOUT	72	RK EDUCATION	47
CadSoft COMPUTER	47	STEWART OF READING	Cover (ii)
CRICKLEWOOD ELECTRONICS	65	TECHNOBOTS	55
ESR ELECTRONIC COMPONENTS	6	TRINITY	49
iCSAT	65	ADVERTISEMENT OFFICES:	
JPG ELECTRONICS	72	113 LYNWOOD DRIVE, MERLEY, WIMBORNE,	
MICROCHIP	Cover (iv)	DORSET BH21 1UU	
LASER BUSINESS SYSTEMS	52	PHONE: 01202 880299	
L-TEK POSCOPE	61	FAX: 01202 843233	
PEAK ELECTRONIC DESIGN	Cover (ii)	EMAIL: stewart.kearn@wimborne.co.uk	
PICO TECHNOLOGY	65	WEB: www.epemag.com	
QUASAR ELECTRONICS	2/3	For editorial address and phone numbers see page 7	

Next Month

Add a UHF link to a universal remote control

Remote control extenders are old hat! Now you can add this tiny UHF module to your IR remote control and operate appliances from *anywhere* inside or outside your home.

PCBirdies

Ever wished you could have beautiful birdsong in your home, without having to own a live caged bird? With PCBirdies, you can have the luxury of not one, but two singing birds. You won't have to buy a cage or even bird seed... and best of all, there's no mess to clean up!

Active RF Detector Probe for DMMs

This low-cost detector probe allows you to measure RF signals from below 100kHz up to over 1GHz using your DMM for signal voltages between about 20mV and 10V RMS. You can use it with a probe or a sniffer loop, and you can even use it to measure the voltage across a coaxial cable load and calculate the RF power.

USB Port Voltage Checker

If you carry valuable data around on a USB flash drive, it's not a good idea to plug it into other people's computers willy-nilly. They could have dead or faulty USB ports and an incorrectly wired USB port can destroy a flash drive. Test it first with this handy project.

AUGUST '14 ISSUE ON SALE 3 JULY 2014

Content may be subject to change




WELCOME TO JPG ELECTRONICS

Selling Electronics in Chesterfield for 29 Years

**Open Monday to Friday 9am to 5:30pm
And Saturday 9:30am to 5pm**

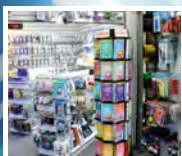- Aerials, Satellite Dishes & LCD Brackets
- Audio Adaptors, Connectors & Leads
- BT, Broadband, Network & USB Leads
- Computer Memory, Hard Drives & Parts
- DJ Equipment, Lighting & Supplies
- Extensive Electronic Components
 - ICs, Project Boxes, Relays & Resistors
- Raspberry Pi & Arduino Products
- Replacement Laptop Power Supplies
- Batteries, Fuses, Glue, Tools & Lots more...



T: 01246 211 202

E: sales@jpgelectronics.com

**JPG Electronics, Shaw's Row,
Old Road, Chesterfield, S40 2RB**

W: www.jpgelectronics.com



Retail & Trade Welcome • Free Parking • Google St View Tour: S40 2RB

PANEL-POOL®
Beta LAYOUT

Custom Front Panels

Digital printing

Free Design Software

www.panel-pool.com

25 YEARS
BETA
LAYOUT
create:electronics

PANEL-POOL® is a registered trademark of Beta LAYOUT GmbH



IT IS BACK...

**EVERYDAY PRACTICAL
ELECTRONICS IS NOW
AVAILABLE IN PDF FORMAT
AGAIN**

REQUIREMENTS:

**YOU NEED TO BE RUNNING A WINDOWS PC
USING ADOBE ACROBAT READER**

**GO TO
www.epemag.com
TO ORDER**

**SUBSCRIPTIONS CAN BE
BACK-DATED UP TO A MAXIMUM OF
3 MONTHS**

Adding Connectivity to Your Design



ZigBee®
Control your world

Wi-Fi®
CERTIFIED

Bluetooth®

Ethernet

LIN
LOCAL INTERCONNECT NETWORK

CAN

MiWi™

USB

Easy to use • Low-cost • Start designing today

Microchip offers support for a variety of wired and wireless communication protocols, including peripheral devices and solutions that are integrated with a PIC® Microcontroller (MCU) or dsPIC® Digital Signal Controller (DSC).

Microchip's Solutions include:

USB

8-, 16- and 32-bit USB MCUs for basic, low-cost applications to complex and highly integrated systems along with free license software libraries including support for USB device, host, and On-The-Go.

Ethernet

PIC MCUs with integrated 10/100 Ethernet MAC, standalone Ethernet controllers and EU1 - 48™/EU1 - 64™ enabled MAC address chips.

CAN

8-, 16- and 32-bit MCUs and 16-bit DSCs with integrated CAN, stand alone CAN controllers, CAN I/O expanders and CAN transceivers.

LIN

LIN Bus Master Nodes as well as LIN Bus Slave Nodes for 8-, 16- and 32-bit PIC MCUs and 16-bit dsPIC DSCs. The physical layer connection is supported by CAN and LIN transceivers.

Wi-Fi®

Innovative wireless chips and modules allowing a wide range of devices to connect to the Internet. Embedded IEEE Std 802.11 Wi-Fi transceiver modules and free TCP/IP stacks.

ZigBee®

Certified ZigBee Compliant Platform (ZCP) for the ZigBee PRO, ZigBee RF4CE and ZigBee 2006 protocol stacks. Microchip's solutions consist of transceiver products, PIC18, PIC24 and PIC32 MCU and dsPIC DSC families, and certified firmware protocol stacks.

MiWi™

MiWi and MiWi P2P are free proprietary protocol stacks developed by Microchip for short-range wireless networking applications based on the IEEE 802.15.4™ WPAN specification.

BEFORE YOUR NEXT WIRED OR WIRELESS DESIGN:

1. Download free software libraries
2. Find a low-cost development tool
3. Order samples

www.microchip.com/usb
www.microchip.com/ethernet
www.microchip.com/can
www.microchip.com/lin
www.microchip.com/wireless



Wi-Fi G Demo Board
(DV102412)



Microcontrollers • Digital Signal Controllers • Analog • Memory • Wireless